

EE 230 – Analog Lab - 2021-22/I (Autumn)

Experiment 2: DC Power Supply

Par A – Unregulated DC Power Supply

Learning Objectives

1. Understanding the problems associated with increasing the capacitor value in an unregulated power supply so as to reduce the ripple.
2. Understanding the limits of performance of a Zener regulator
3. Understanding a BJT based series voltage regulator to appreciate the basic blocks of an IC voltage regulator.

1.1 Step Down Transformer (15-0-15)

We will use a 15-0-15V step-down transformer. (See Fig.1), i.e. a transformer with a centre tap, hence the name 15-0-15 V transformer.

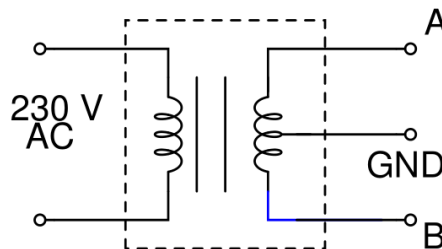


Fig 1 230 V to 15-0-15V Step-down transformer

1.2 Unregulated DC Power Supply (using Bridge Rectifier)

A) Unregulated Supply – without and with a Capacitive Filter

Fig.2 shows the circuit diagram of the unregulated DC power supply. In the absence of a Capacitor, the V_{out} waveform will be a pulsating DC waveform. Diodes used are IN4007 (Peak current = 1 A, Breakdown voltage = 1000V).

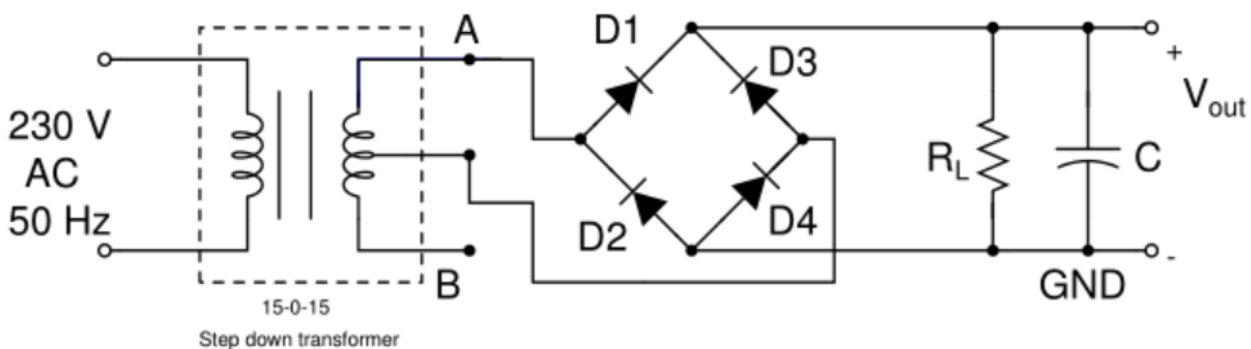


Fig. 2 Unregulated DC Power supply using a Bridge Rectifier

1.2.1 NGSPICE Simulation

Simulate the Bridge rectifier circuit. Plot the V_{out} waveform as one plot; plot the currents through the diodes D1 and D3 as the second plot. Choose $R_L = 1\text{ k}\Omega$. Do not connect any Capacitor for this part. Note that the transformer output voltage of 15 V is its RMS value. Choose a voltage source as appropriate.

Hint: You need to use the **.tran** command for analysis. Also, choose a sine waveform with the correct amplitude and frequency. Use appropriate voltage sources for obtaining the currents through D1 and D2.

Diode Model:

You need to use an appropriate diode model for the diodes used. Note that the diodes used (1N4007) are not switching diodes, but power diodes. 1N4007 has a peak current rating of 1 A and breakdown voltage 1000 V. Model for 1N914 switching diode is given below (taken from WEL Lab site).

```
.MODEL 1N914 D (IS=6.2229E-9 N=1.9224 RS=0.33636 IKF=42.843E-3 CJO=764.38E-15  
+ M=0.1001 VJ=0.99900 BV=100.14 IBV=0.25951 TT=2.8854E-9)
```

Modify the above model parameters appropriately for your simulations.

(Please refer to the Spice_3f3_Users_Manual.pdf. Available in the Google drive location shared for Expt 1. We shall discuss more on this in the Lab Lecture).

B) Unregulated Supply - with a Capacitive Filter

Once a Capacitor is connected across R_L as in Fig.2, the V_{out} waveform will become smoother, i.e. a large dc with a ripple voltage riding on it. The ripple voltage will depend on: i) the load current (or R_L), and ii) the value of C.

For a given load R_L , one solution employed by some to reduce the ripple voltage is to increase C. In the following NGSPICE simulations you should investigate and decide for yourself whether this strategy is right or not.

1.2.2 NGSPICE Simulation

Simulate and plot the V_{out} waveform of the unregulated power supply with C. Observe and estimate the approximate peak-to-peak ripple voltage. Plot the currents through the diodes D1 and D3 separately. Try simulations for the following combinations of R_L and C values.

Obtain the above plots for the following cases:

Cases (i) to (iii) : $R_L = 1\text{ k}\Omega$, and C = 100 μF , 470 μF , and 1000 μF

Cases (iv) to (vi) : $R_L = 500\ \Omega$, and C = 100 μF , 470 μF , and 1000 μF

Observation and comments:

Note the changes in the voltage and current waveforms as R_L and C are varied. Note also, the approximate ratio of peak diode current to the load current. Comment as to why for a given value of R_L , the diode currents are different for different C values.

1.3 DC Power Supply with Zener Diode Regulator

1.3.1 Zener Regulator - Analysis

Analyse the Zener diode regulator circuit given below.

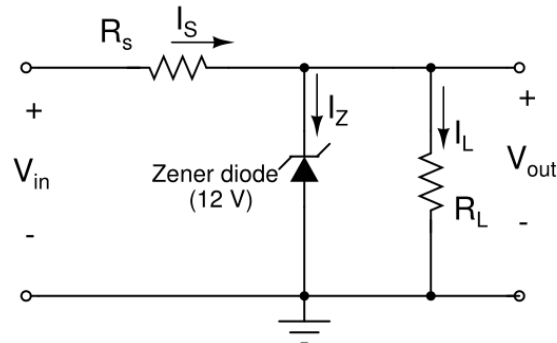


Fig.3 Zener regulator

Case (i): For $V_{in} = 20\text{ V}$ (dc). Choose $R_s = 470\ \Omega$, $R_L = 1\text{ k}\Omega$. Assume Zener voltage = 12 V and Zener region diode resistance = $125\ \Omega$. Calculate V_{out} , I_s , I_Z and I_L .

Case (ii): For V_{in} varying from 15 V to 25 V . $R_s = 470\ \Omega$, $R_L = 1\text{ k}\Omega$. (Zener voltage = 12 V and Zener region diode resistance = $125\ \Omega$). Consider a few V_{in} values between 15 and 25 V .

Hint: For a given V_{in} value, apply Thevenin's theorem and represent the Zener regulator by its equivalent Thevenin voltage and resistance. This would make it easier to calculate V_{out} , and I_L , and then I_s and I_Z .


1.3.2 NGSPICE Simulation

a) For $V_{in} = 20\text{ V}$, $R_s = 470\ \Omega$, $R_L = 1\text{ k}\Omega$, simulate and print V_{out} , I_s , I_Z and I_L . Compare your simulation results with your earlier calculations. Best to use **.op** command for this.

(For obtaining currents I_L , and then I_s and I_Z you need to put a series voltage source with zero voltage, and then print the currents).

Zener Diode Model

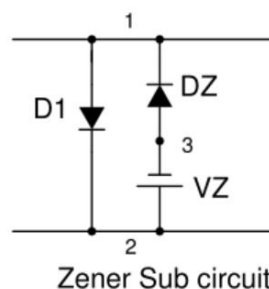The best way to model a Zener diode is to consider it as a sub-circuit consisting of a forward diode connected in parallel with a reverse diode with a dc offset. The dc offset is typically chosen to be about 1 to 1.2 V lower than the Zener voltage. We shall use the following sub circuit for the 12 V Zener diode.



```
.SUBCKT ZENER_12 1 2
D1 1 2 DF
DZ 3 1 DR
VZ 2 3 10.8
.MODEL DF D ( IS=27.5p RS=0.620 N=1.10 CJO=78.3p VJ=1.00 M=0.330 TT=50.1n )
.MODEL DR D ( IS=5.49f RS=50 N=1.77 )
.ENDS
```

You may key in the above sub circuit in your .CIR file and then use it through the sub circuit command:

x1 A K ZENER_12

where A and K are the anode and cathode nodes of the Zener diode, respectively.

b) See how well the Zener regulator regulates V_{out} for a range of V_{in} values. You should use the **.dc** command for this purpose. Format for the .dc command:

.dc source startval stopval stepsize

Obtain the V_{out} , I_S , I_Z and I_L values when V_{in} is varied from 15 to 25 V in steps of 0.5 V. (Assume $R_S = 470 \Omega$, $R_L = 1 \text{ k}\Omega$). Observe I_Z values for $V_{in} \leq 17 \text{ V}$ and explain the results.

c) For $V_{in} = 20 \text{ V}$, and $R_S = 470 \Omega$, simulate for different values of R_L lower than $1 \text{ k}\Omega$. For the given values, verify the simulation results with the theoretical value for the lowest value of R_L allowed for a Zener regulator.

1.4 DC Power Supply with a BJT Series Regulator

Circuit diagram of the BJT series regulator is shown below in Fig.4. You could think of this as the next step towards better regulation of output voltage against changes in V_{in} and R_L . This circuit has the basic blocks of a sophisticated IC regulator, such as 7812 (fixed 12 V regulator). A general-purpose adjustable Voltage regulator IC essentially has about four parts, viz. a reference voltage, an error amplifier, a series active element and a resistor network for adjusting V_{out} .

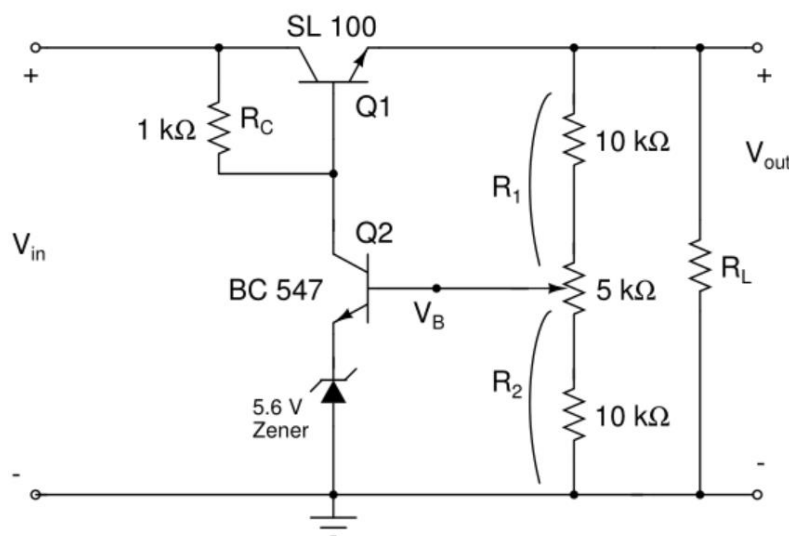


Fig.4 BJT series voltage regulator

In the circuit shown Q_1 (SL100) is a medium power BJT with β of about 100, whereas Q_2 (BC547) is a low power BJT having $\beta > 200$, which is commonly used in amplifier circuits.

Operation of the BJT Series Regulator

The BJT series regulator is a combination of a reference voltage, error amplifier, a series element for regulating the voltage and a resistor network for sampling V_{out} . In Fig 4, Zener diode acts as the reference voltage, Q_2 acts as the error amplifier and Q_1 , the series regulating element, and R_1 , R_2 and the potentiometer as the resistive network. The circuit is essentially a negative-feedback amplifier.

Note that $V_B = V_{out} \cdot R_2 / (R_1 + R_2)$, is directly proportional to V_{out} . Assume that V_{out} increases from the steady-state value due to $R_L \uparrow$ (or less load current). This would result in V_B also increasing proportionately, which

would cause more base current to flow in Q_2 and consequently more collector current in Q_2 , which would then drain away some of the base current flowing into Q_1 , resulting in increased V_{CE} drop in Q_1 , which would reduce V_{out} . Similar argument can be given for corrections when V_{out} decreases. Hence, we see that the circuit continuously samples V_{out} and corrects any voltage variations.

1.4.1 NGSPICE Simulation

BJT Models

The series regulator circuit has two BJTs, a medium power BJT and a low power BJT commonly used for small-signal amplifier applications. Their model files (sample model values) are given below. Since ours is a dc application many of the small-signal parameters are not very important for our analysis. However, the ac parameters would be required to check whether the circuit is stable or not.

```
.model bc547a NPN IS=10f BF=200 ISE=10.3f IKF=50m NE=1.3
+ BR=9.5 VAF=80 IKR=12m ISC=47p NC=2 VAR=10 RB=280 RE=1 RC=40
+ tr=0.3u tf=0.5n cje=12p vje=0.48 mje=0.5 cjc=6p vjc=0.7 mjc=0.33 kf=2f

.model SL100 NPN IS=100f BF=80 ISE=10.3f IKF=50m NE=1.3
+ BR=9.5 VAF=80 IKR=12m ISC=47p NC=2 VAR=10 RB=100 RE=1 RC=10
+ tr=0.3u tf=0.5n cje=12p vje=0.48 mje=0.5 cjc=6p vjc=0.7 mjc=0.33 kf=2f
```

Format for BJTs: Q1 C B E bc547a, where C, B and E are the Collector, Base and Emitter nodes of the BJT.

Refer to the Common Emitter amplifier example given in Chapter 21 (page 451) of the NGSPICE-34-manual. There a 'generic npn' model is used. Here we are specifying the model parameters.

Simulation

Create a .CIR file to simulate the BJT series regulator circuit of Fig.4. Use $V_{in} = 20\text{ V}$, $R_L = 1\text{ k}\Omega$.

Note that in Fig 4, the value of R_1 is: $10\text{ k}\Omega$ + part of the $5\text{ k}\Omega$ potentiometer; similarly, R_2 is: $10\text{ k}\Omega$ + the remaining part of the $5\text{ k}\Omega$ potentiometer). Hence, $R_1 + R_2 = 25\text{ k}\Omega$.

Case i) For $V_{in} = 20\text{ V}$, $R_L = 1\text{ k}\Omega$, keep $R_1 = R_2 = 12.5\text{ k}\Omega$. Print all the node voltages.

Case ii) Vary R_1 and R_2 (while keeping $R_1 + R_2 = 25\text{ k}\Omega$) so as to get $V_{out} = 12\text{ V}$ approximately.

Case iii) for the R_1 and R_2 values you got for $V_{out} = 12\text{ V}$, perform a .dc analysis. (Keep $R_L = 1\text{ k}\Omega$, and vary V_{in} from 15 V to 25 V in steps of 0.5 V). Compare these results with the ones you got for the Zener regulator.

Lab Report

1. Hereafter, in view of the hardships you may be facing due to the online mode, we want you to submit only a short Lab report, say a maximum of 3 or 4 pages.
2. For Experiment 2, please limit your Lab report to just 3 pages – one page for the Unregulated Supply with Capacitive Filter, one page for the DC Power Supply with Zener Diode Regulator, and the last page for the DC Power Supply with a BJT Series Regulator.
3. In each page, please include one of your NGSPICE programs, and one or two plots or the printed values, as the case may be. No analysis required. Please also add one line of what you learned.
4. The purpose of asking you to make shorter Lab reports is to make sure that you save some time. However, we assume that you have done all that was asked in the Lab handout (analysis and simulations). These and related topics may be asked in the Quizzes, as well as in the Midsem and Endsem examinations.