

Q1.

Analysis:

$$R_{eq} = 2.2 \parallel 10 = 1.8k. V_{eq} = 12 * 2.2 / 12.2 = 2.16V.$$

$$V_{eq} = I_b \times R_{eq} + 0.7 + (\beta + 1) * I_b * R_e \Rightarrow I_b = 7.2 \mu A.$$

$$I_c = \beta * I_b \Rightarrow I_c = 1.44 \text{ mA}$$

$$V_o = 12 - I_c * R_c = 10.272V$$

$$V_e = (\beta + 1) * I_b * R_e = 1.45V$$

$$V_b = V_e + 0.7 = 2.15V$$

Simulation:

```
v(1) = 1.474208e+00
v(2) = 2.143645e+00
v(3) = 1.024445e+01
i(v2) = 1.125117e-05
i(v3) = 1.462957e-03
```

(refer to the code below to see what node number is what node)

Code:


```
19D070052 Sheel Shah Expt3 CE Amp Biasing
.model bc547a NPN IS=10f BF=200 ISE=10.3f IKF=50m NE=1.3
+ BR=9.5 VAF=80 IKR=12m ISC=47p NC=2 VAR=10 RB=280 RE=1 RC=40
+ tr=0.3u tf=0.5n cje=12p vje=0.48 mje=0.5 cjc=6p vjc=0.7 mjc=
0.33 kf=2f
** nodes:
** 1 emitter, 2 base, 3 collector/output
** 4 Vcc
q0 3 2 1 bc547a
re 1 0 1k
r2 20 0 2.2k
r1 20 4 10k
v2 20 2 0
** to measure Ib
rc 4 30 1.2k
v3 30 3 0
** to measure Ic
vcc 4 0 12
.op
.control
run
print v(1)
print v(2)
print v(3)
print i(v2)
print i(v3)
.endc
.end
```

Learnings:

1. Not all the assumptions we make are accurate/correct.
2. Simulations and analysis can be slightly different, but shouldn't be too off.

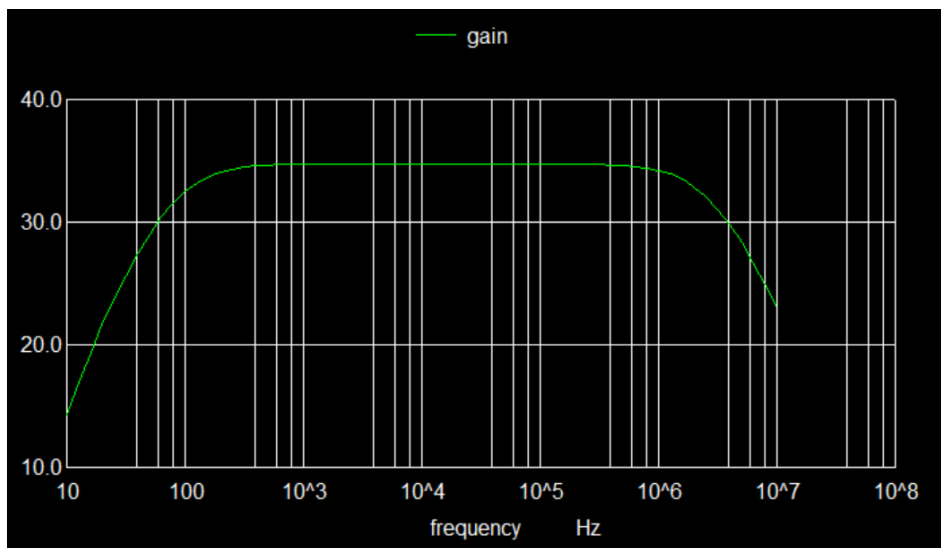Q2.

```
19D070052 Sheel Shah Expt3 CE Amp
.model bc547a NPN IS=10f BF=200 ISE=10.3f IKF=50m NE=1.3
+ BR=9.5 VAF=80 IKR=12m ISC=47p NC=2 VAR=10 RB=280 RE=1 RC=40
+ tr=0.3u tf=0.5n cje=12p vje=0.48 mje=0.5 cjc=6p vjc=0.7 mjc=
0.33 kf=2f
** nodes:
** 1 emitter, 2 base, 3 collector
** 4 Vcc
** 5 Vin
** 6 Vout
q0 3 2 1 bc547a
vcc 4 0 12
vin 5 0 dc 0 ac 10m
c1 5 2 10u
re 1 0 1k
ce 1 0 100u
r2 2 0 2.2k
r1 2 4 10k
rc 4 3 1.2k
c2 3 6 10u
rl 6 0 100k
.ac dec 10 10 0.01g
.control
run
let gain = vdb(6) - vdb(5)
meas ac peak MAX gain
let f3db = peak/sqrt(2)
meas ac fl WHEN gain=f3db RISE=1
meas ac fh WHEN gain=f3db FALL=1
plot gain
.endc
.end
```



```
peak          = 3.474902e+01 at= 1.584893e+04
fl            = 2.803502e+01
fh            = 8.382100e+06
fh - fl = 8.382072e+06
```

Learnings:


The CE amp has good gain, and a decent bandwidth. However, we know that  $R_{in}$  and  $R_{out}$  values are not appropriate.

Q3.

```
19D070052 Sheel Shah Expt3 CE Amp Biasing
.model bc547a NPN IS=10f BF=200 ISE=10.3f IKF=50m NE=1.3
+ BR=9.5 VAF=80 IKR=12m ISC=47p NC=2 VAR=10 RB=280 RE=1 RC=40
+ tr=0.3u tf=0.5n cje=12p vje=0.48 mje=0.5 cjc=6p vjc=0.7 mjc=0.33 kf=2f
** nodes:
** 1 emitter, 2 base, 3 collector
** 4 Vcc
** 5 Vin
** 6 Vout
q0 3 2 1 bc547a
vcc 4 0 12
vin 5 0 dc 0 ac 10m
rs 5 50 0
** rs is changed
c1 50 2 10u
re 1 0 1k
ce 1 0 100u
r2 2 0 2.2k
r1 2 4 10k
rc 4 3 1.2k
c2 3 6 10u
rl 6 0 100k
** rl is changed
.ac dec 10 10 0.01g
.control
run
let gain = vdb(6) - vdb(5)
meas ac peak MAX gain
let f3db = peak/sqrt(2)
meas ac fl WHEN gain=f3db RISE=1
meas ac fh WHEN gain=f3db FALL=1
plot gain
.endc
.end
```

When  $R_l$  is 12k, gain is 34.038 dB. When  $R_l$  is 1.2k, gain is 28.917 dB.

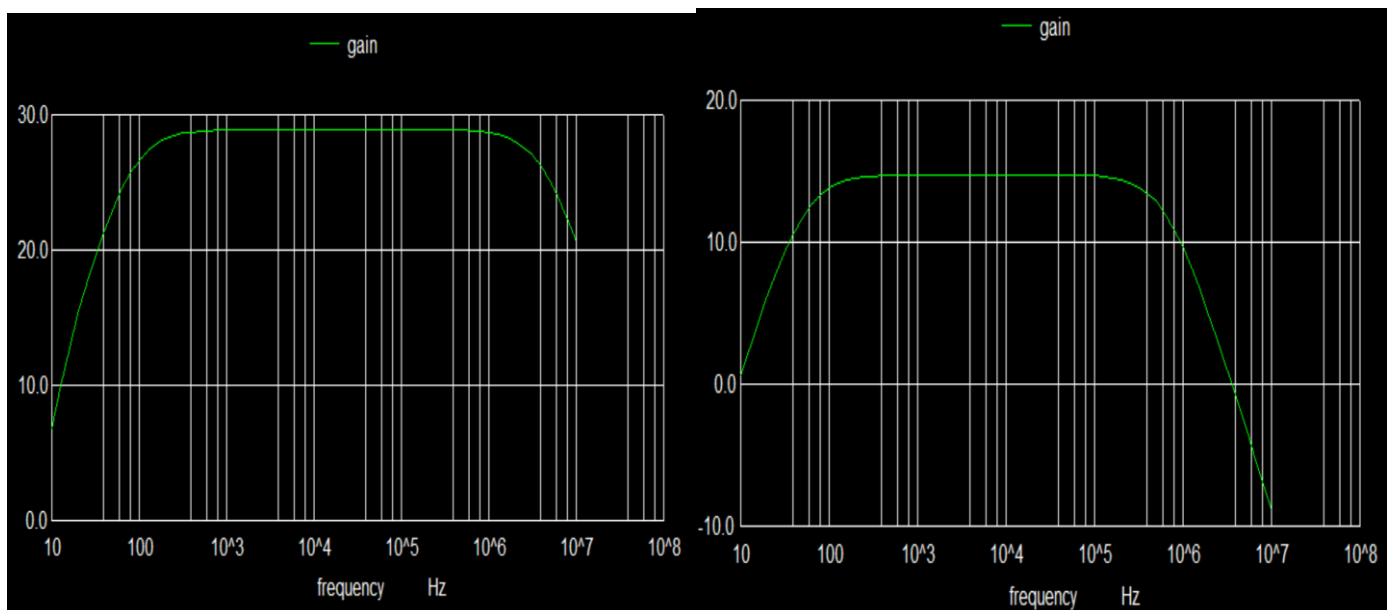When  $R_s$  is 2.2k, gain is 25.283 dB. When  $R_s$  is 10k, gain is 14.774 dB.



Learning:

Gain is directly proportional to  $R_c \parallel R_l$  and hence decreases with  $R_l$ .

As  $R_s$  increases, gain decreases.

Q4.

```
1 19D070052 Sheel Shah Expt3 CE Amp Biasing
2 .model bc547a NPN IS=10f BF=400 ISE=10.3f IKF=50m NE=1.3
3 + BR=9.5 VAF=80 IKR=12m ISC=47p NC=2 VAR=10 RB=280 RE=1 RC=40
4 + tr=0.3u tf=0.5n cje=12p vje=0.48 mje=0.5 cjc=6p vjc=0.7 mjc=0.33 kf=2f
5 ** nodes:
6 ** 1 Vin, 2 Rs-C1, 3 base1
7 ** 4 emitter1
8 ** 5 collector1, 6 base2
9 ** 7 emitter2, 8 Re2
10 ** 9 vcc/collector2
11 ** 10 vout
12 vin 1 0 dc 0 ac 10m
13 vcc 9 0 12
14
15 rs 1 2 0
16 c1 2 3 10u
17
18 q1 5 3 4 bc547a
19 r2 3 0 2.2k
20 r1 3 9 10k
21 re 4 0 1k
22 ce 4 0 100u
23 rc 5 9 1.2k
24
25 vib2 5 4 0
26 vie2 7 8 0
27
28 q2 9 6 7 bc547a
29 re2 8 0 10k
30 c2 7 10 10u
31 rl 10 0 10k
32
33 .op
34 .control
35 run
36 print i(vib2) i(vie2)
37 .endc
38 .end
39
```

```
i(vib2) = 5.550494e-06
i(vie2) = 9.566787e-04
```

Learnings:

The CC amp buffer helps increase  $R_{in}$ , as well as decrease  $R_{out}$ , making the overall amplifier much better.