

Q1. Inverting Amplifier

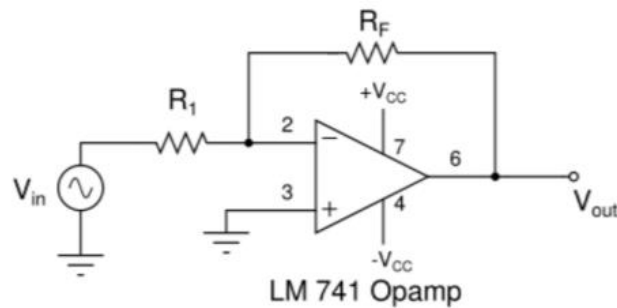


Fig.2 Inverting amplifier

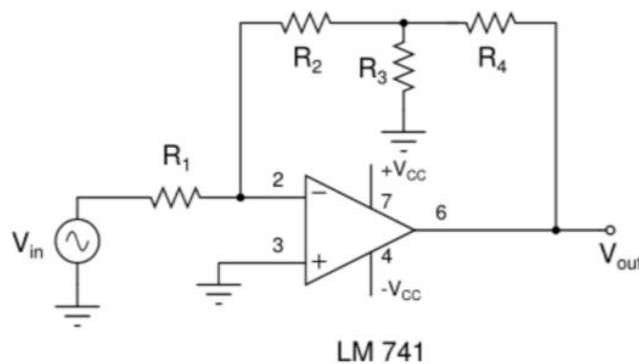


Fig.3 A special type of inverting amplifier

- Unique features of inverting amplifier:
 - The output is out of phase with the input and this helps improve stability and reduce oscillations.
 - The gain can theoretically be of any magnitude, and can be less than 1.
 - The output won't clip due to common mode offset.
- Limitations of inverting amplifier:
 - Input resistance is R_1 , which is a major drawback.
 - The input must be noiseless, as the noise as well as the dc component get amplified, and this might lead to clipping of the output.
- Applications of inverting amplifier:
 - A summer, where the gains are independent. A summer can be used in audio systems etc.
 - The small feedback resistance can decrease distortion.
- Advantages of the special amplifier:
 - R_2 need not be too large for large gains, as R_3 and R_4 help too.
 - We can use it as a current amplifier too, with a different gain.

Q2. Non-inverting Amplifier

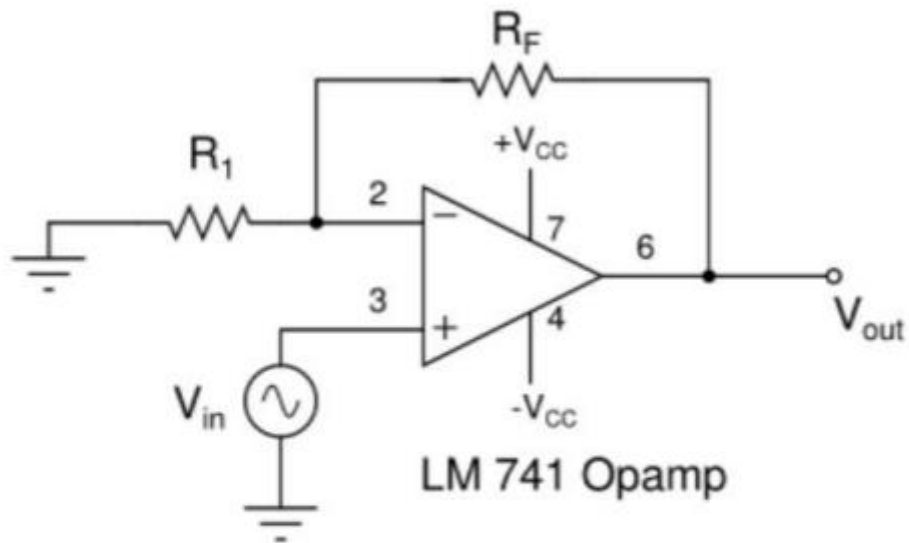


Fig.5 The non-inverting voltage amplifier

- Unique features of non-inverting amplifier:
 - The input resistance is very high, and the output resistance is very low.
 - The gain is always be positive and greater than 1.
- Limitations of non-inverting amplifier:
 - Input resistance and output resistance vary with the op-amp used.
 - Gain can't be less than 1.
- Applications of inverting amplifier:
 - Voltage follower, due to high R_{in} .
 - Isolating two circuits that the op-amp is connecting.

Q3. Differential Amplifier

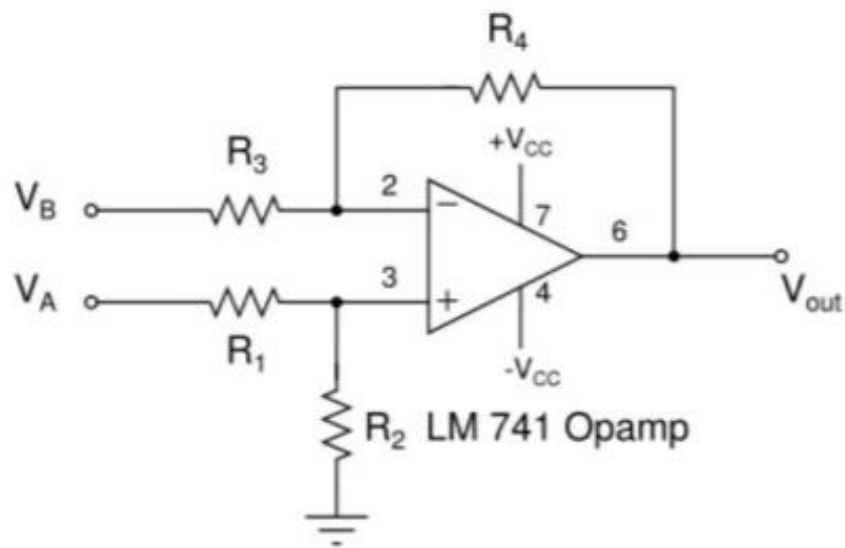


Fig. 6 Single-opamp difference amplifier

- Features of differential amplifier useful in applications:
 - If the resistances are matched, the common mode gain is very low (~ 0).
 - Signals with noise can be processed as common noise gets cancelled.
 - We can configure a linear amplifier very easily by passing the output in negative feedback to one of the inputs.
- Limitations of differential amplifier:
 - The size is large, due to more resistors and complexity
 - Input impedance is only moderately high.
 - If the resistors are not well matched, common mode amplification is seen.

Q4. Applications of Differential Amplifier

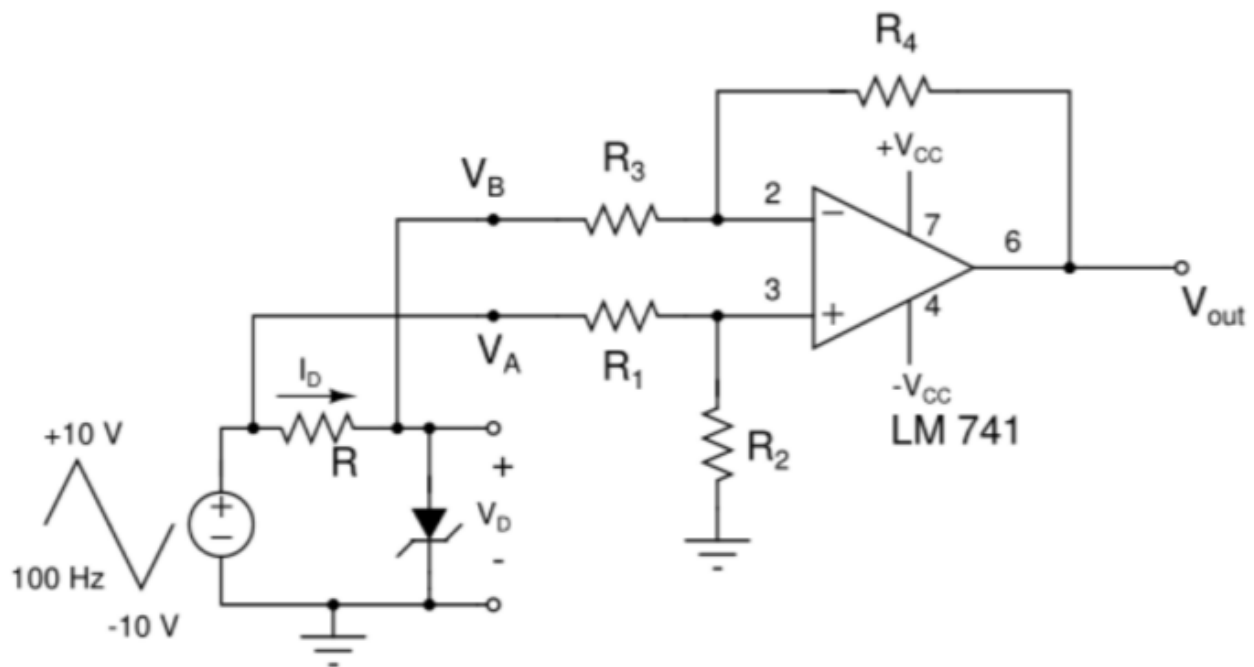


Fig. 8 Setup for measuring the i-v characteristic of the Zener diode

- Why is a triangular signal used:
 - We are plotting I vs V , and we want our x-axis(V) to be linear, and hence a triangular input is used.
 - If a sinusoid input is used, the IV characteristic will get distorted, and for a square input, we only see the I values for the extreme ends of the V values.
- Why is frequency low:
 - At high frequency, the op-amp might start to slew and not be exactly in sync with the I values.
- Difference in LEDs:
 - The semiconductor used is different, and the energy gap lies in the visible spectrum, unlike the Si/Ge diodes.
 - The different cutoff voltages for different colors is because of the difference in frequency of light of the different colors emitted (and hence different energy bands).

Learnings:

- I learned about the uses of different types of op-amp based amplifiers.
- I understood the pros and cons between the different types, and about what type of amp would be most suited for which application.
- I learned a ingenious technique for plotting the I-V characteristics of diodes.

