

# Expt 7 – Instrumentation Amplifiers

Sep 24, 2021 (Friday)  
EE 230 Analog Circuits Lab  
Joseph John  
2021-22/I

# Summary

## A) Introduction

- Single-Opamp Difference Amplifiers (problems)


## B) Three-Opamp Instrumentation Amplifiers

## C) TL 084 Quad Opamps based Instrumentation Amplifier

## D) INA 128 Instrumentation Amplifier


## E) Loadcell and its Interfacing – using Instrumentation Amplifiers

# Single-Opamp Difference Amplifier

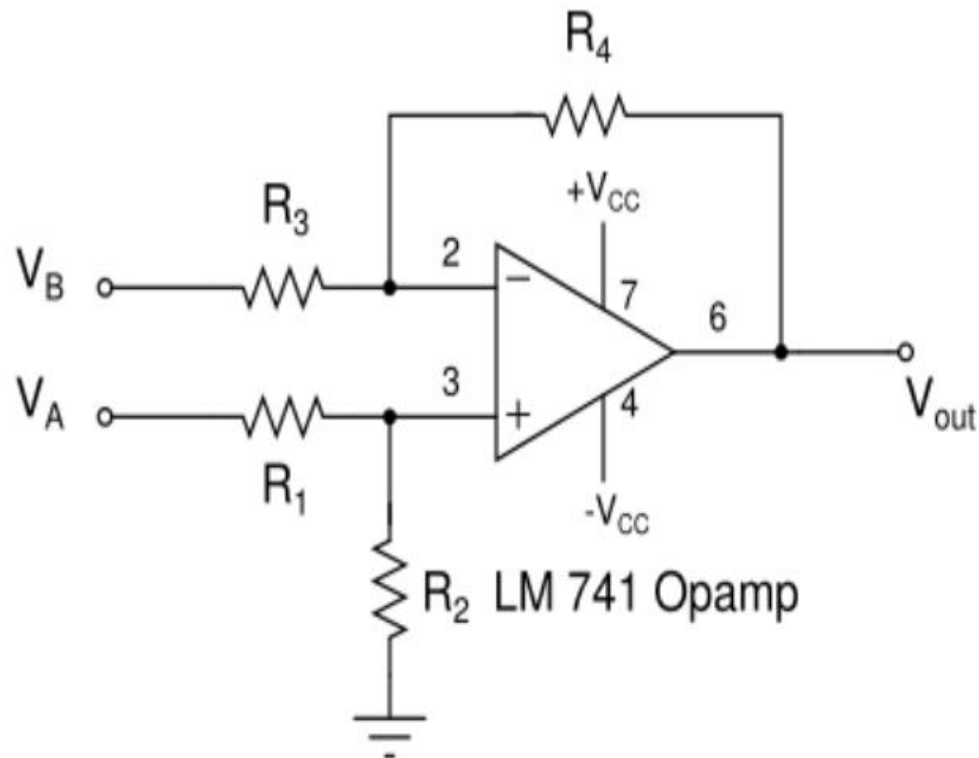

- Major Features
- Uses differential input signals
- Works as a difference amp if  $(R_4/R_3 = R_2/R_1)$
- $A_d = V_{out}/(V_A - V_B) = R_4/R_3$
- $A_{cm} = 0$  (ideally)
- $CMRR = A_d/A_{cm}$  (ideally  $\infty$ )

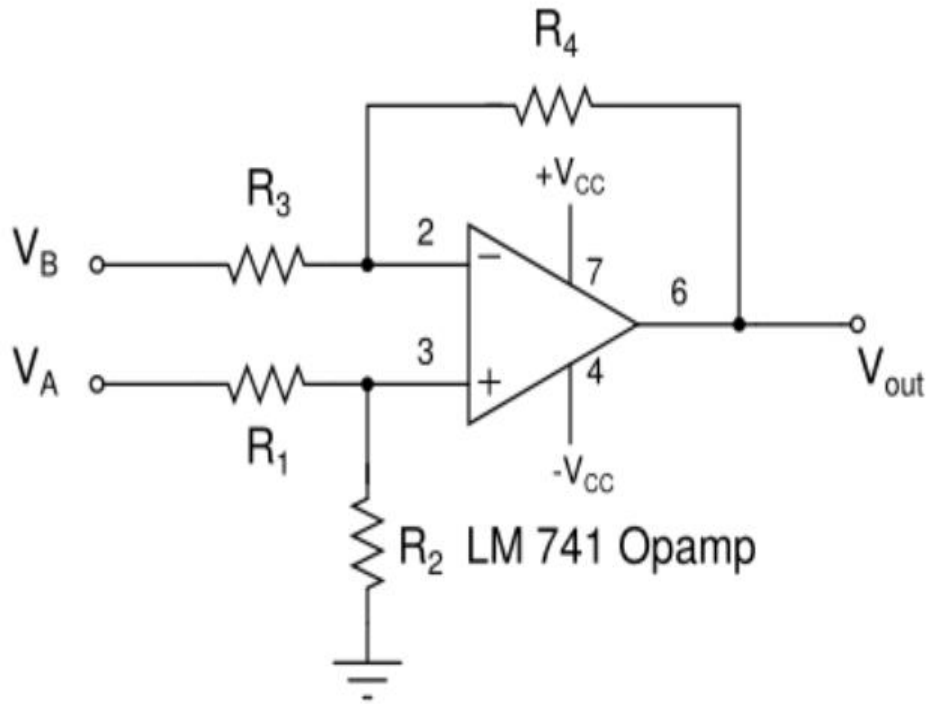
# Problems of Single-Opamp Difference Amplifiers



## Problems

- Difficult to change  $A_d$
- Limited  $A_d$
- Limited differential input resistance
- Limited CMRR (due to poor  $A_{cm}$ )
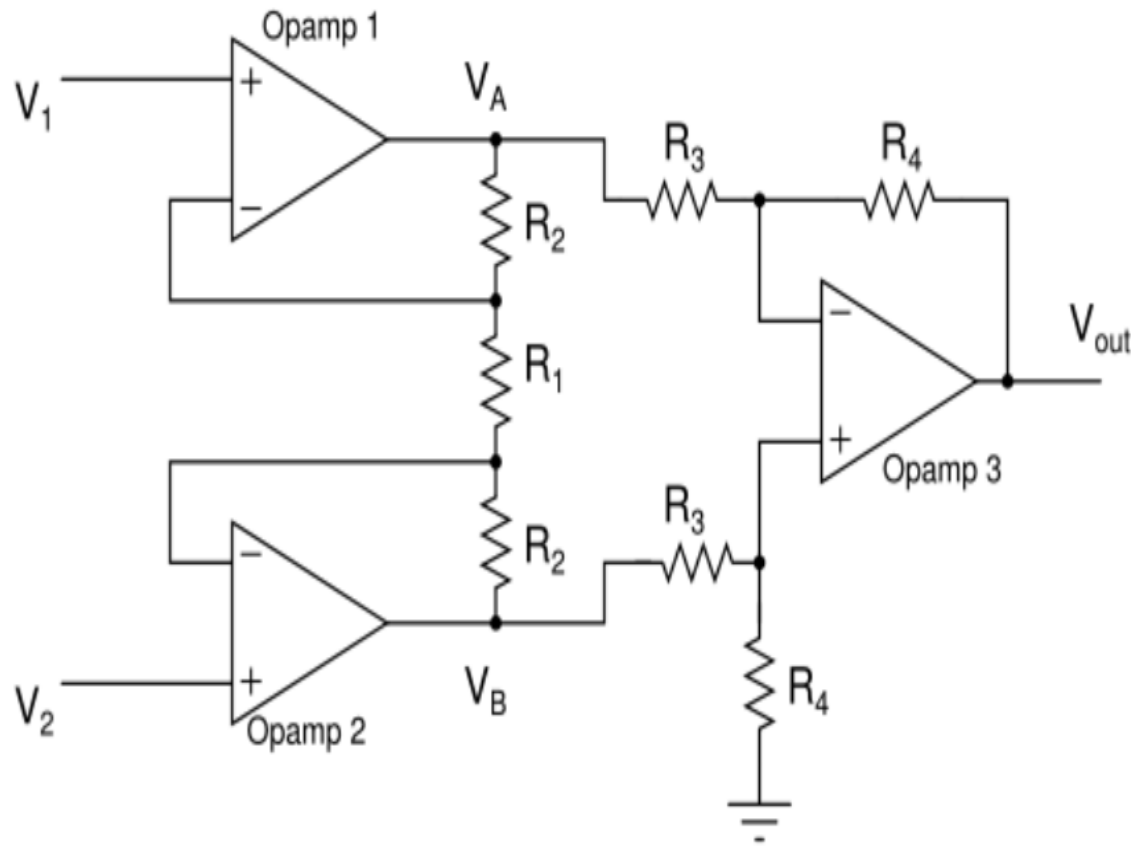
## B) Three-Opamp Instrumentation Amplifiers



### Major features


- Very high input resistance

- Easy to change  $A_d$

$$A_d = V_{out}/(V_2 - V_1)$$
$$= (R_4/R_3) [1 + (2R_2/R_1)]$$


- Possible to have high  $A_d$
- High CMRR
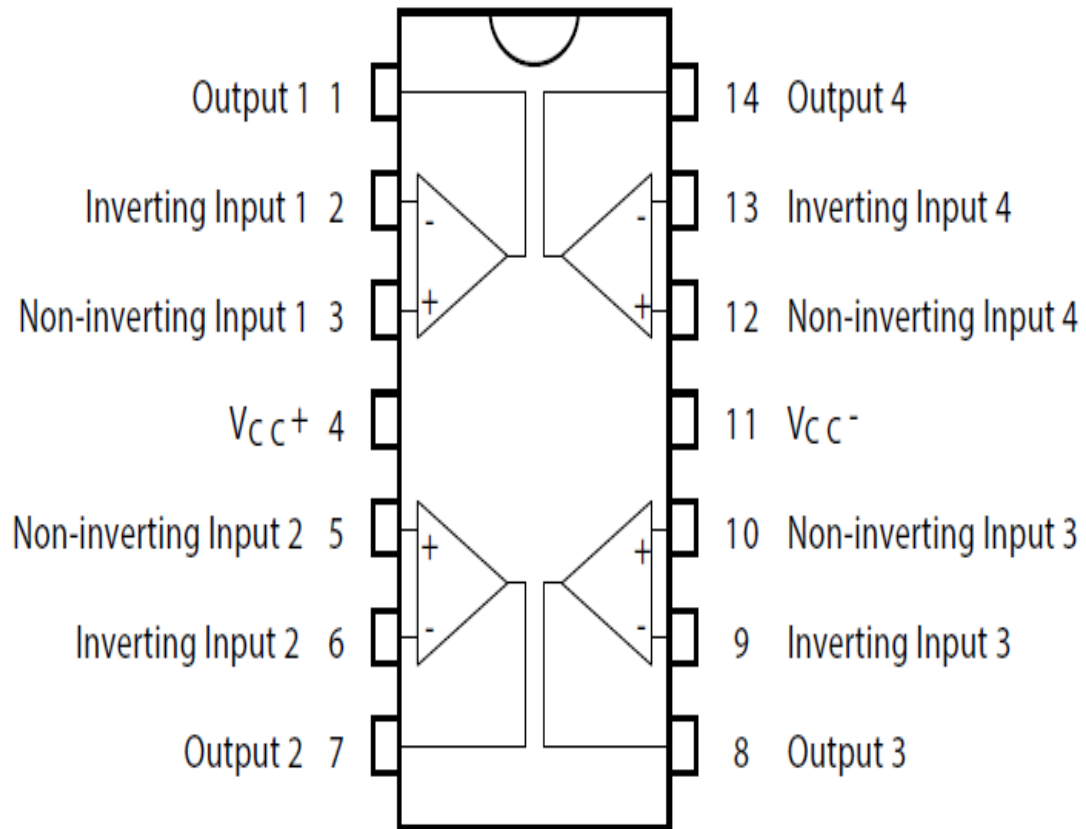
## C) TL 084 Quad Opamps based Instrumentation Amplifier


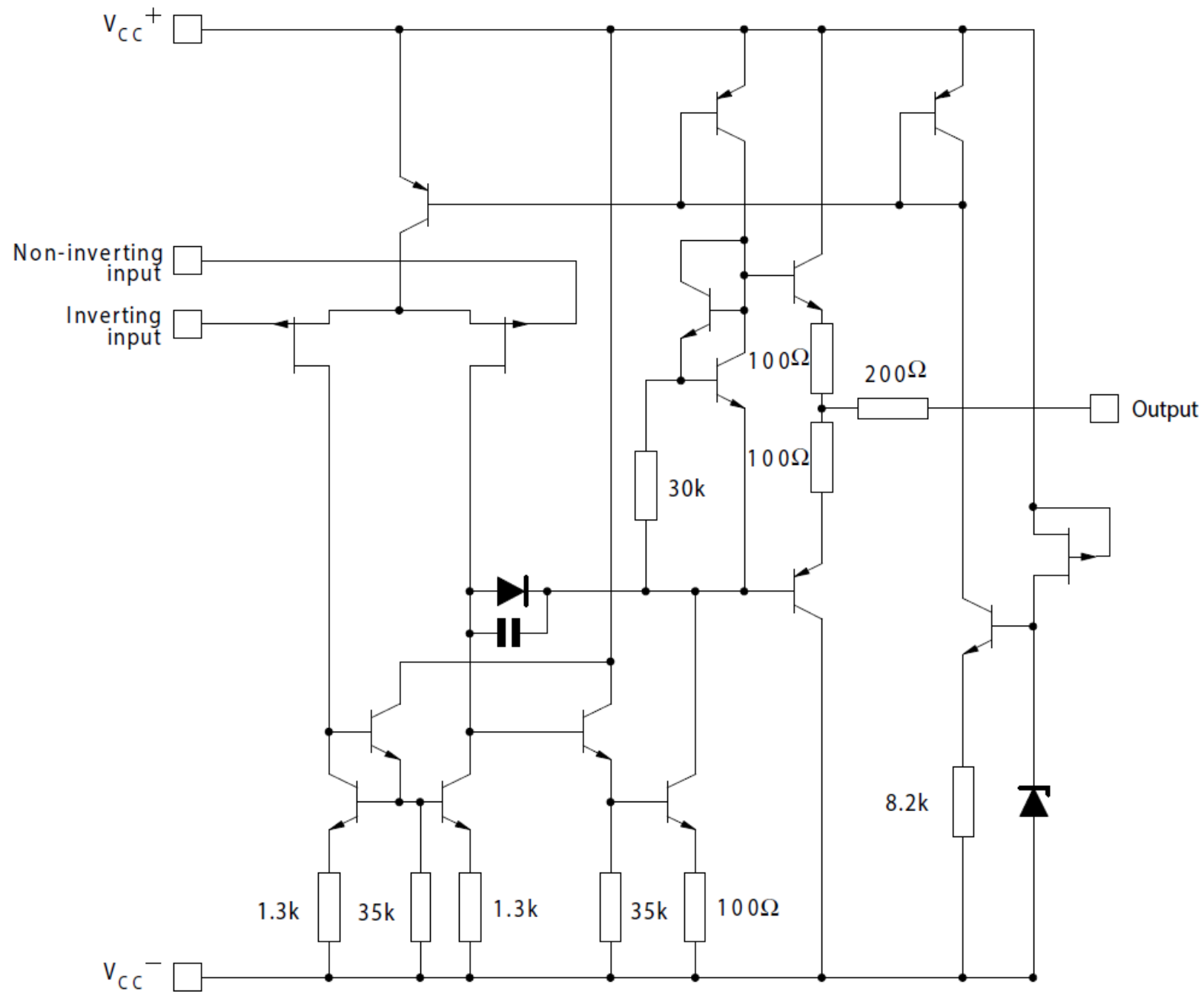
### TL 084 JFET Input Opamps


- Input offset voltage: 3 mV (typ)
- Input bias current: 20 pA
- CMRR: 86 dB
- Slew rate: 16 V/  $\mu$ s
- GB product: 4 MHz



## TL 084

- Circuit schematics (for each amplifier)
- Active loads
  - Used in all Opamps and other Linear ICs
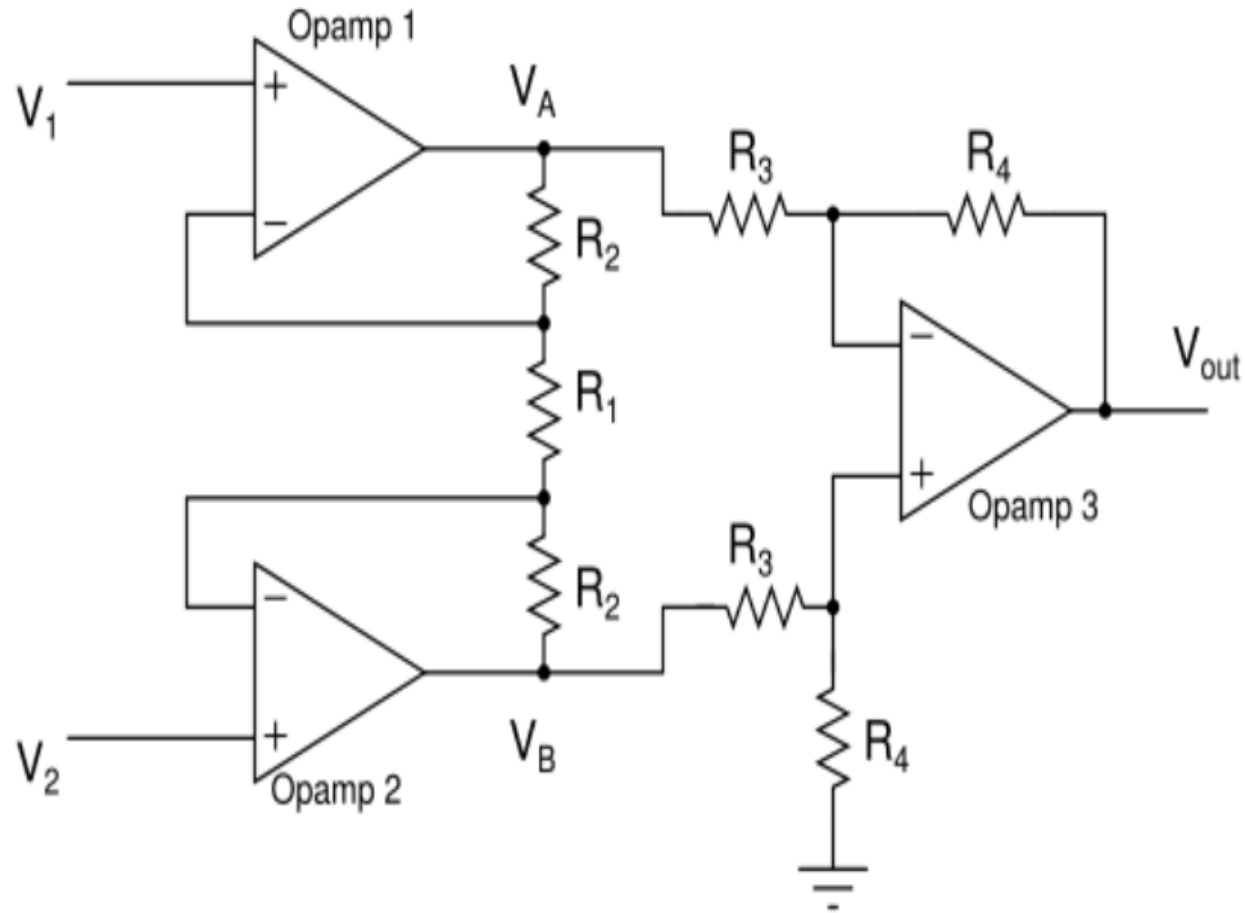
# Three-Opamp Instrumentation Amplifier using TL084




$+V_{cc} = 15\text{ V}$

$-V_{cc} = -15\text{ V}$


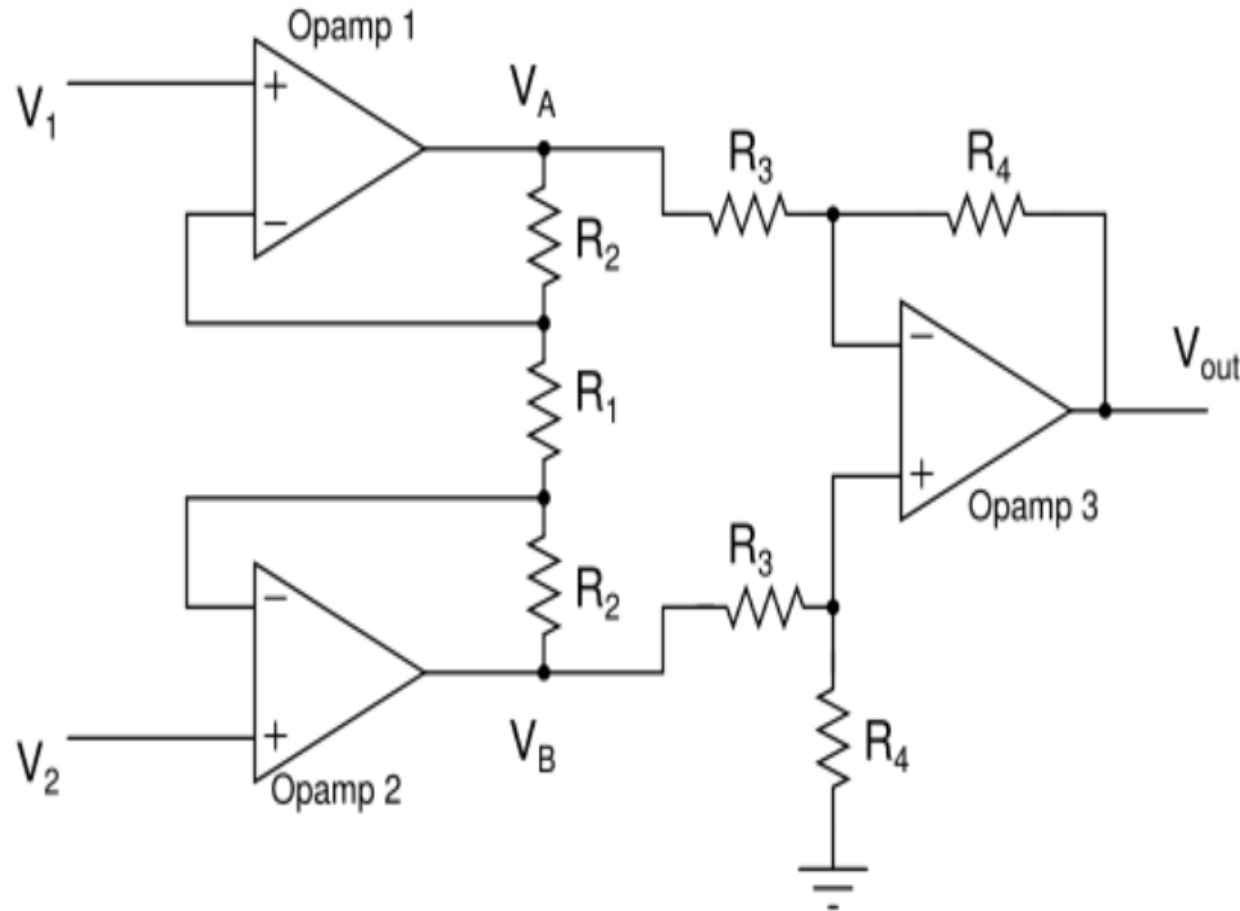
# Measurement of the Common-mode Voltage Gain, $A_{cm}$



$$V_1 = V_2 = 10 \sin \omega t \text{ V}$$

Circuit values:


$+V_{cc} = +15 \text{ V}$ ,  $-V_{cc} = -15 \text{ V}$ ,

$R_1 = R_2 = 10 \text{ k}\Omega$ ,

$R_3 = 1 \text{ k}\Omega$ , and

$R_4$  (connected to the inverting input of Opamp 3) =  $100 \text{ k}\Omega$  ;

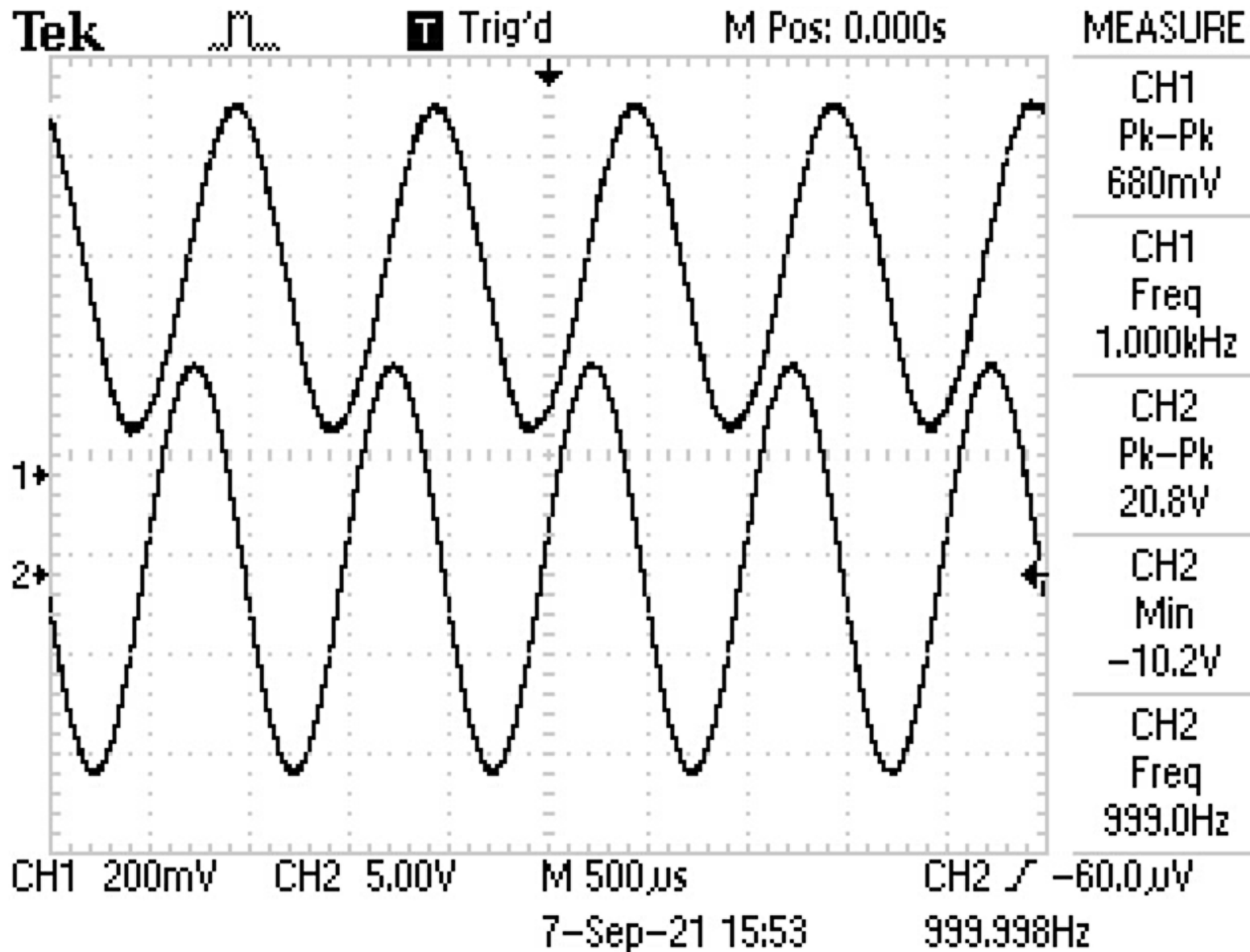$R_4$  (connected to the non-inverting input of Opamp 3) =  $91 \text{ k}\Omega + 10 \text{ k}\Omega$  (Pot).



$A_{cm}$  measurement


$$V_1 = V_2 = 10 \sin \omega t \text{ V}$$

(20 Vp-p)

$V_{out} : 680 \text{ mV}$

$A_{cm} = 0.034$   
(too high)
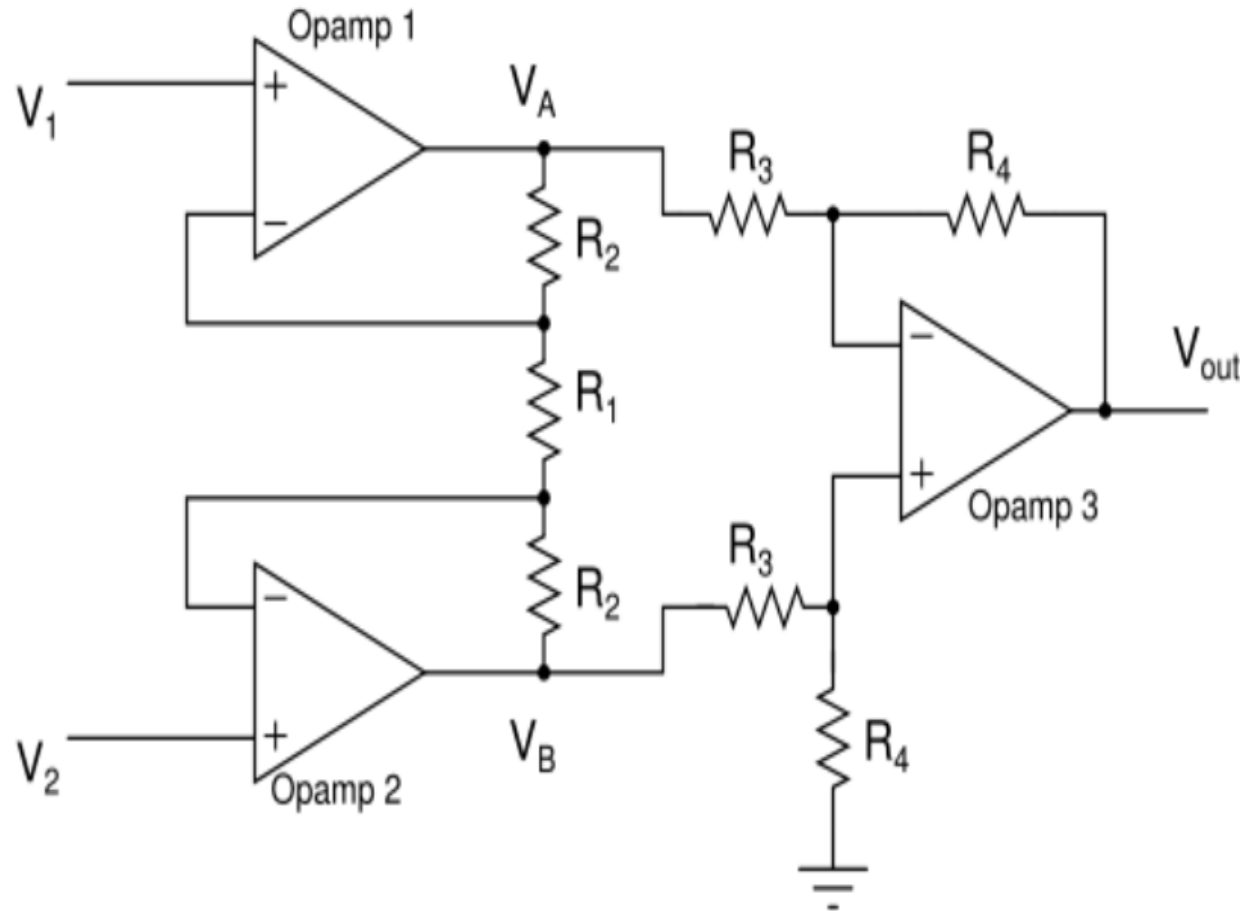
# Measurement of the Differential Voltage Gain, $A_d$



$$V_1 = 0, V_2 = 10 \sin \omega t \text{ mV}$$

Circuit values:


$+V_{cc} = +15 \text{ V}$ ,  $-V_{cc} = -15 \text{ V}$ ,

$R_1 = R_2 = 10 \text{ k}\Omega$ ,

$R_3 = 1 \text{ k}\Omega$ , and

$R_4$  (connected to the inverting input of Opamp 3) =  $100 \text{ k}\Omega$  ;

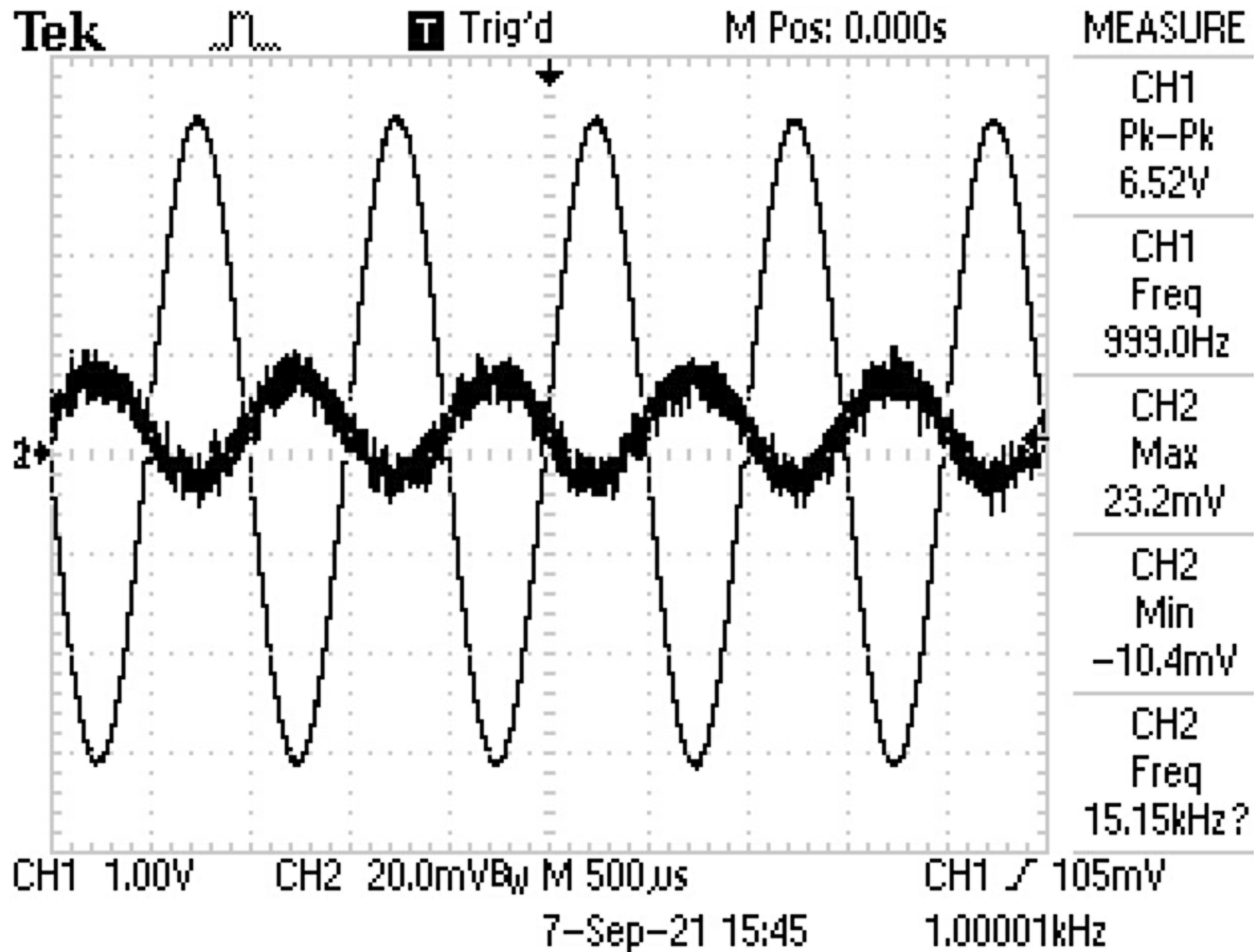$R_4$  (connected to the non-inverting input of Opamp 3) : adjusted for the lowest  $A_{cm}$



$A_d$  measurement

$$V_1 = 0$$

$$V_2 = 10 \sin \omega t \text{ mV}$$

(20 mV p-p)


$$V_{out} : 6.5 \text{ Vp-p}$$

$$A_d = 6.52 / 0.02$$


$$= 326$$

(As per design: 300)

## D) INA 128 Instrumentation Amplifier

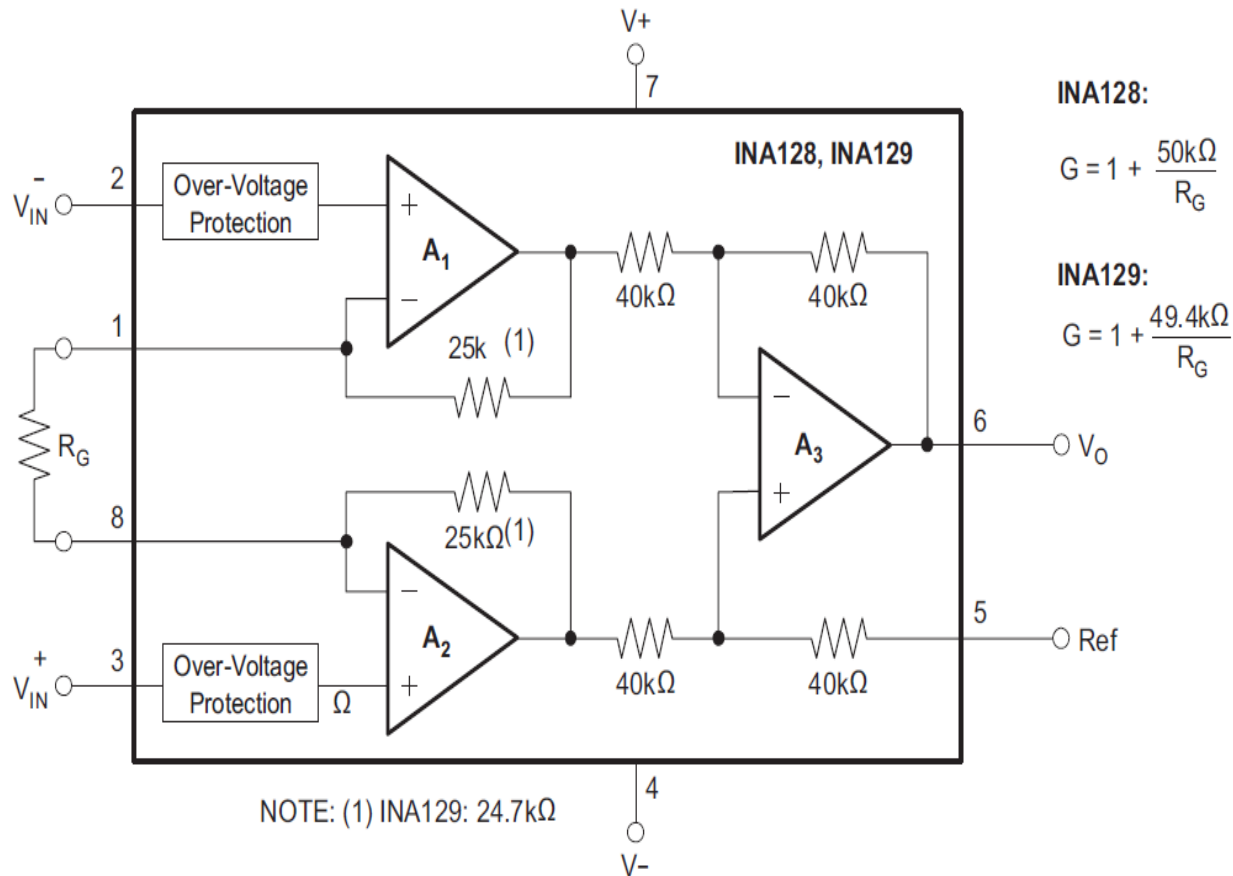

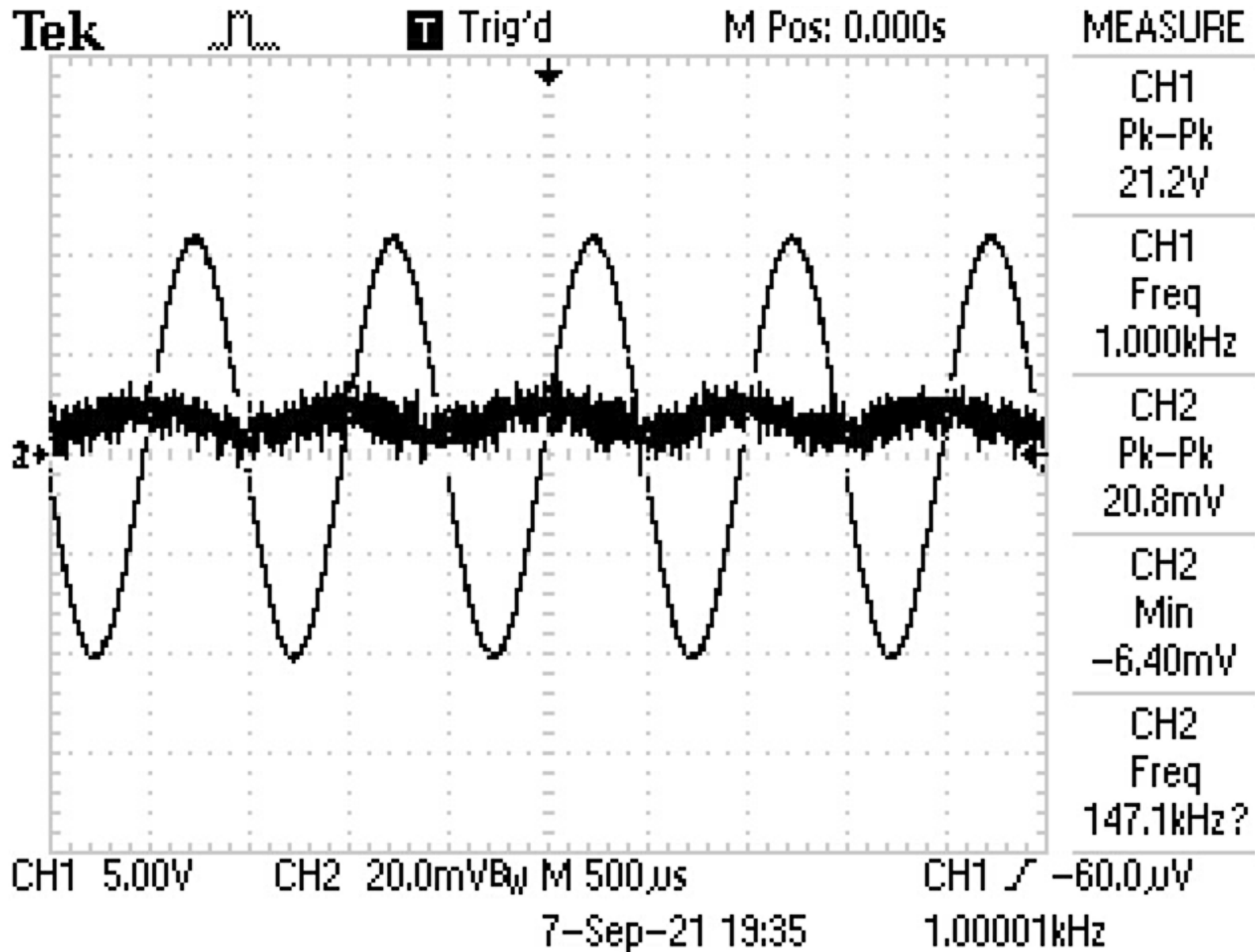- A popular INA
- Applications:
  - Bridge amplifier
  - Thermocouple amplifier
  - RTD sensor amplifier
  - Medical instrumentation
  - Data acquisition
- Low offset voltage: 50  $\mu$ V maximum
- Low drift: 0.5  $\mu$ V/ $^{\circ}$ C maximum
- Low Input Bias Current: 5 nA maximum
- High CMR: 120 dB minimum



$A_{cm}$  measurement


$$V_1 = V_2 = 10 \sin \omega t$$

(20 Vp-p)

$V_{out} : 10 \text{ mV}$

$$A_{cm} = 5 \times 10^{-4}$$

(very good)

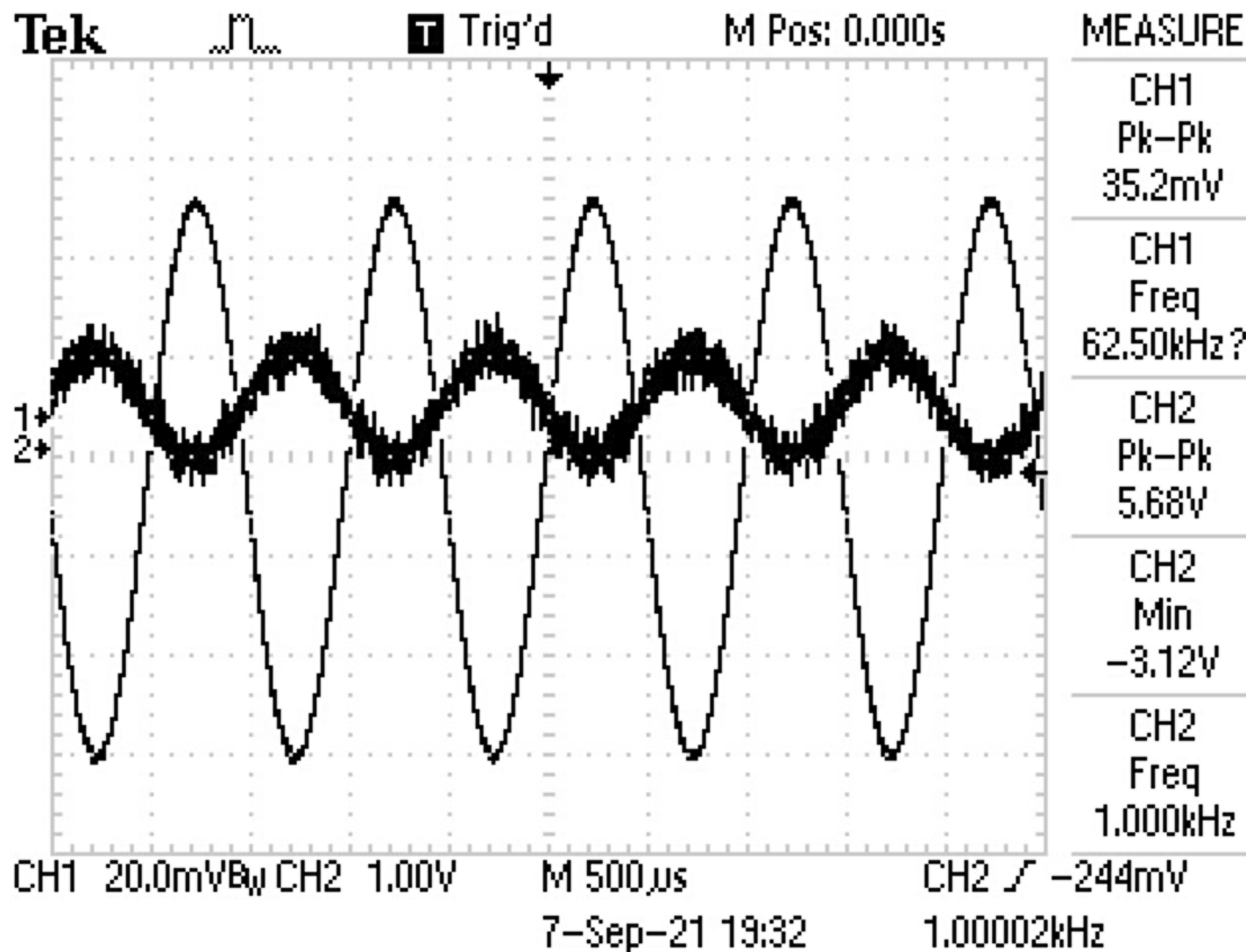

## $A_d$ measurement

$$V_1 = 0$$

$$V_2 = 10 \sin \omega t \text{ mV}$$

(20 mV p-p)

$$V_{out} : 5.68 \text{ Vp-p}$$

$$A_d = 5.68 / 0.02$$

$$= 284$$

(As per design:

$$[1 + (50k / 0.18)] = 279]$$


Measured CMRR:

$$(284 / 5 \times 10^{-4}) = 568,000$$

or 115 dB
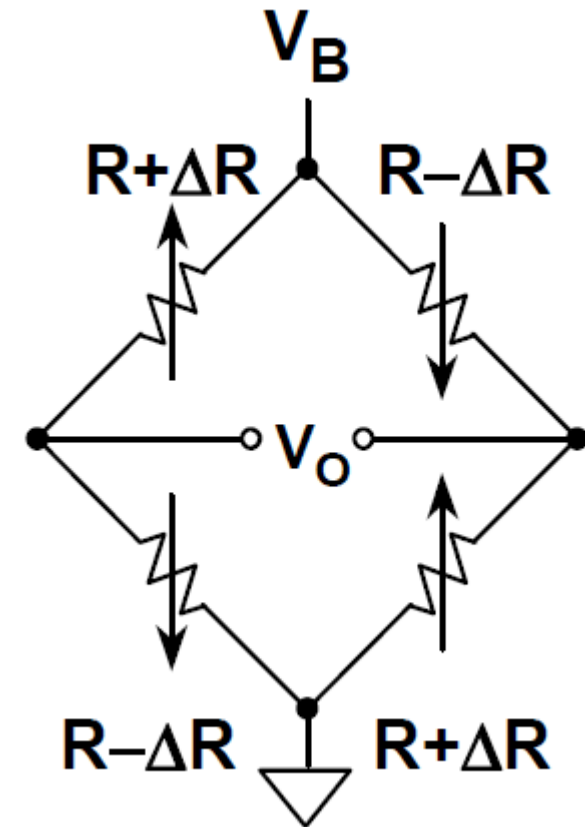
## E) Loadcell and its Interfacing – using Instrumentation Amplifiers

- **Load Cell**
- A commonly used sensor for measuring weight/pressure.
- Uses a full-bridge strain gage network (i.e. a Wheatstone bridge made of four strain gages)



Source: Sec 4-2, Sensor Signal Conditioning  
– Bridge Circuits, Walt Kester





# Output voltage sensitivity and linearity of constant voltage drive bridge configurations

$V_O: \frac{V_B}{4} \left[ \frac{\Delta R}{R + \frac{\Delta R}{2}} \right]$	$\frac{V_B}{2} \left[ \frac{\Delta R}{R + \frac{\Delta R}{2}} \right]$	$\frac{V_B}{2} \left[ \frac{\Delta R}{R} \right]$	$V_B \left[ \frac{\Delta R}{R} \right]$
Linearity Error: 0.5%/‰	Linearity Error: 0.5%/‰	Linearity Error: 0	Linearity Error: 0
(A) Single-Element Varying	(B) Two-Element Varying (1)	(C) Two-Element Varying (2)	(D) All-Element Varying



Source: Sec 4-2, Sensor Signal Conditioning – Bridge Circuits, Walt Kester

# Strain Gages

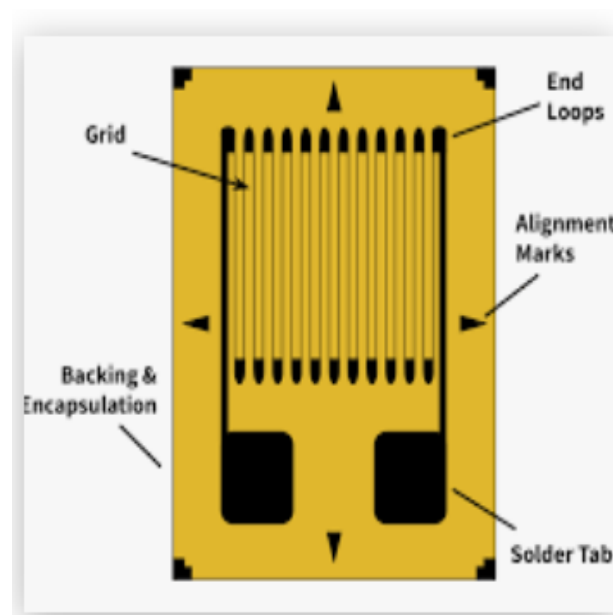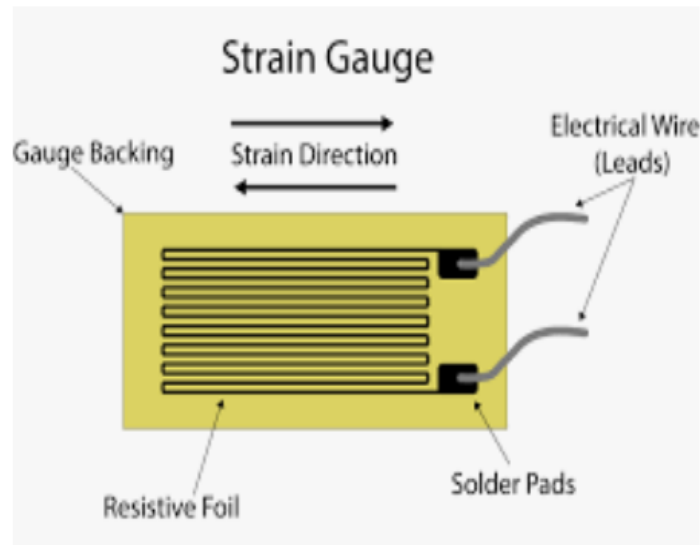


- Strain Gages
  - 120  $\Omega$ , 350  $\Omega$ , 3500  $\Omega$
- Weigh-Scale Load Cells: 350 to 3500  $\Omega$

Strain gages (Source: Internet)

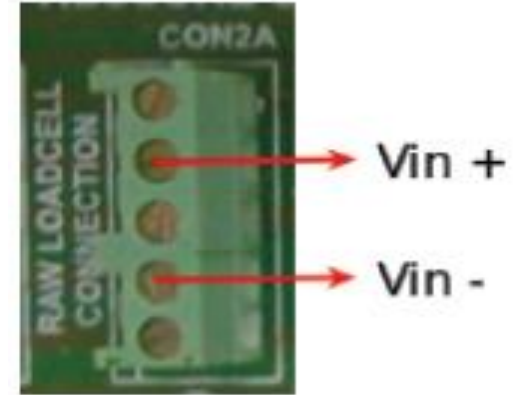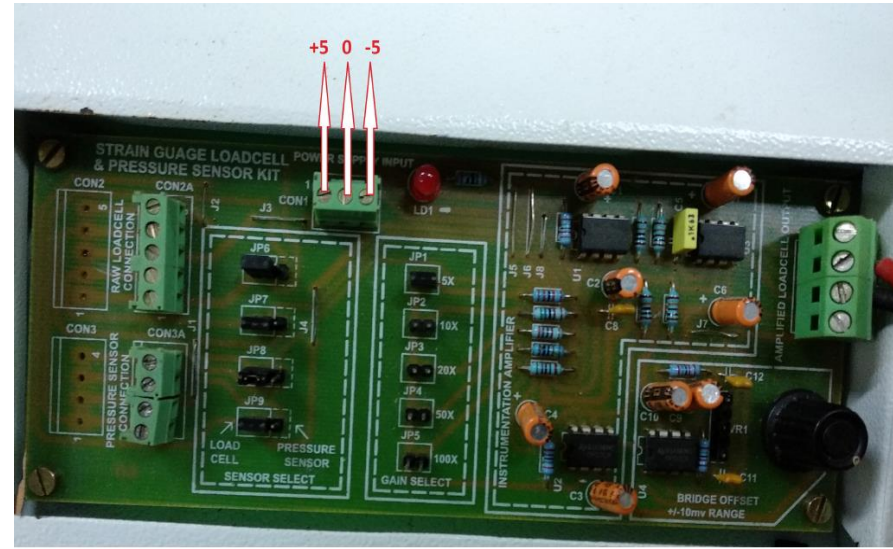

Loadcell for Weight Measurement

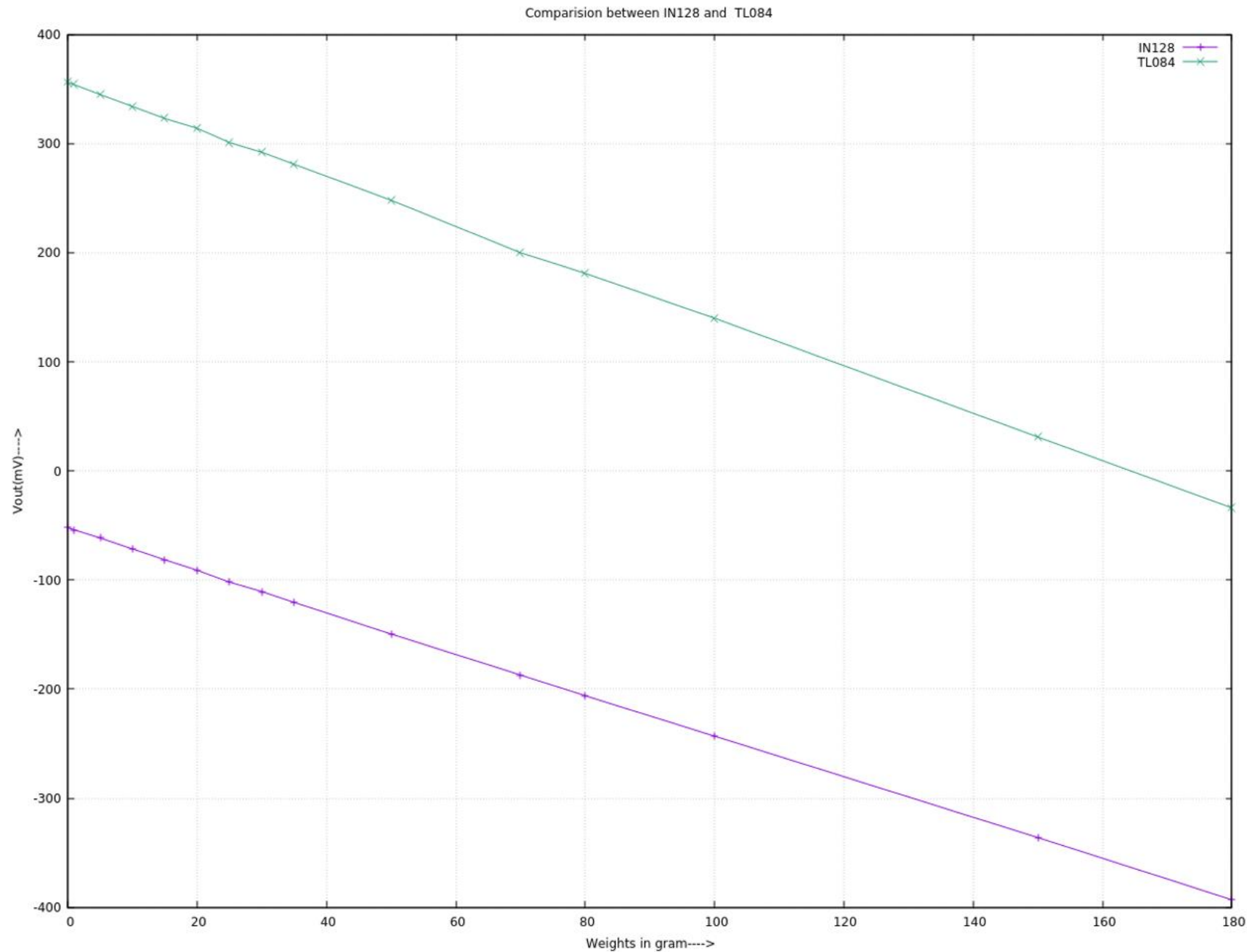

- Output of Loadcell interface circuit:
- Comparison - INA128 vs TL084 based Instrumentation Amplifier