


Expt 10 – Opamp based Sinusoidal RC Oscillators and Astable Multivibrators

Oct 22, 2021 (Friday)
EE 230 Analog Circuits Lab
Joseph John
2021-22/I

Summary


- Introduction to Oscillators and Multivibrators
- Wien-bridge Oscillator
- Phase-shift Oscillator
- Astable Multivibrator

Introduction

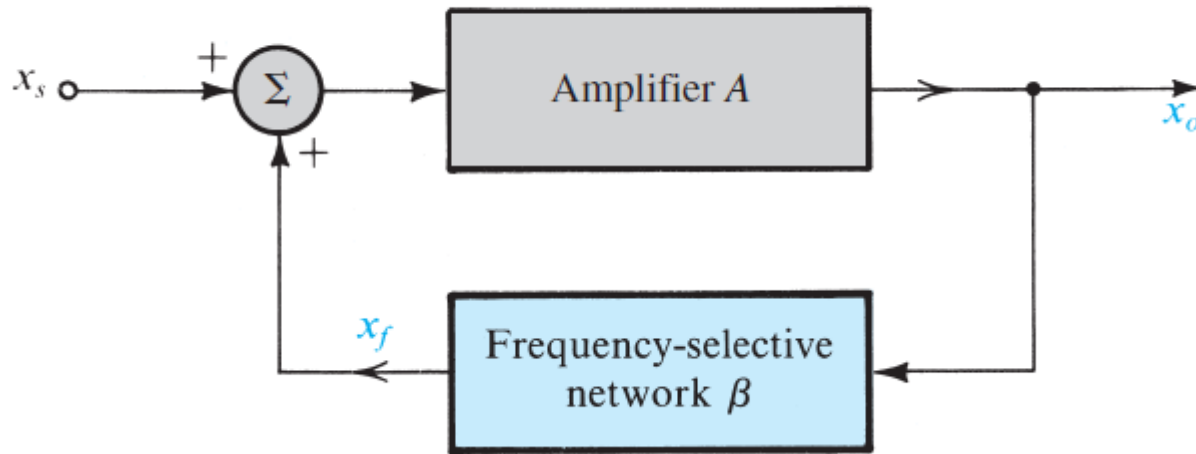


- Loop-gain = $A \beta$
- $L(j\omega_0) \equiv A(j\omega_0) \beta(j\omega_0) = 1$
 - At ω_0 the phase of the loop gain should be zero, and
 - the magnitude of the loop gain *should be unity*.
- **Barkhausen criterion.**

Wien-bridge Oscillator

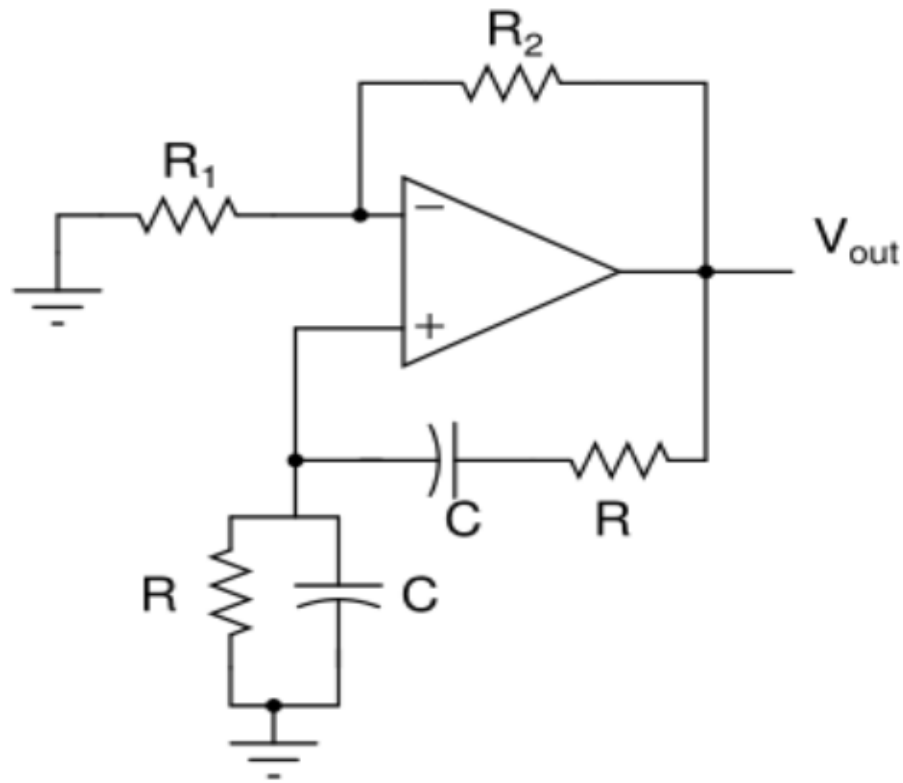




- Opamp: UA741
- Circuit values: $+V_{cc} = +12\text{ V}$, $-V_{cc} = -12\text{ V}$;
- $R_2 = 10\text{ k}\Omega$, $R_1 = 4.7\text{ k}\Omega$,
- $R = 4.7\text{ k}\Omega$, $C = 0.1\text{ }\mu\text{F}$
- Two parts:
 - a non-inverting amplifier with (resistors R_2 and R_1 for gain), and
 - a bandpass filter circuit made up of the RC Wien network.
 - At $\omega_0 = 1/RC$, BPF amplitude of the transfer function = $(1/3)$ with zero phase angle.
 - Circuit will work as an oscillator, if the voltage gain $\geq 3\text{ V/V}$.
 - For sustained oscillations, R_2/R_1 should be slightly > 2 .

tran22: wien-bridge oscillator - expt 10

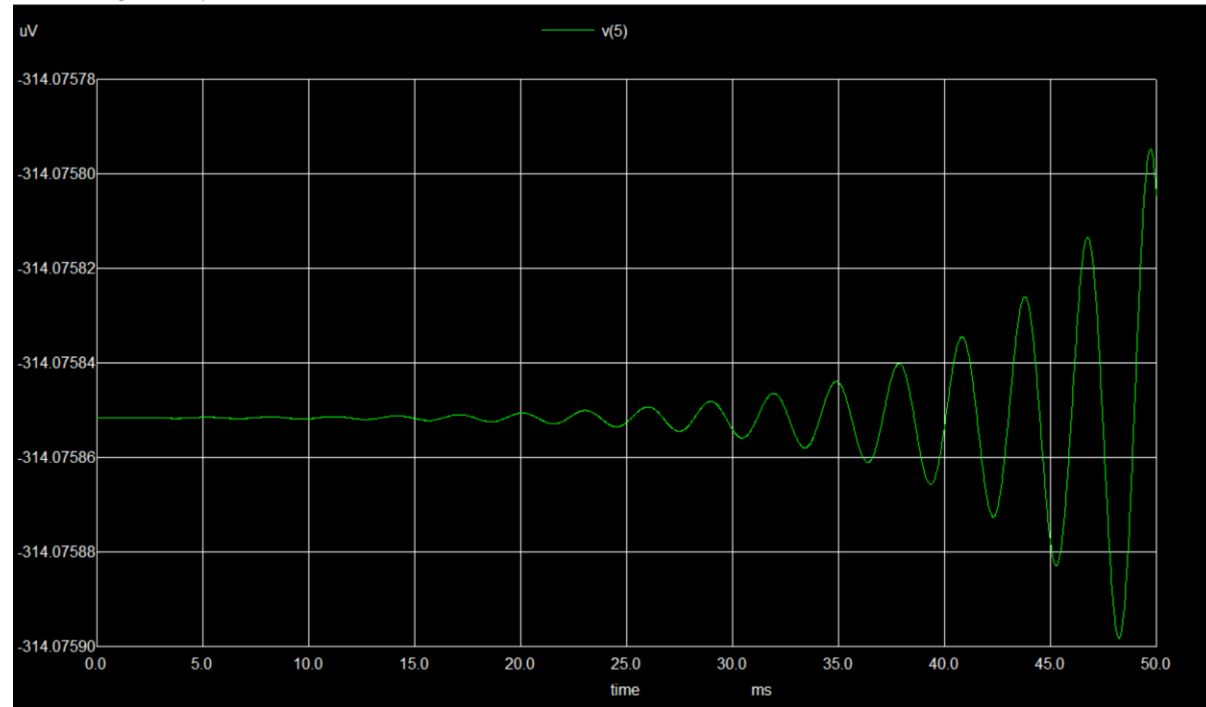

tran24: wien-bridge oscillator - expt 10

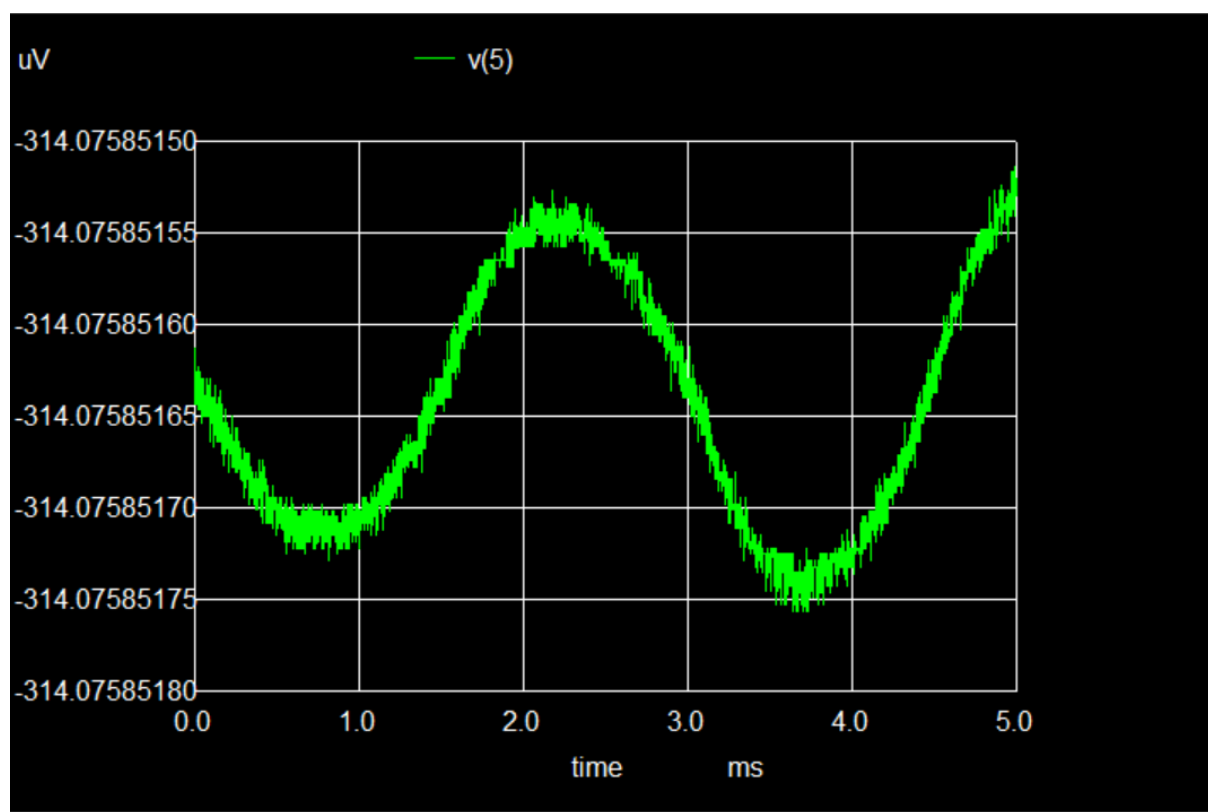


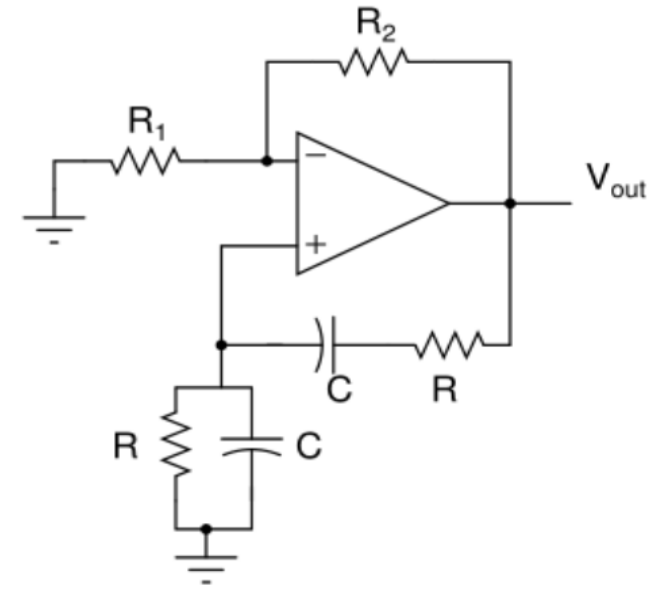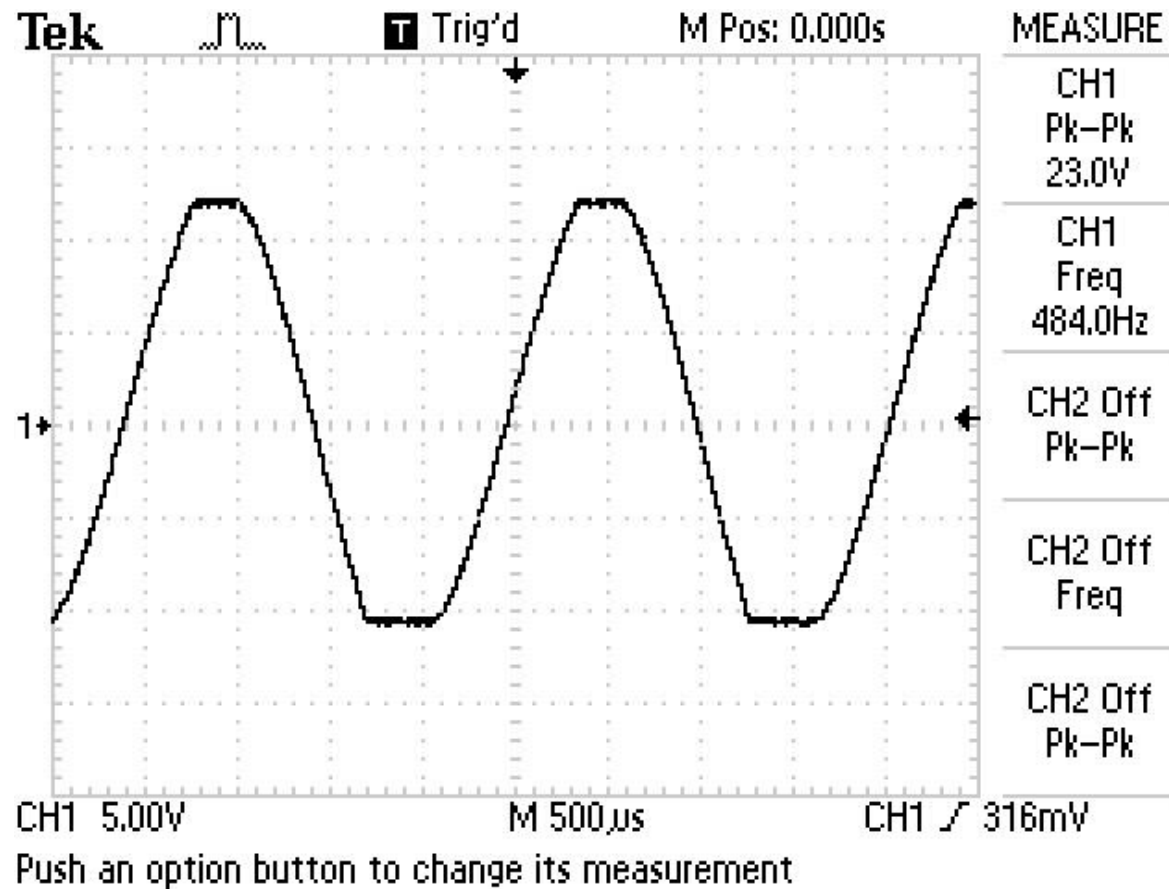

- $R_2 = 10 \text{ k}\Omega$, $R_1 = 4.7 \text{ k}\Omega$
- If $R_2 \gg 2 R_1$, V_{out} would saturate (distorted sinewave)

No scheme for amplitude stabilization

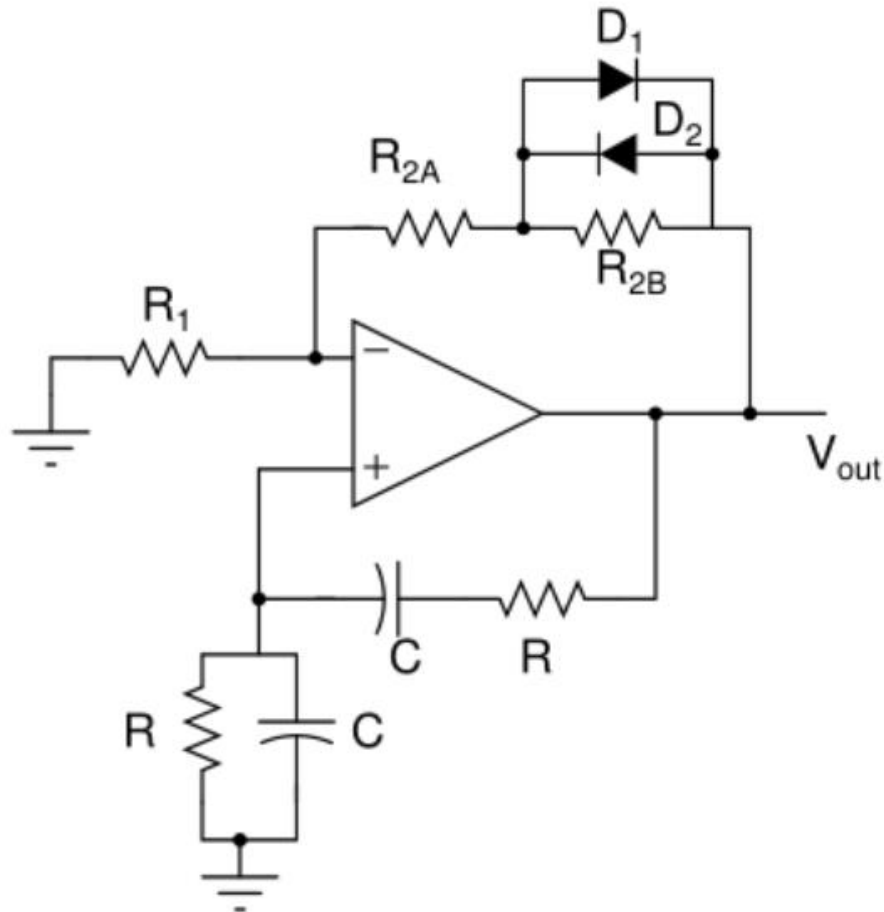Wien-bridge Oscillator with Amplitude Stabilization




- Purpose
- Keep voltage gain close to 3 V/V
- Control V_{out} amplitude through non-linear means, $R_2 = R_{2A} + R_{2B}$
- Choice of R_{2B} would decide the overall V_{out} amplitude

THE WIEN-BRIDGE OSCILLATOR:


The Wien bridge consisting of four resistors and two capacitors was invented in 1891 by Max Wien, a Prussian physicist, for inductance measurement. Much later, William Hewlett (cofounder in 1939 of Hewlett-Packard), while working toward his master's degree at Stanford University, realized the importance of placing part of the Wien bridge in a positive-feedback loop to form what was called the Wien-bridge oscillator. The first product in 1939 of the new Hewlett-Packard Company was the HP200A, a flexible, precision sine-wave generator using vacuum tubes to implement the amplifier and a tungsten lamp to control the loop gain and thus the amplitude of the sine wave.

Source: Sedra & Smith, 7ed., Chap 18

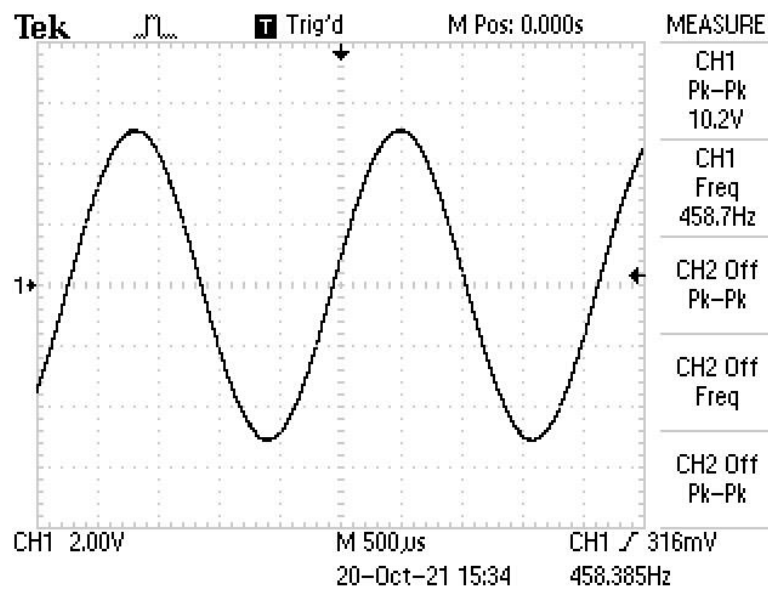



Good sinewaves

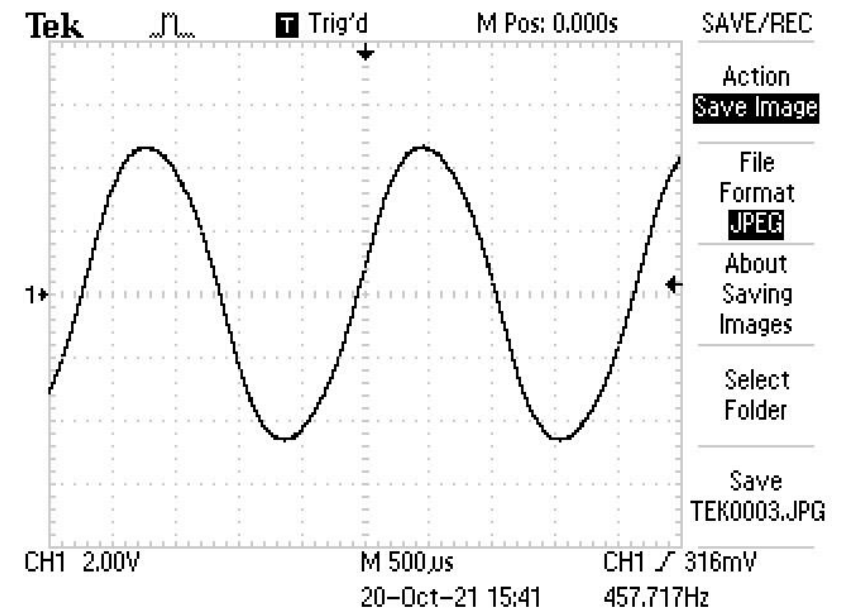($R_{FA} = 6.8 \text{ k}\Omega$, $R_{FB} = 10\text{k pot}$ – adjusted just sufficient to oscillate)




Slightly distorted sinewave

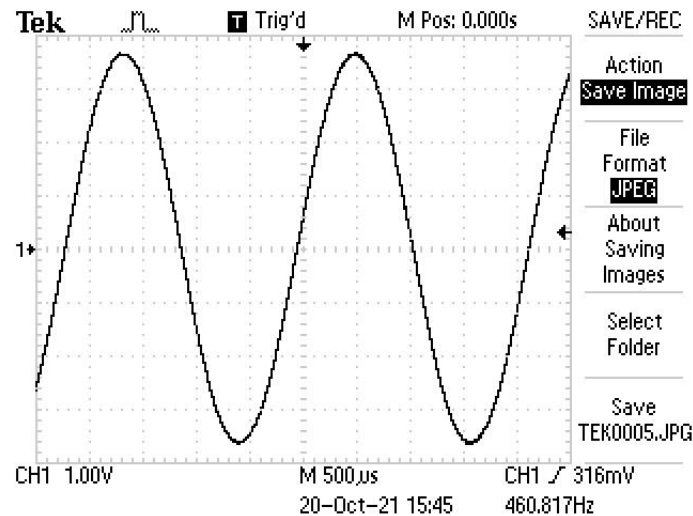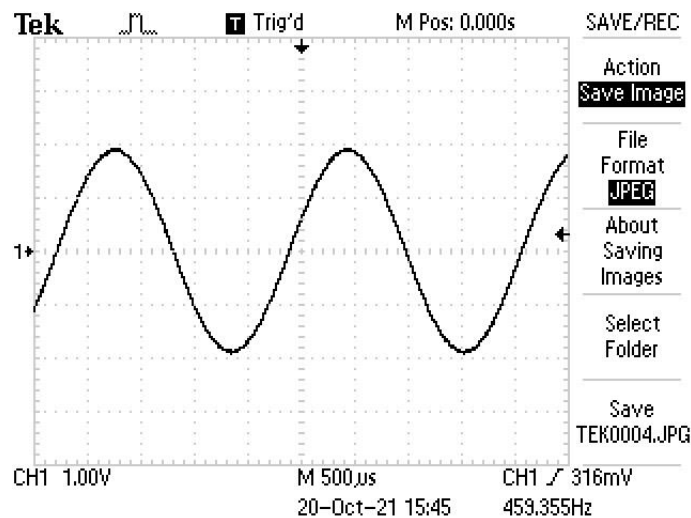($R_{FA} = 6.8 \text{ k}\Omega$, $R_{FB} = 3.3 \text{ k}\Omega$)




Phase-shift Oscillator

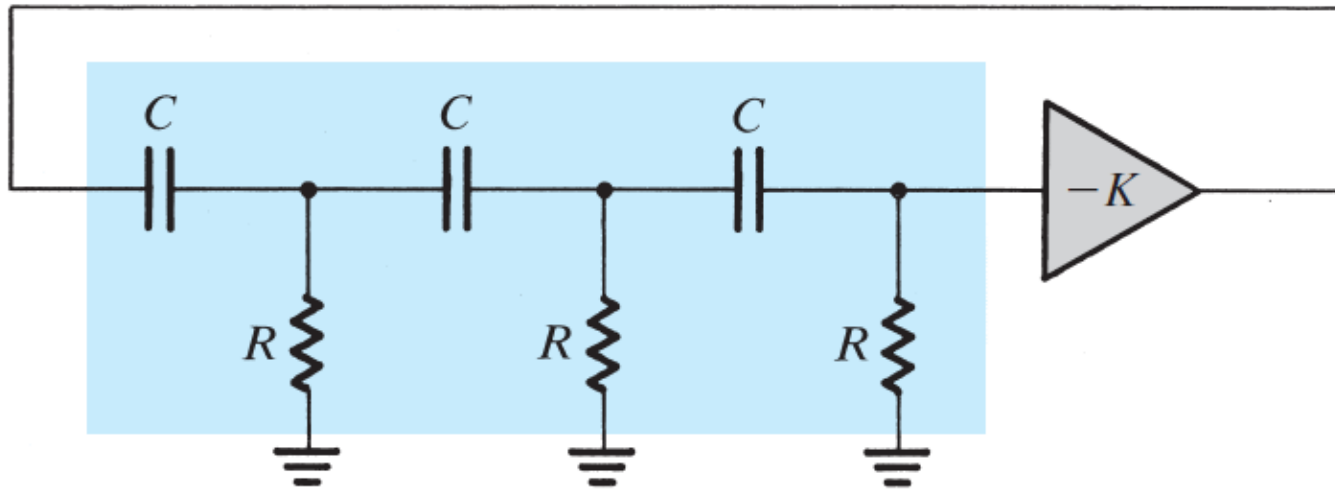- Two parts
 - A negative-gain amplifier ($-K$), and
 - A three-section (third-order) RC ladder network in the feedback.
- Will oscillate at the frequency for which the phase shift of the RC network is 180°
- Each section of RC introduces 60°




Source: Sedra & Smith, 7ed., Chap 18

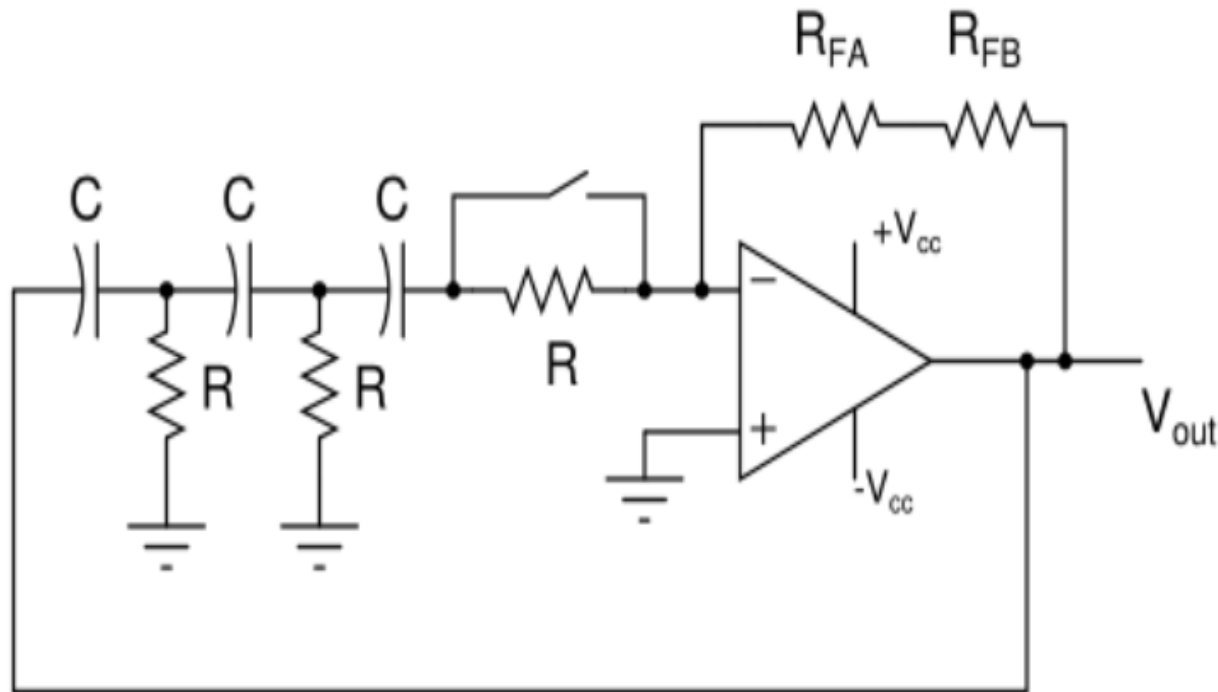Phase-shift Oscillator Implementation – Suggested Options





- Difficult circuit to work with
- Not as straightforward as the Wien-bridge oscillator
- Frequency of oscillation, $\omega \neq 1/RC$

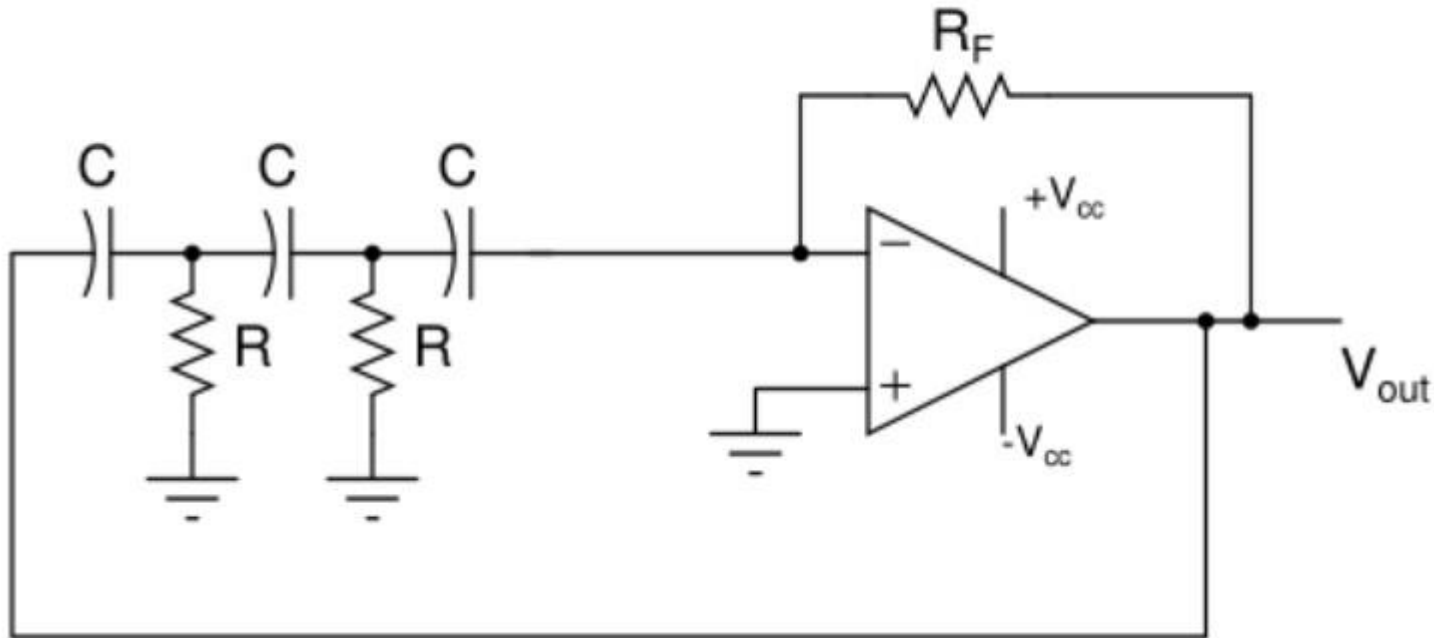Phase-shift Oscillator circuit used (in Expt)




Circuit values:

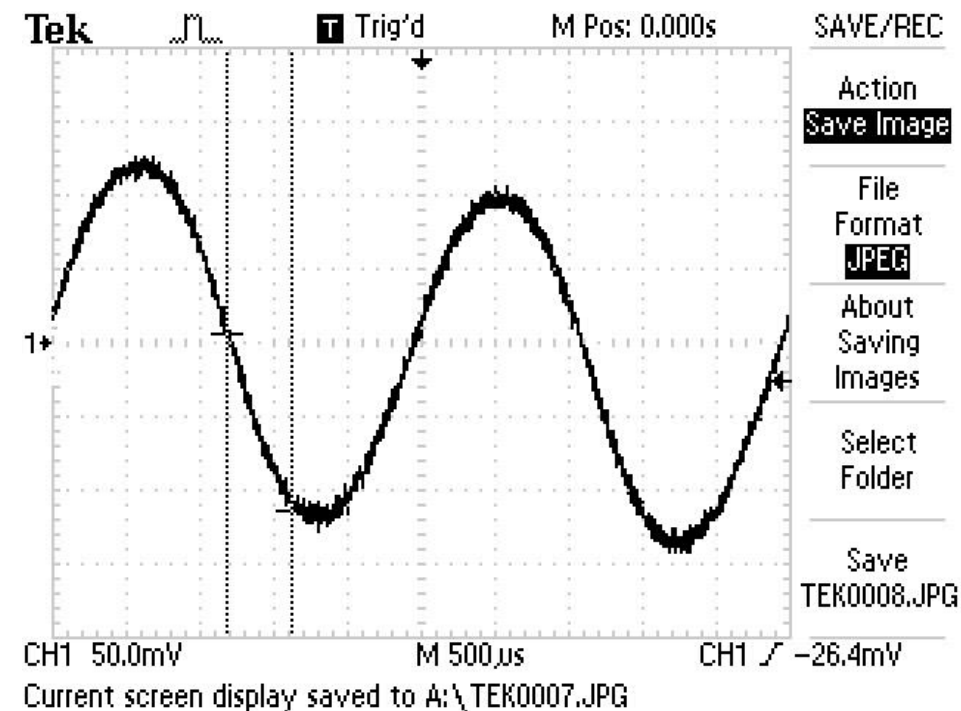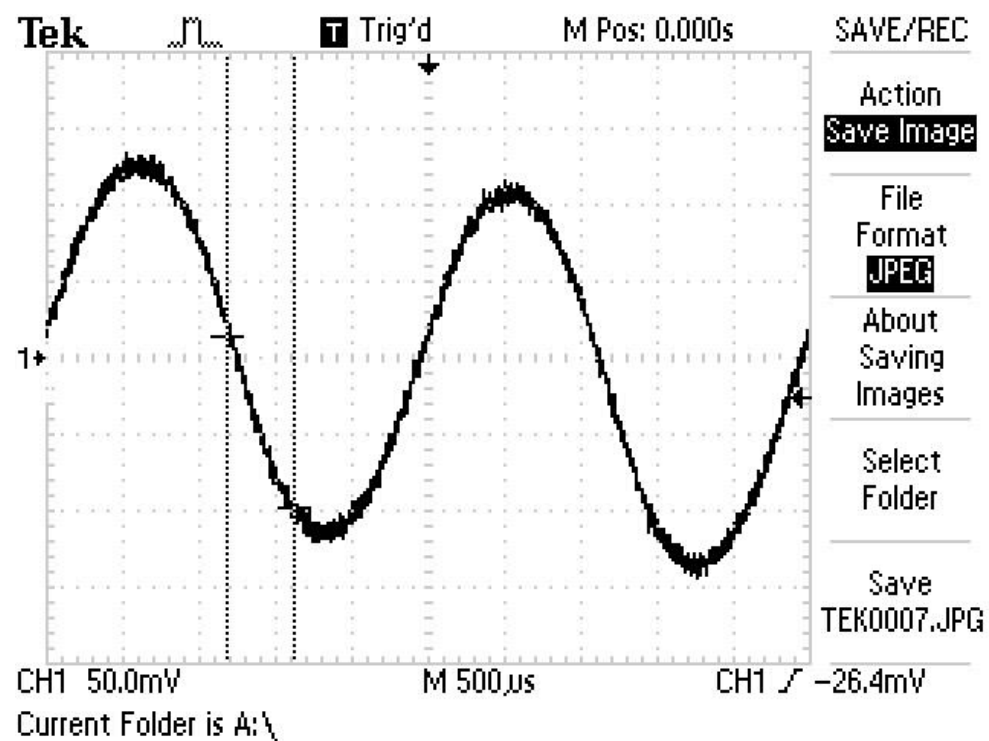- $R = 10 \text{ k}\Omega$, $C = 22 \text{ nF}$
- $R_F : 120 \text{ k}\Omega + 100\text{k pot}$
- No amplitude stabilization scheme





Low amplitude : 250 mv p-p



Astable Multivibrator

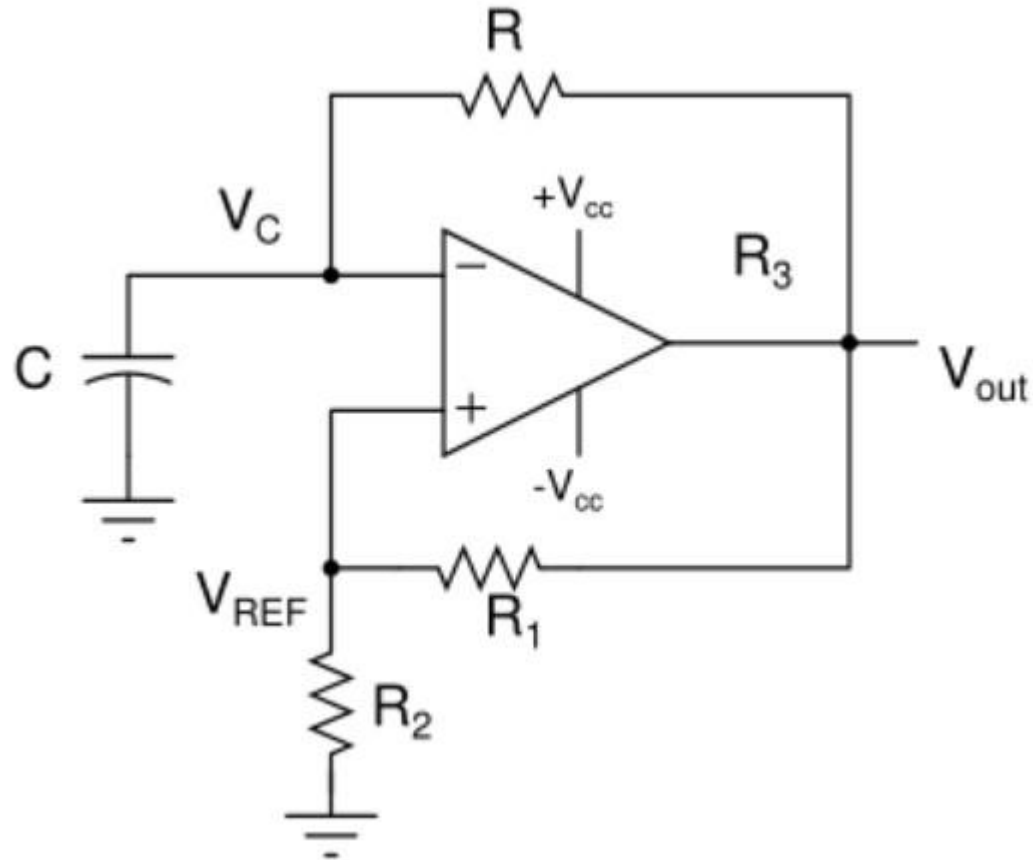

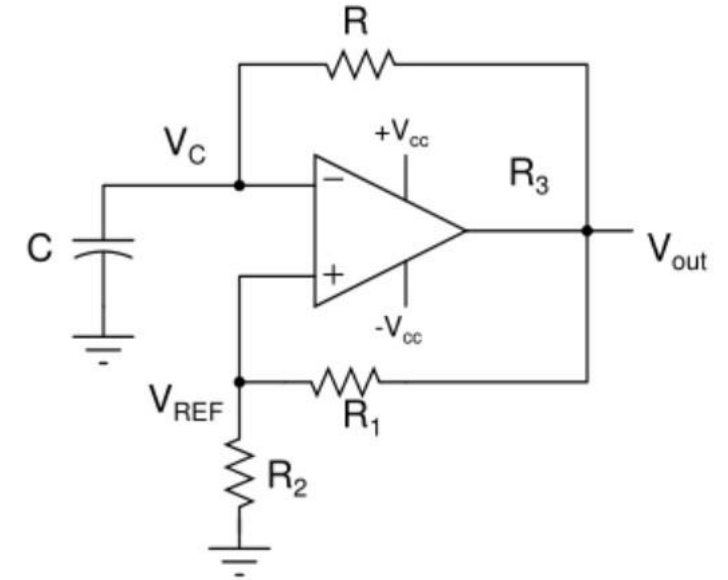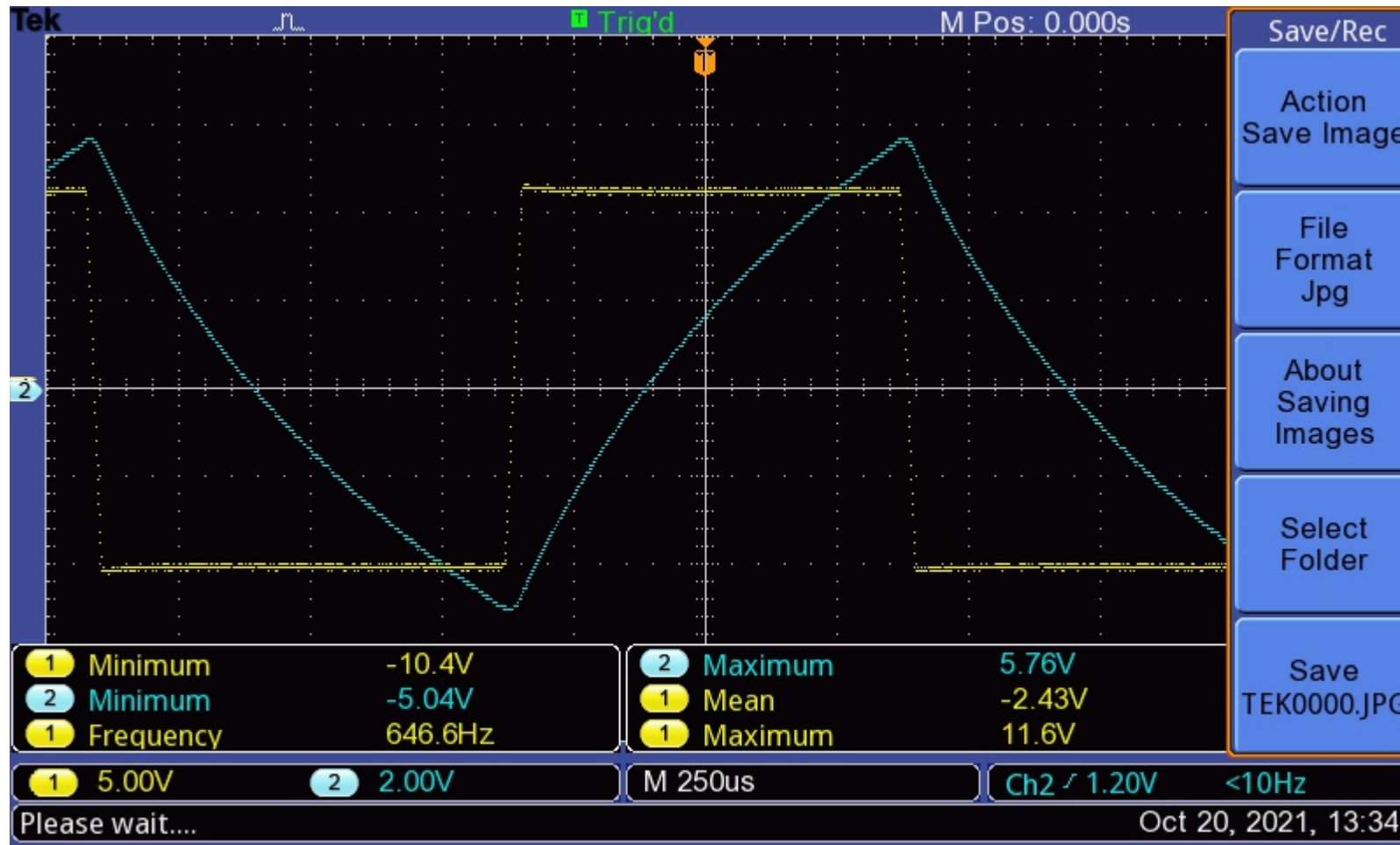- Similar to a Schmitt Trigger Circuit
- +ve feedback (R_1 and R_2)
- Charging of C facilitated through R
- Free-running (astable or quasi stable)
- This is a non-linear circuit (do not get confused with the RC circuit connected to the V_- input)




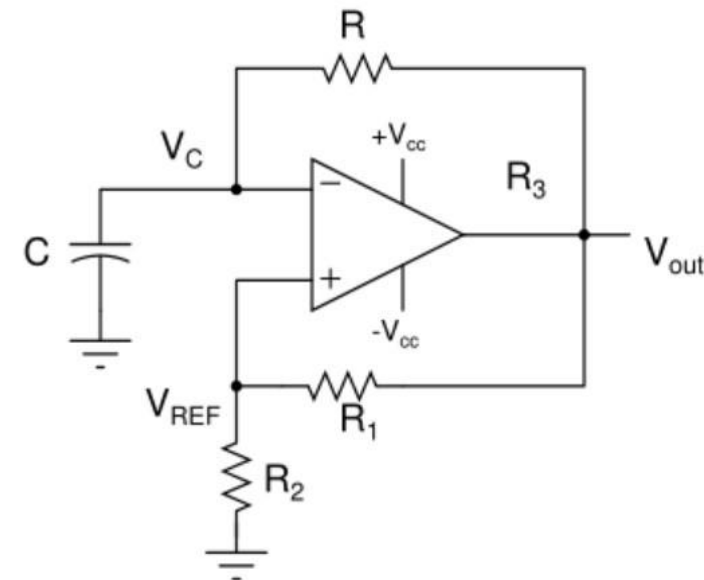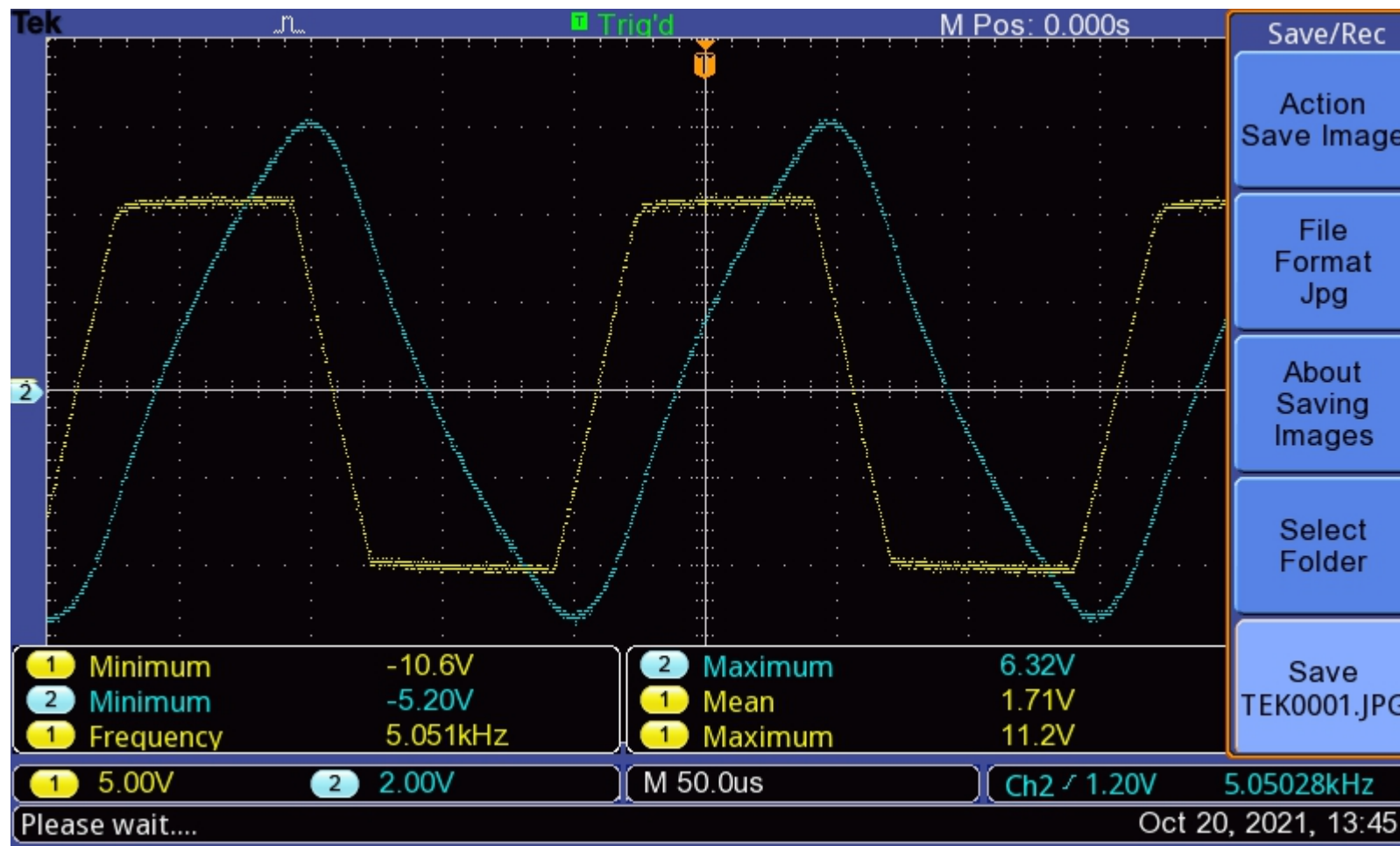- $R = 10 \text{ k}\Omega$, $C = 0.1 \text{ }\mu\text{F}$
- $R_1 = R_2$
- No Zener diodes at the output
- Problems
 - $V_{OH} = 11.6 \text{ V}$
 - $V_{OL} = -10.4 \text{ V}$
 - $T_H \neq T_L$
 - $T_H < T_L$




- $R = 1 \text{ k}\Omega$, $C = 0.1 \text{ }\mu\text{F}$
- $R_1 = R_2$
- No Zener diodes at the output
- Problems
 - $V_{OH} = 11.2 \text{ V}$
 - $V_{OL} = -10.6 \text{ V}$
- $T_H \approx T_L$
- Freq = 5 kHz
- Slew-rate problem

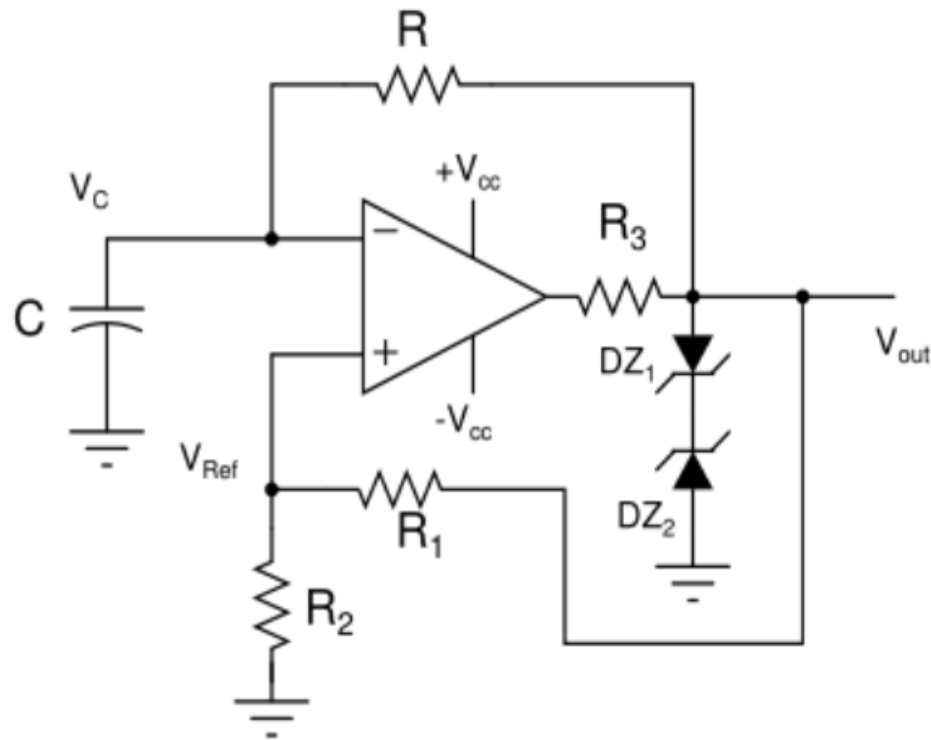Astable Multivibrator – with Zener diodes at the Output



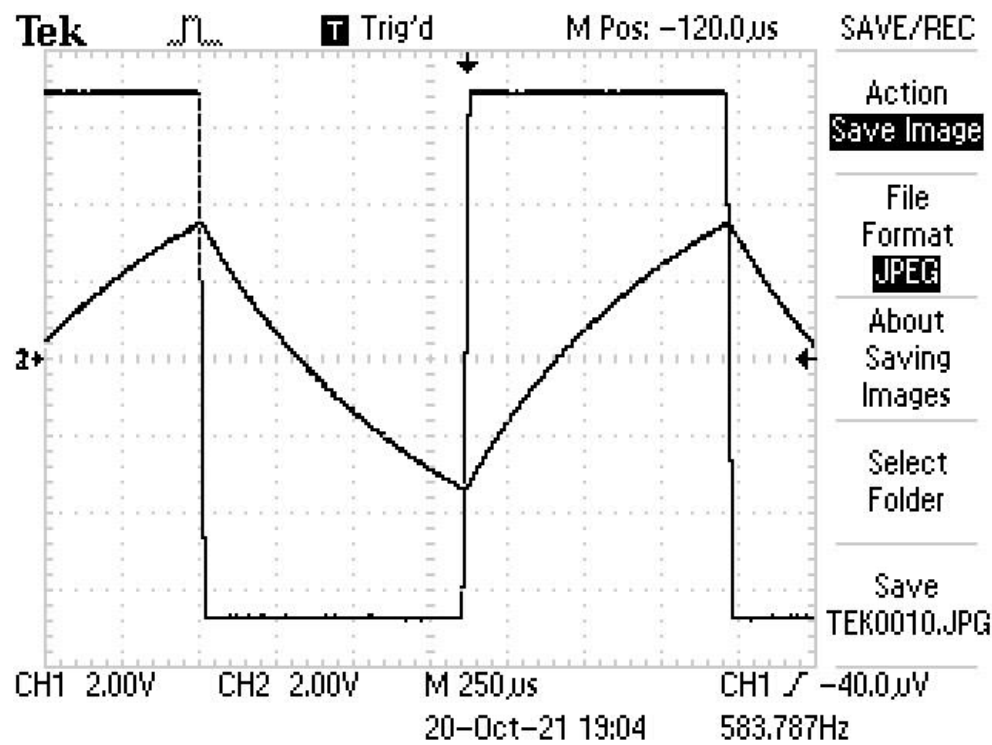
- Zener diodes connected back-to-back
- $V_{OH} = V_{OL}$
- $T_H = T_L$
- Symmetrical square wave
- To some extent, slew-rate limitation can be addressed (by lowering V_{OH} and V_{OL} levels)





$R = 10 \text{ k}\Omega$, $C = 0.1 \text{ }\mu\text{F}$

• $V_{OH} = 7 \text{ V}$

• $V_{OL} = -7 \text{ V}$

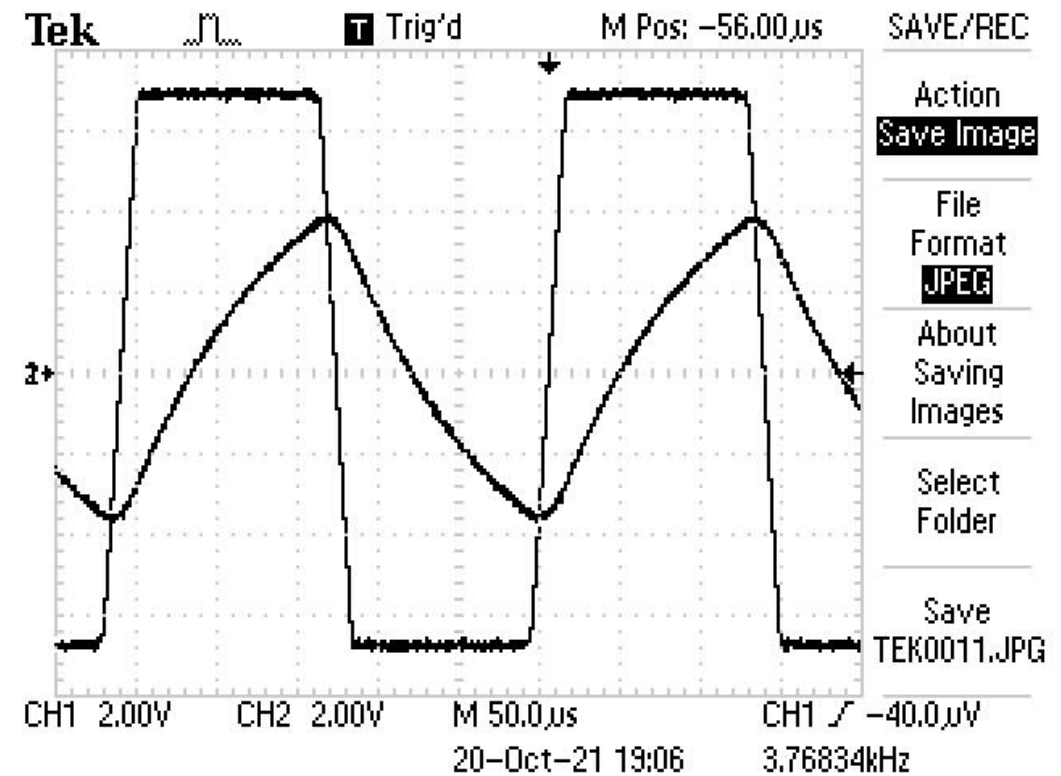

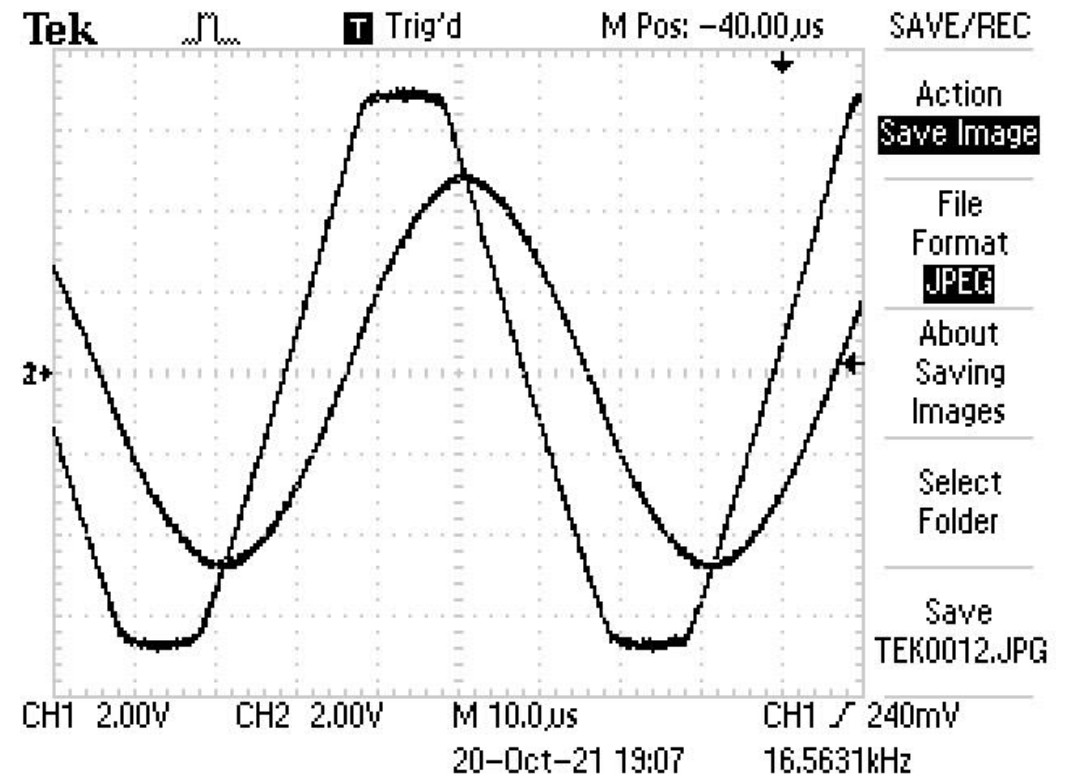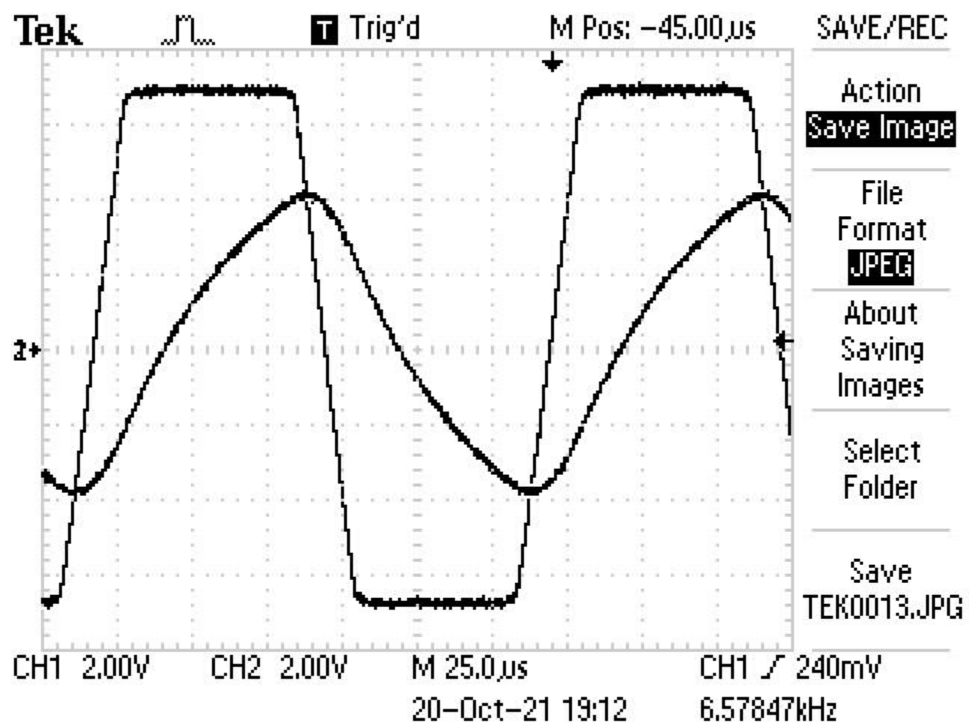
$R = 10 \text{ k}\Omega$, $C = 0.01 \text{ }\mu\text{F}$



$R = 10 \text{ k}\Omega$, $C = 0.005 \text{ }\mu\text{F}$

$V_{OH} = 7 \text{ V}$
 $V_{OL} = -7 \text{ V}$

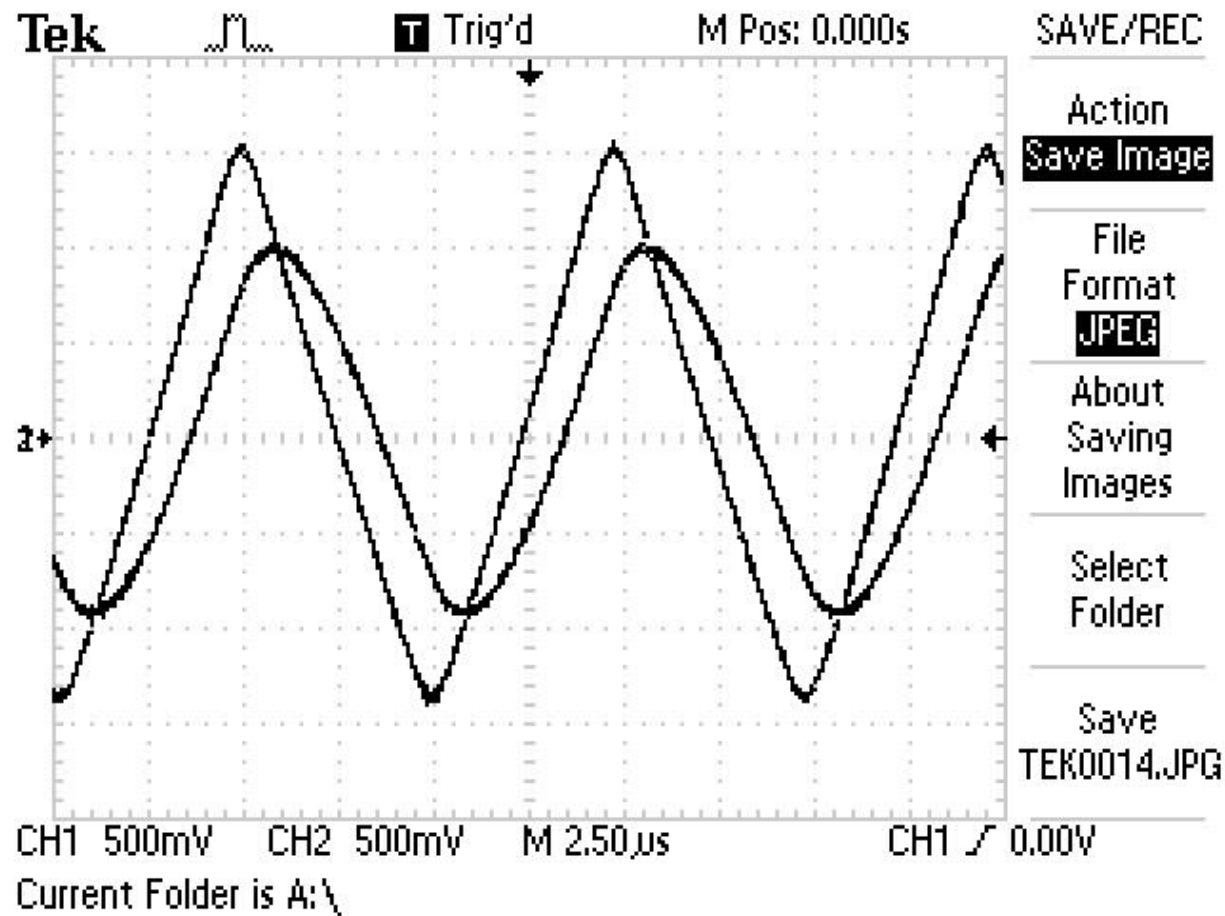$R = 10 \text{ k}\Omega$, $C = 0.001 \text{ }\mu\text{F}$



$R = 10 \text{ k}\Omega$, $C = 0.1 \text{ nF}$

- $V_{OH} = 1.5 \text{ V}$
- $V_{OL} = -1.5 \text{ V}$

Announcements

- Quiz 8 – corrections – nearly over
- Endsem Exam – Oct 29 Fri
 - Two parts:
 - First part – SAFE Auto corrected, 1 hr ; 2:00 – 3:00pm
 - Second part - Fully image answers (conventional answer paper, with Question paper through SAFE): 1 hr, 3:30-4:30pm