

Expt 8 – Precision Rectifier and Active Filters

Oct 1, 2021 (Friday)

EE 230 Analog Circuits Lab

Joseph John

2021-22/I


Summary

- Precision Rectifiers
 - Half-wave Precision Rectifier - Standard circuit
 - Improved Half-wave Precision Rectifier (Circuit A)
 - Improved Half-wave Precision Rectifier (Circuit B)
 - Precision Full-wave Rectifier
- Active Filters
 - Single-pole (LPF and HPF)
 - Sallen-Key (2-pole) – LPF and HPF

Precision Rectifiers


- Rectifier circuits diode drops neglected (as these drops typ. 0.7 V)
 - were much smaller compared to the input ac signal, roughly $20 \sin \omega t$.
- What about if the signal (to be rectified) – of the order of the diode drops or much smaller.
- We can combine a diode and an Opamp (with negative feedback)
 - Problem can be easily addressed.
 - Combination of an Opamp and a diode is often called a 'Super diode' or a 'Precision Rectifier' circuit.

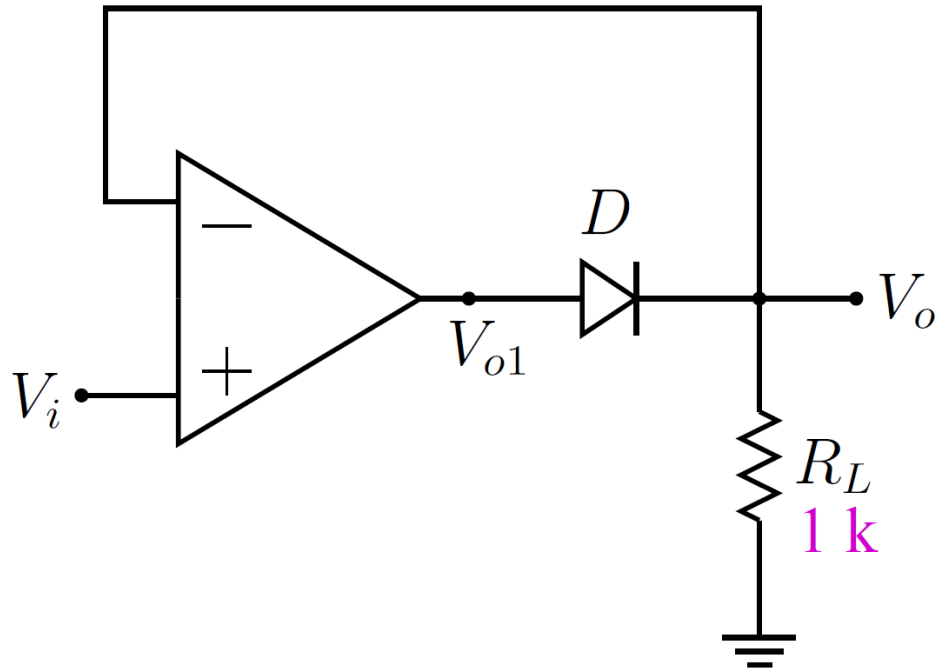Half-wave Precision Rectifier - Standard circuit




Half-wave rectifier

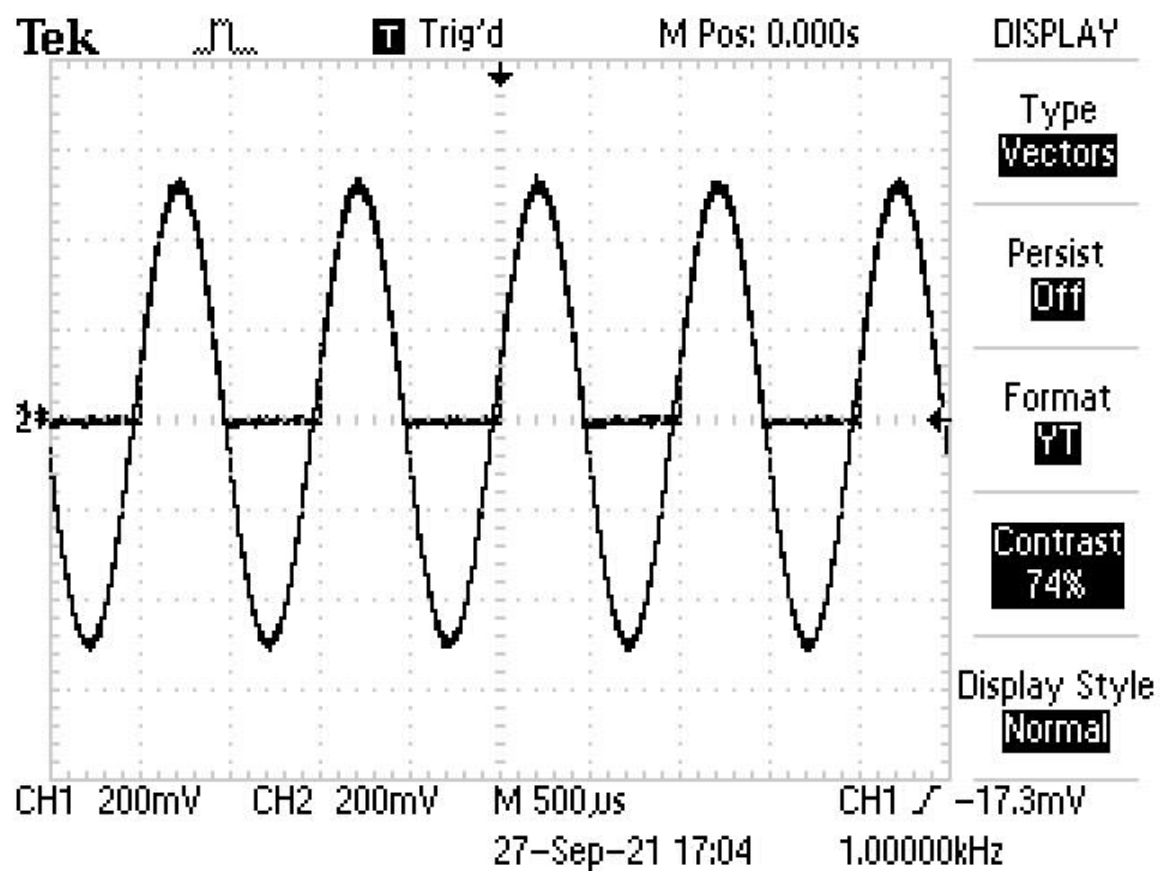
- Here, $V_o = V_i$, when $V_i > 0$;
 $V_o = 0$, when $V_i < 0$
- Problems
 - When $V_i < 0$, Opamp is saturated
 - Will affect its switching speed



V_o

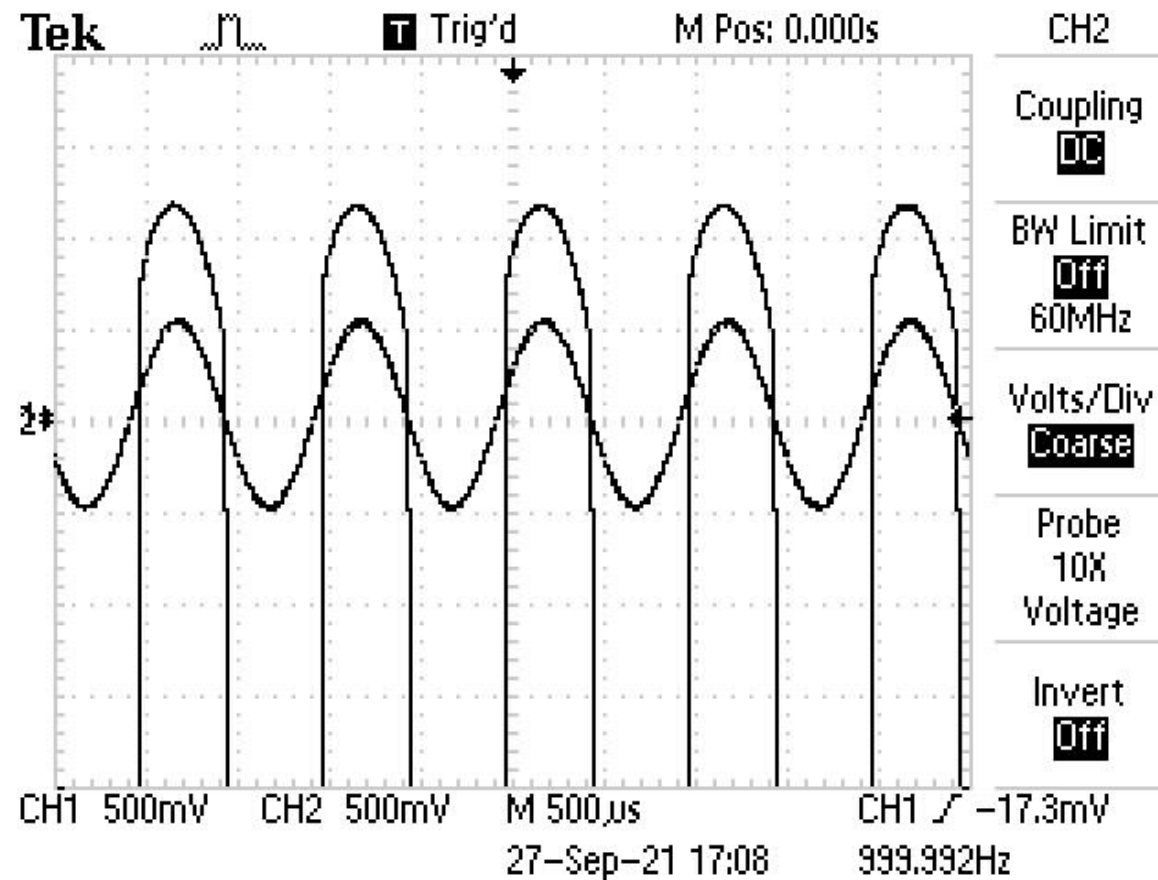


V_{o1}

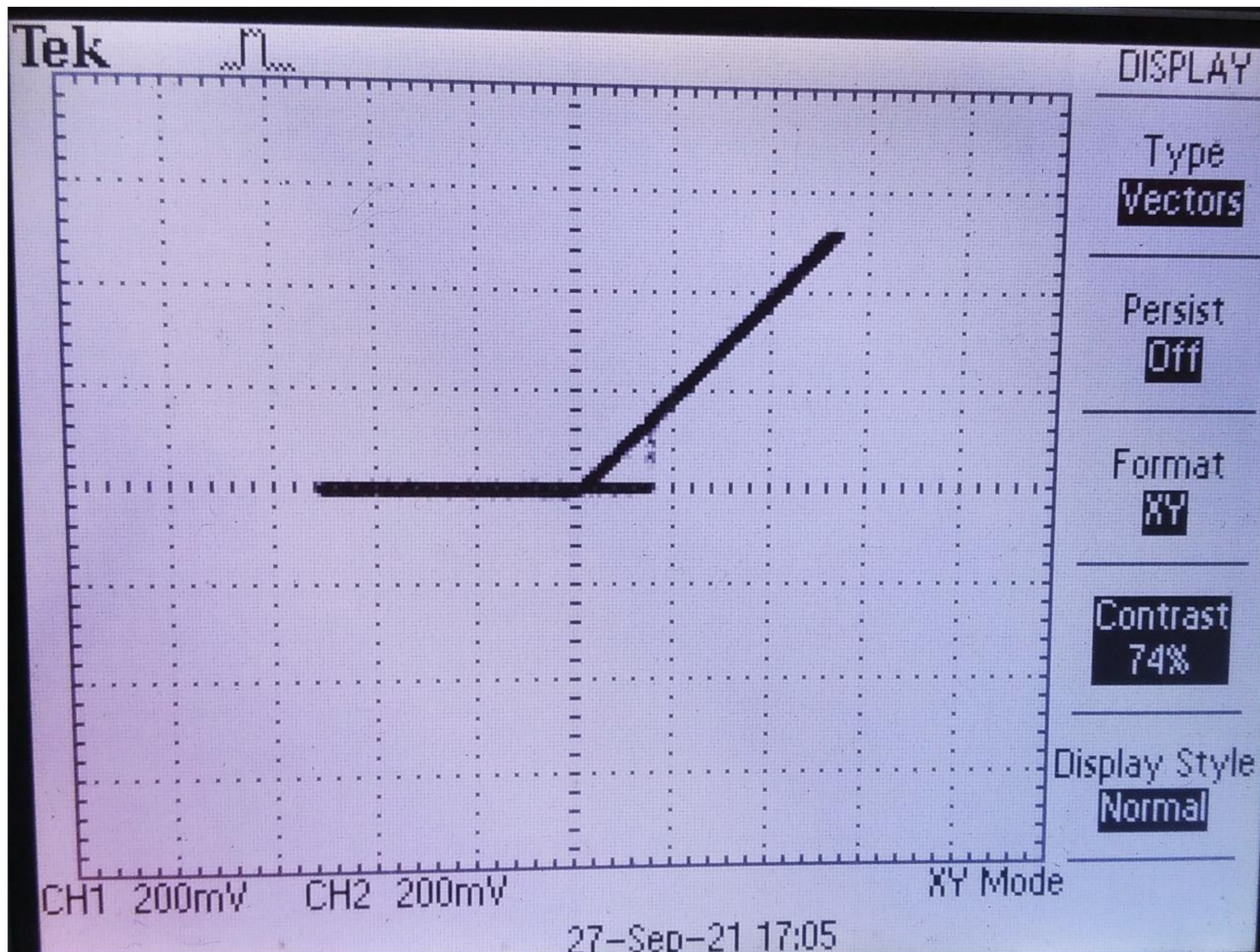


V_o vs V_i

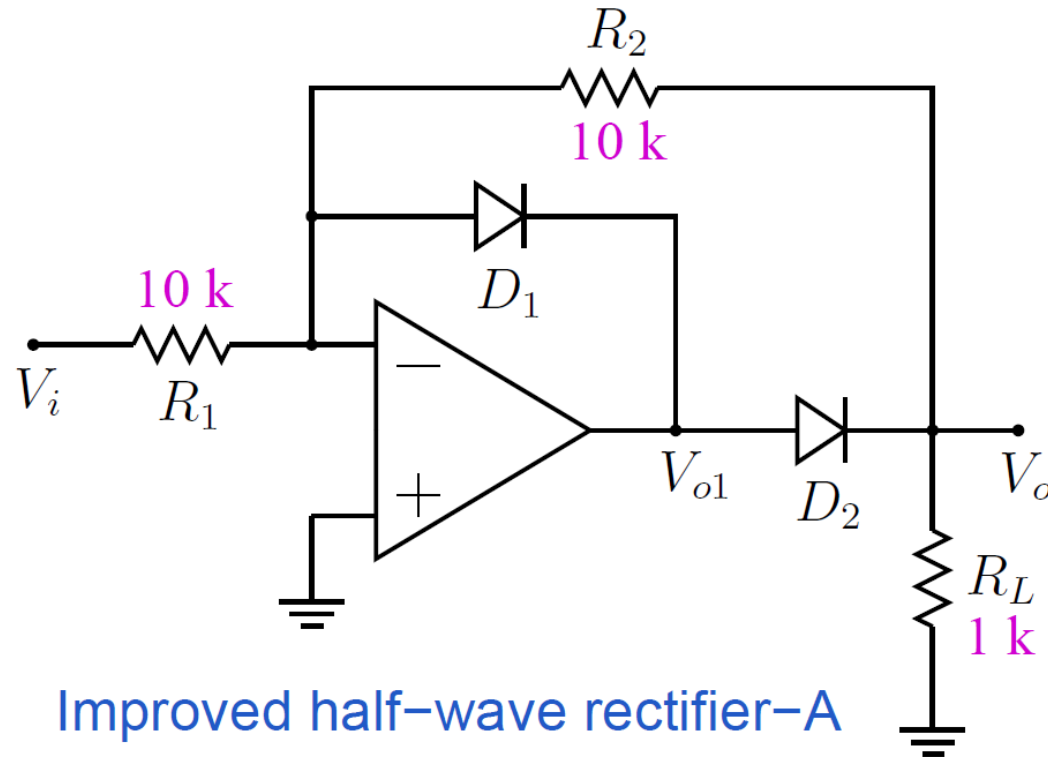Improved Half-wave Precision Rectifier (Circuit A)




Improved half-wave rectifier-A

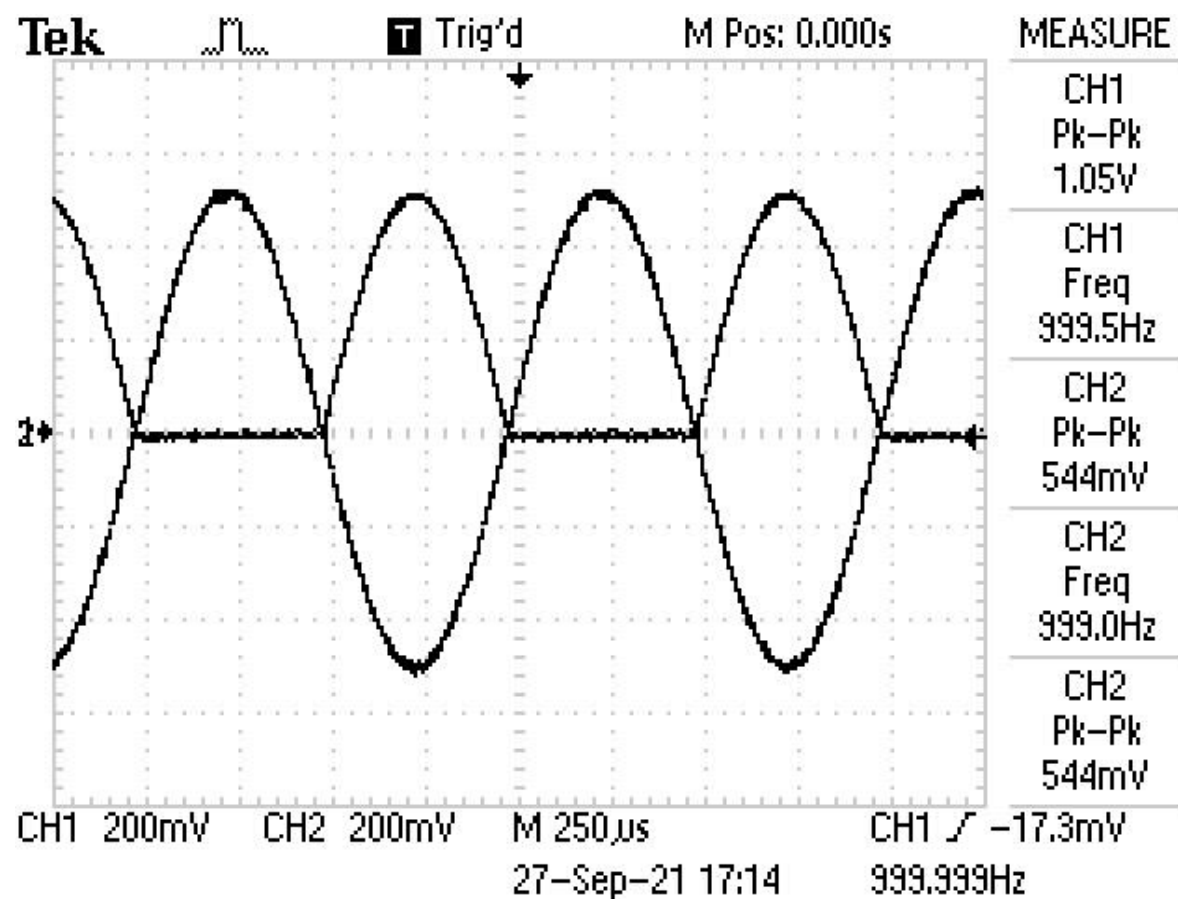- One more diode introduced
- Opamp in linear region at all times
- Speeds improved




V_o

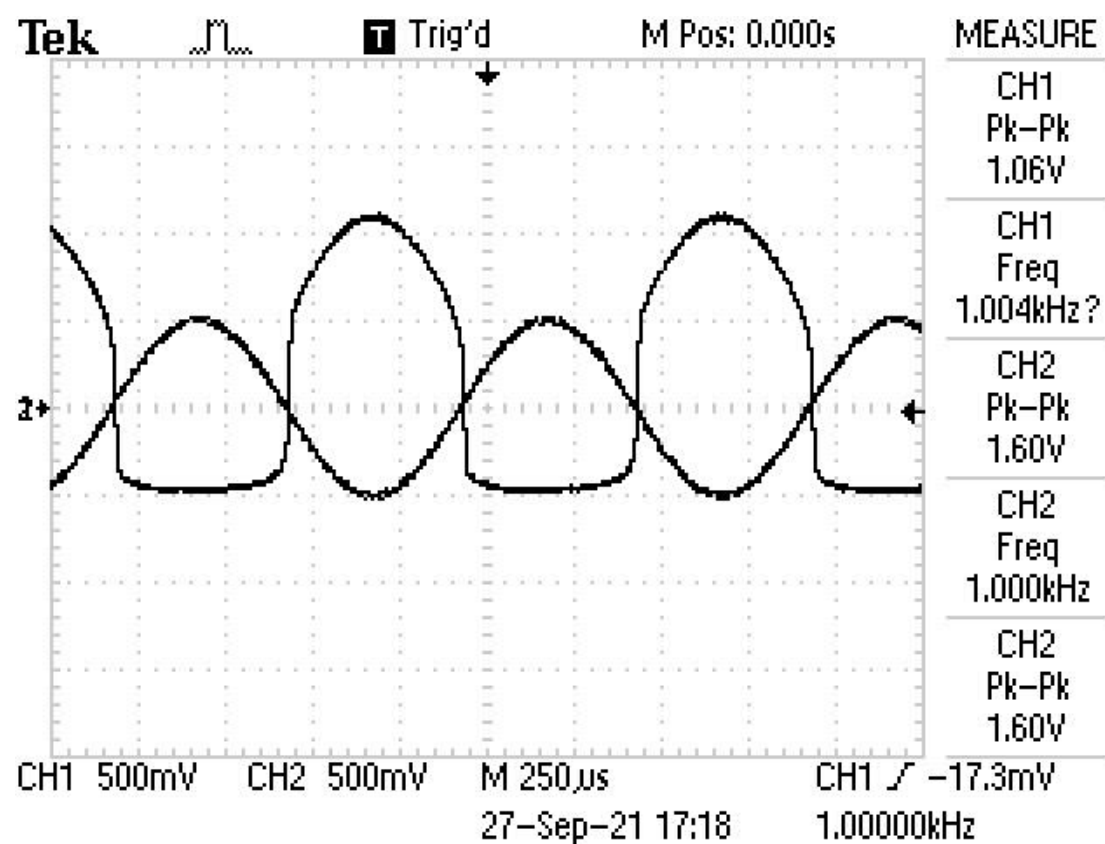

V_{o1}

lek

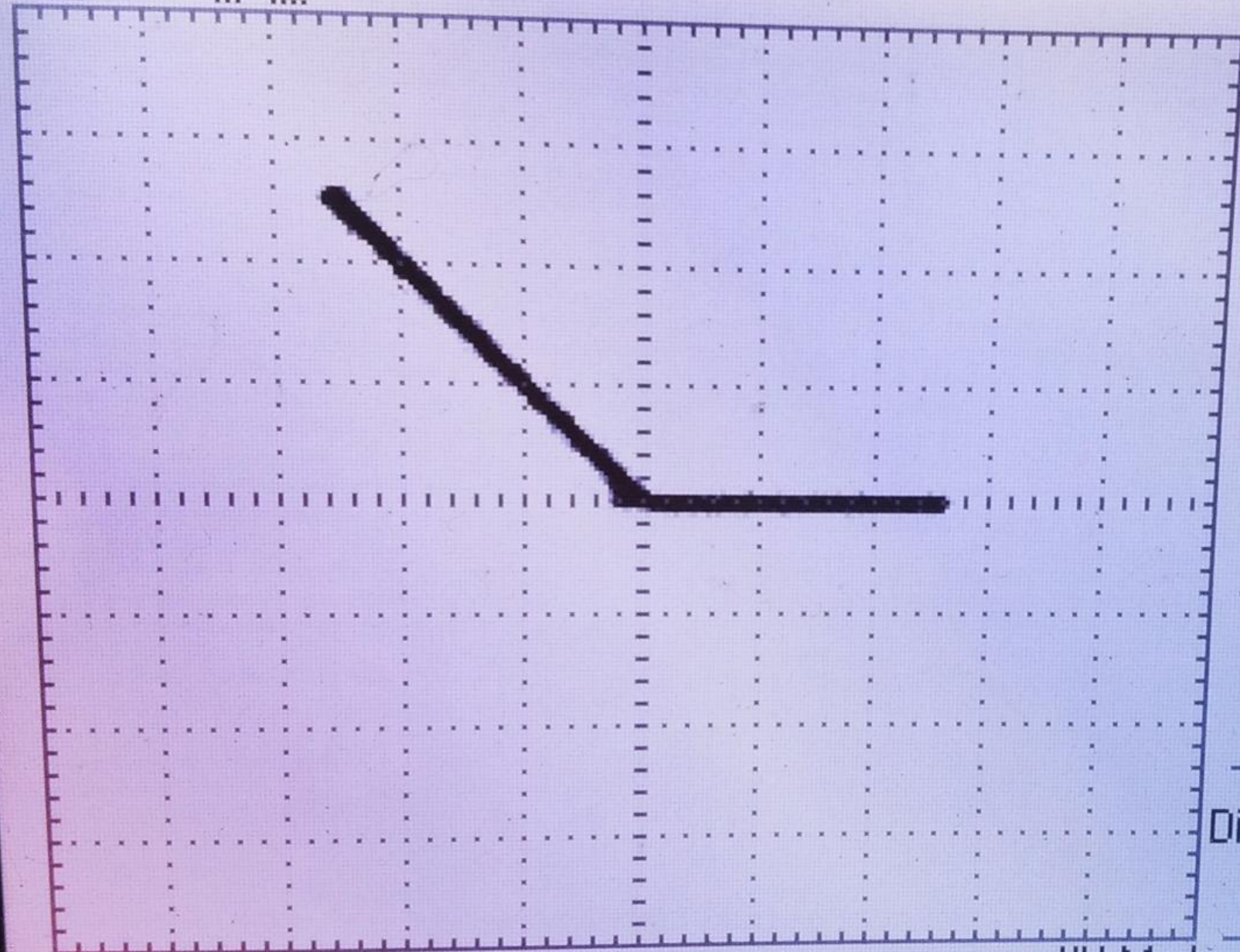

CH1 200mV CH2 200mV

XY Mode

27-Sep-21 17:16

DISPLAY

Type

Vectors

Persist

Off

Format

XY

Contrast


74%

Display Style


Normal

V_o vs V_i

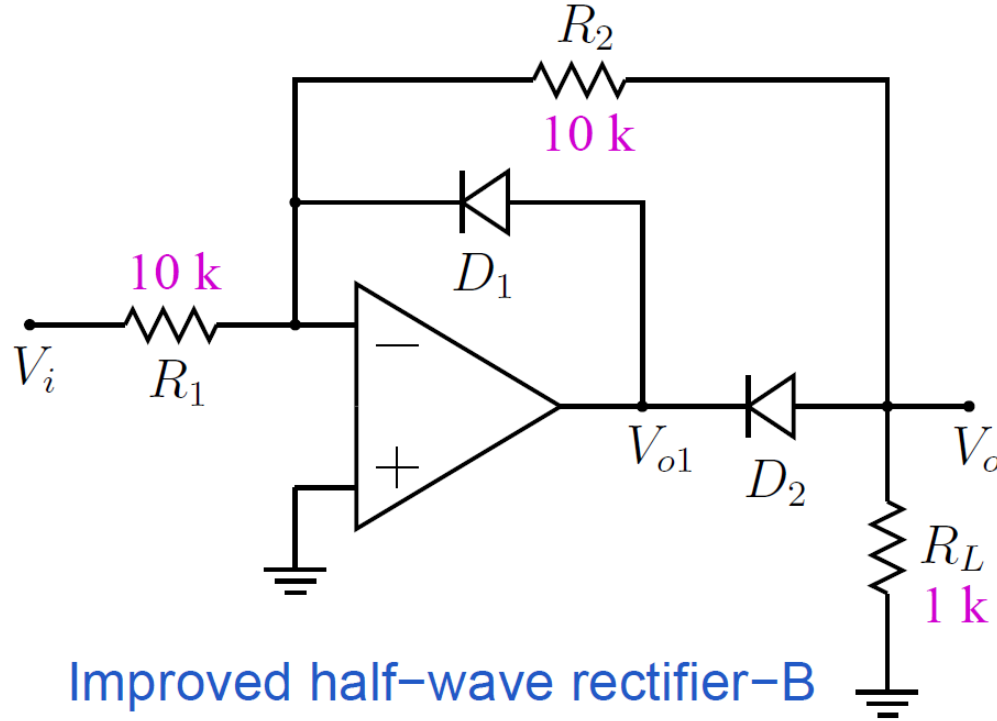
Improved Half-wave Precision Rectifier (Circuit B)



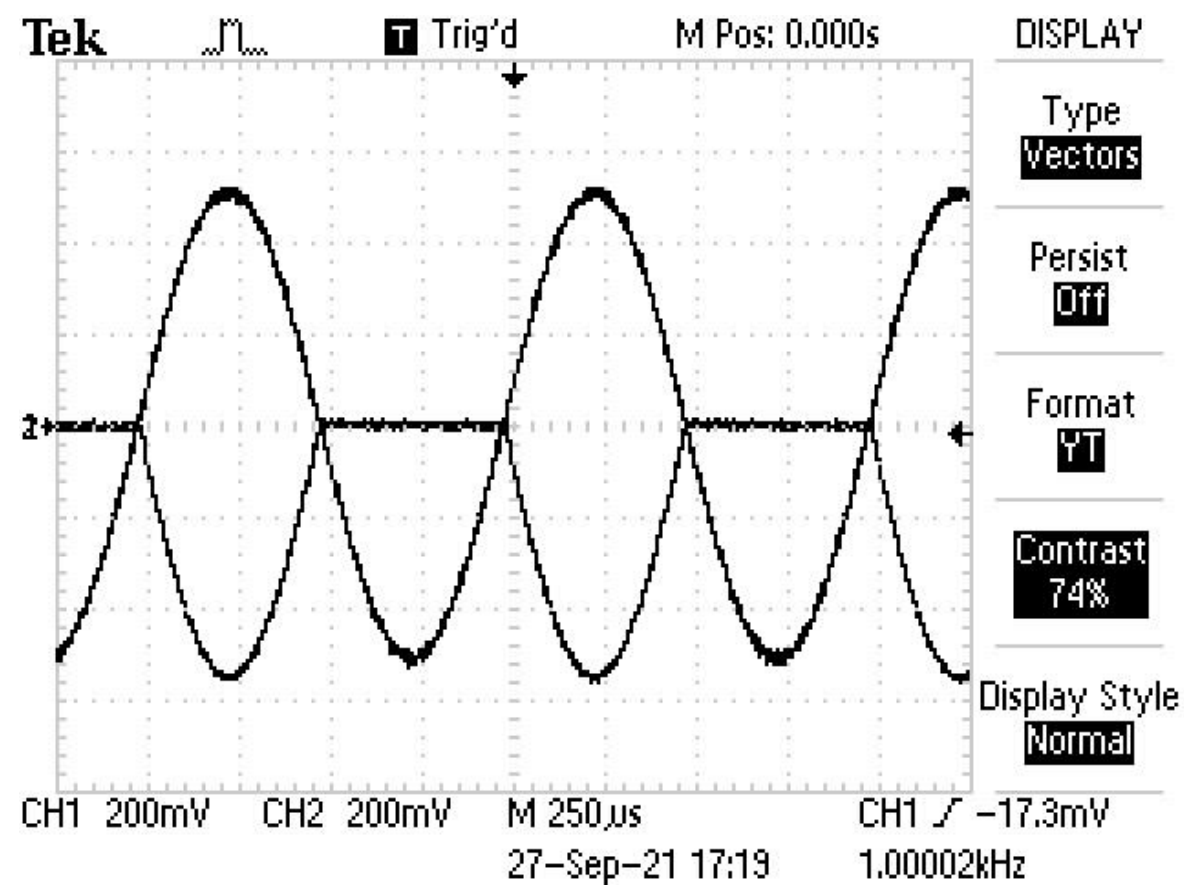
- One more diode introduced
- Opamp in linear region at all times
- Speeds improved



V_o

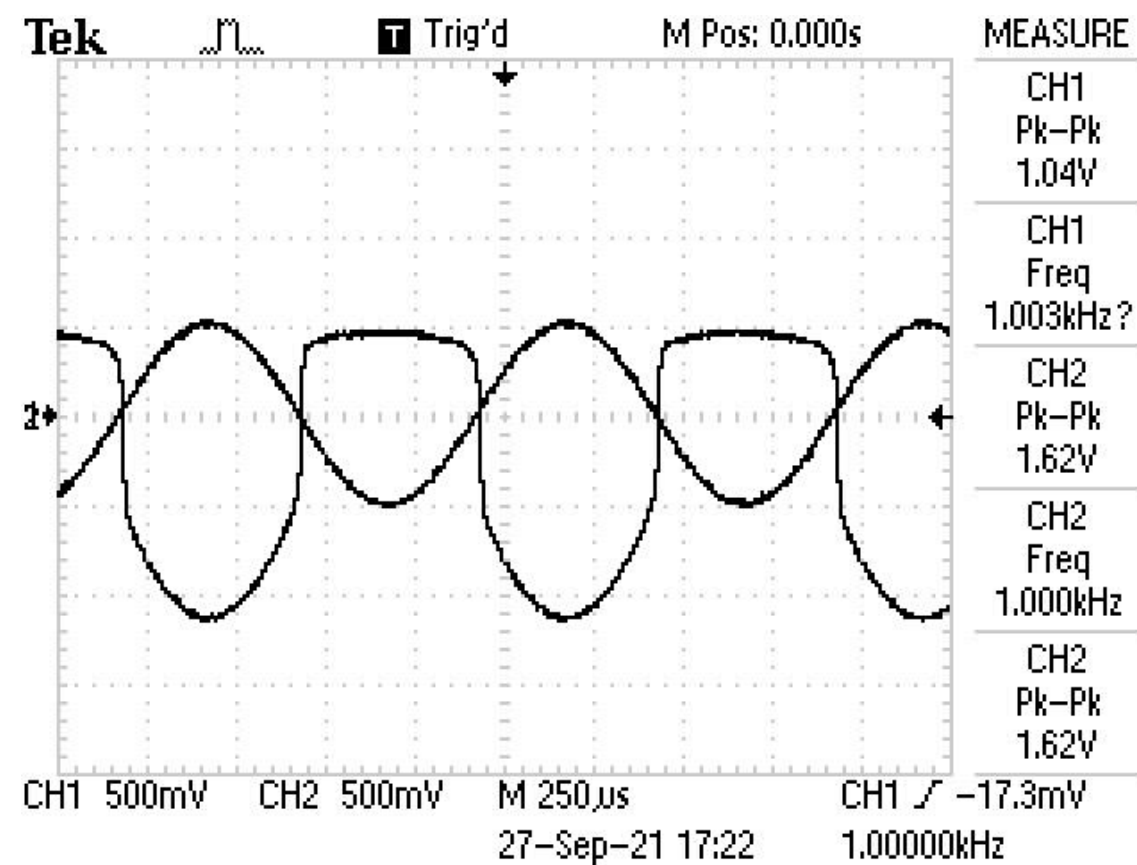


V_{o1}

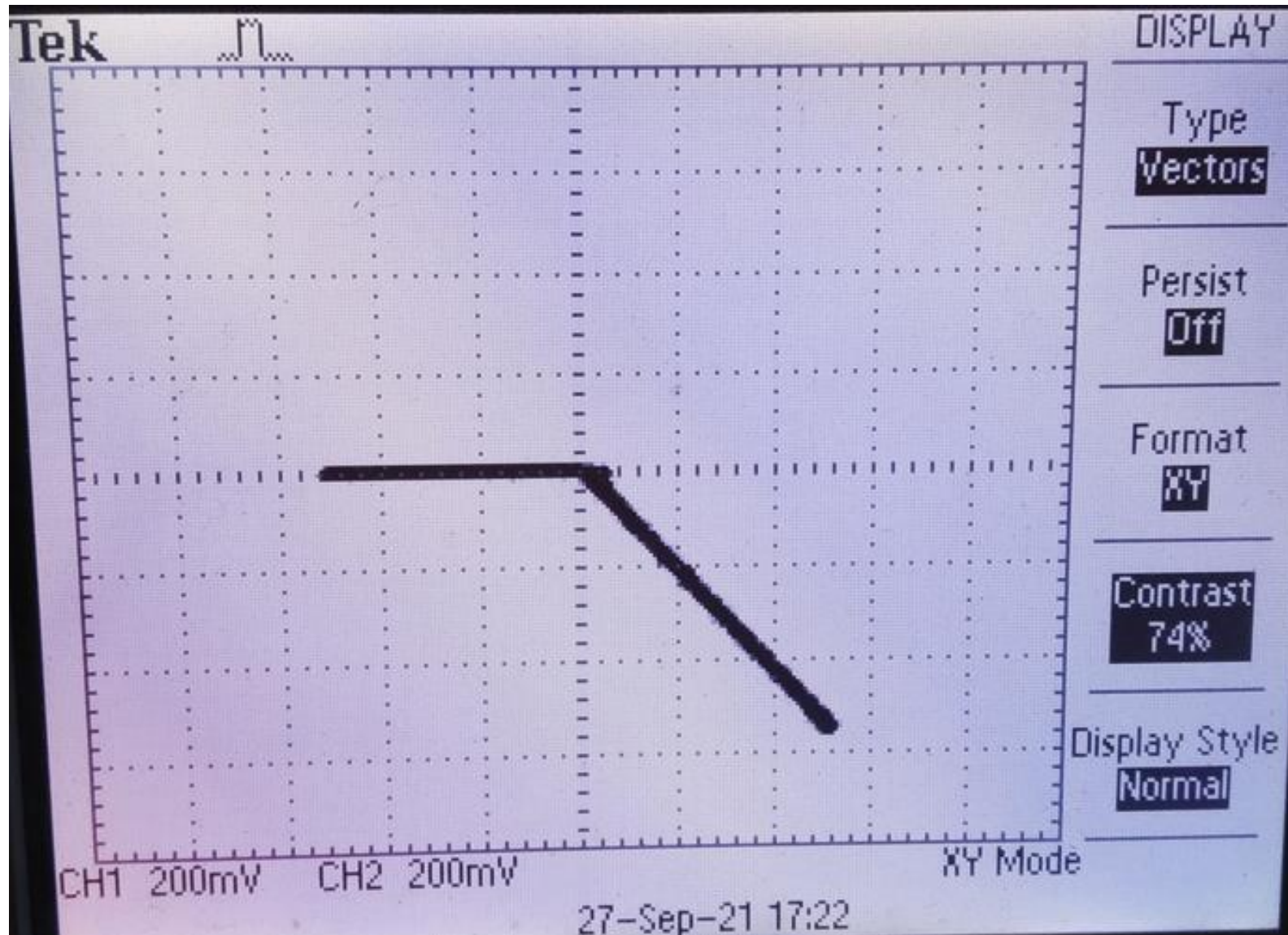


V_o vs V_i


Precision Full-wave Rectifier

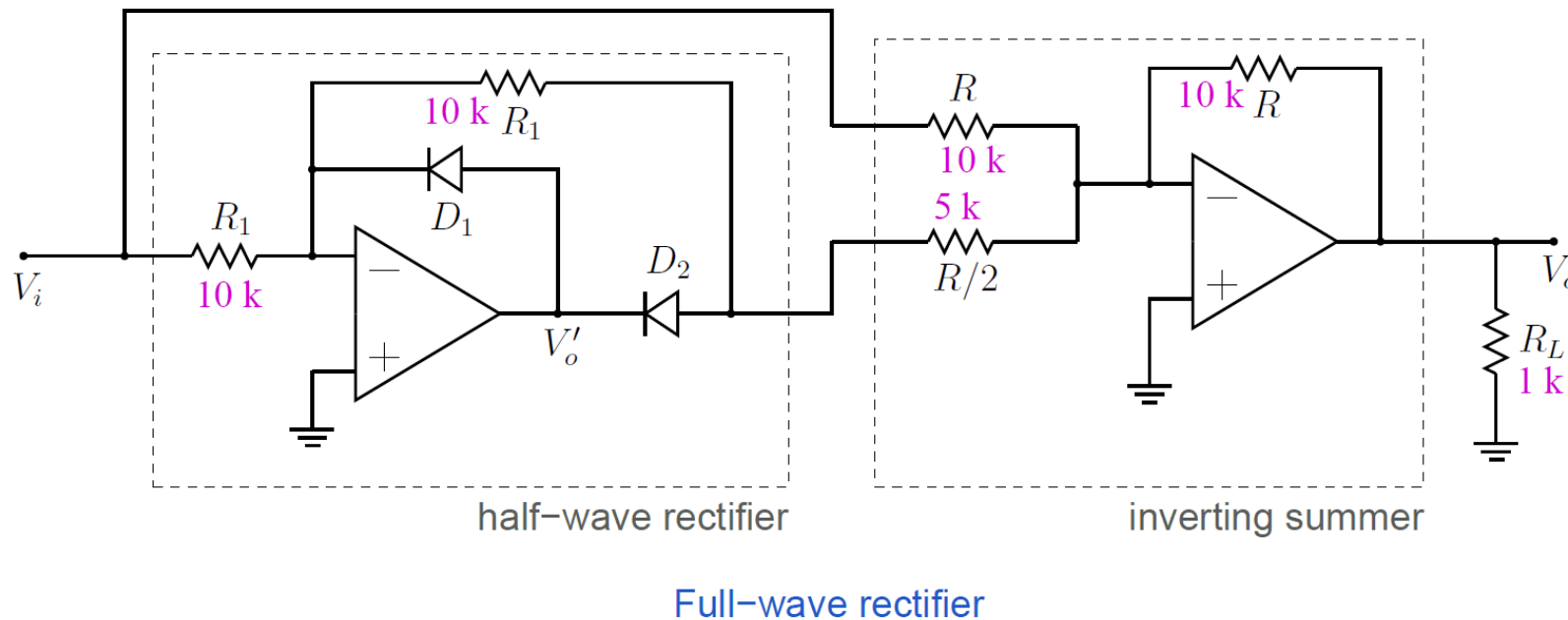

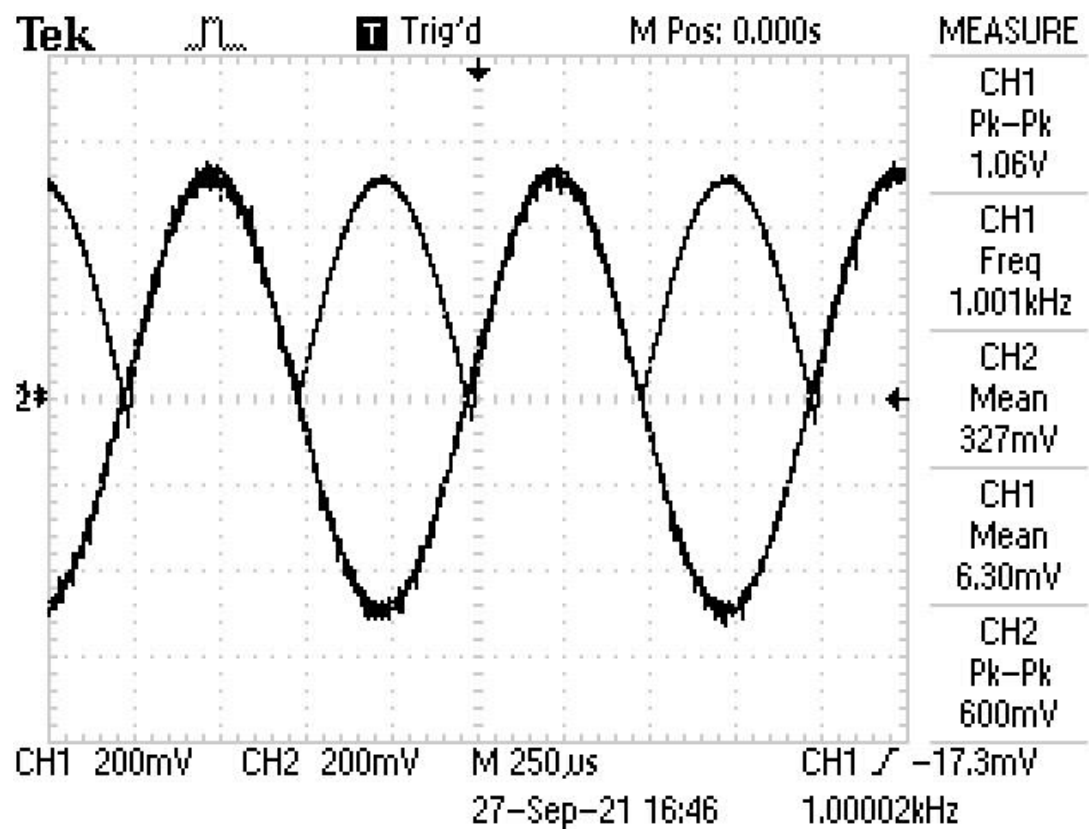- Combination of a Half-wave and an inverting summer
- Half-wave rectifier output combined with V_i through a summer.




V_o

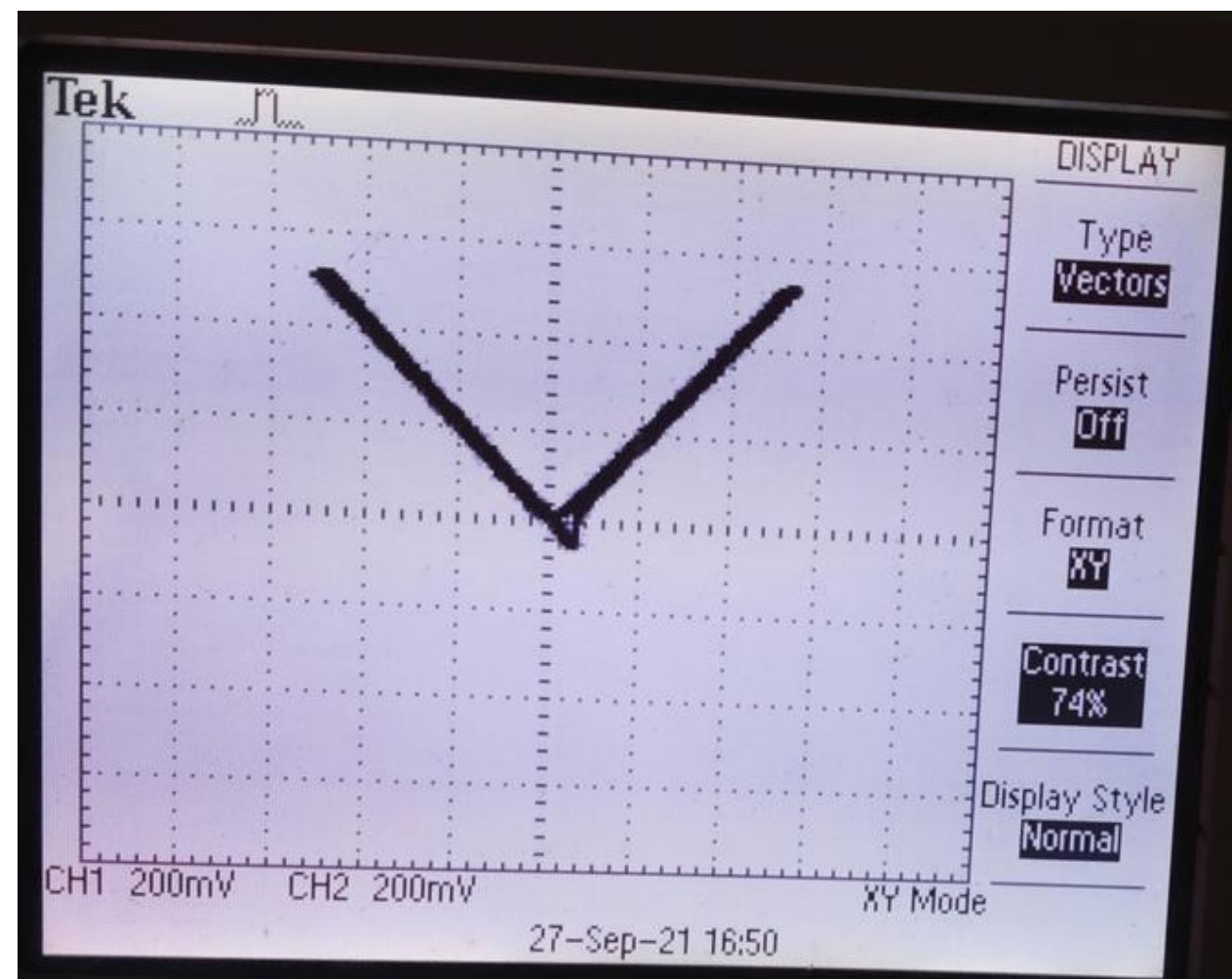

V_o vs V_i

Single-pole Active Low-pass Filter

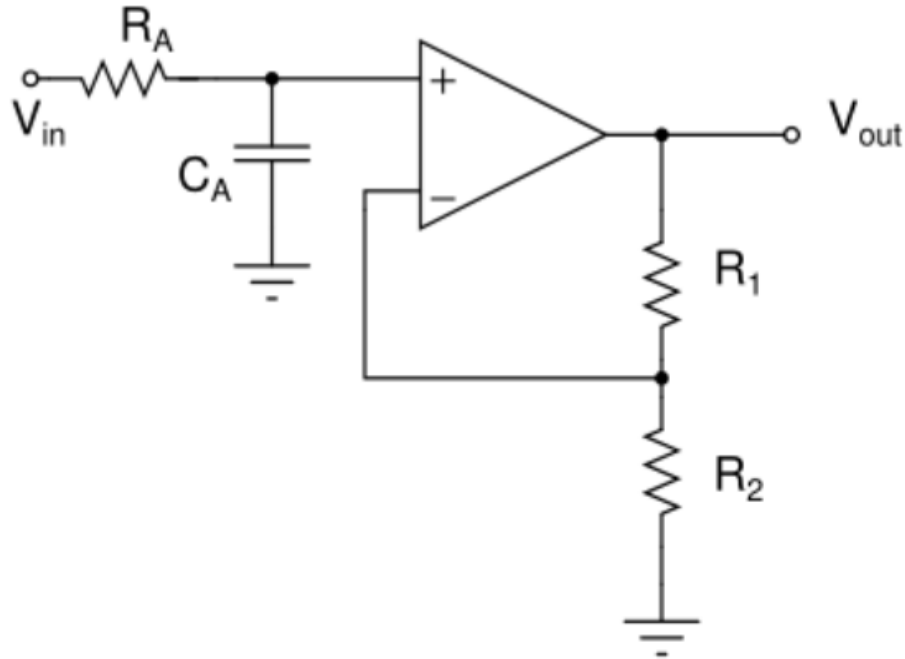


- Very popular
- Can avoid using inductors
- Gain can be provided
- RC filter + a non-inverting amplifier
- Single-pole (-20 dB/decade roll-off)

- Circuit values:

$$R_A = 4.7 \text{ k}\Omega, C_A = 0.1 \text{ }\mu\text{F}, R_1 = 9.1 \text{ k}\Omega, R_2 = 1 \text{ k}\Omega$$


$$\text{Voltage gain} = 10$$

Single-pole Active High-pass Filter

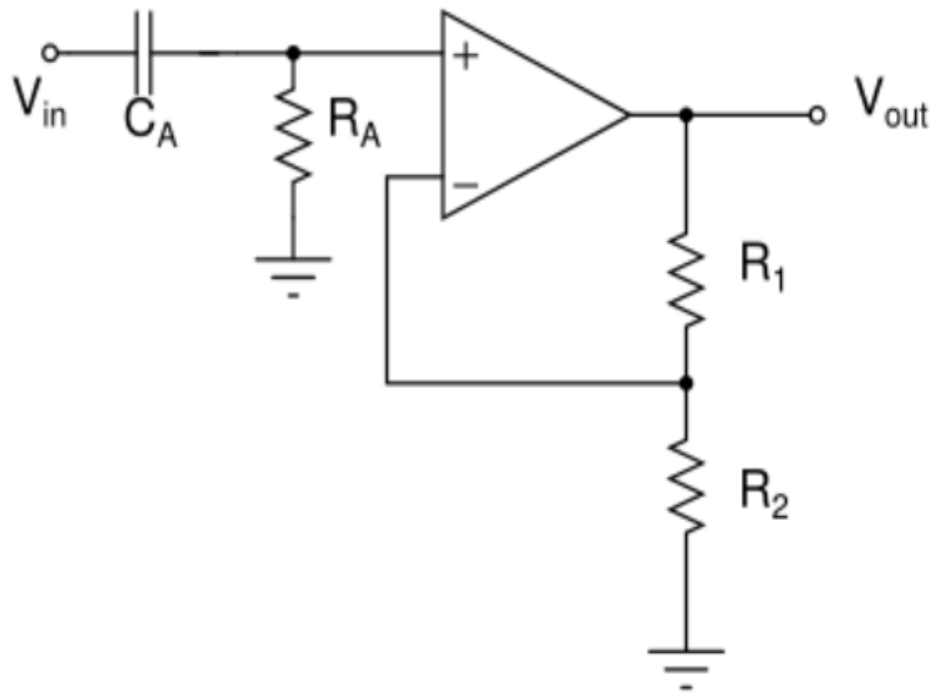


- RC filter + a non-inverting amplifier
- Single-pole (-20 dB/decade roll-off)
- Circuit values:
 $R_A = 4.7 \text{ k}\Omega$, $C_A = 0.1 \text{ }\mu\text{F}$,
 $R_1 = 9.1 \text{ k}\Omega$, $R_2 = 1 \text{ k}\Omega$
- Voltage gain = 10

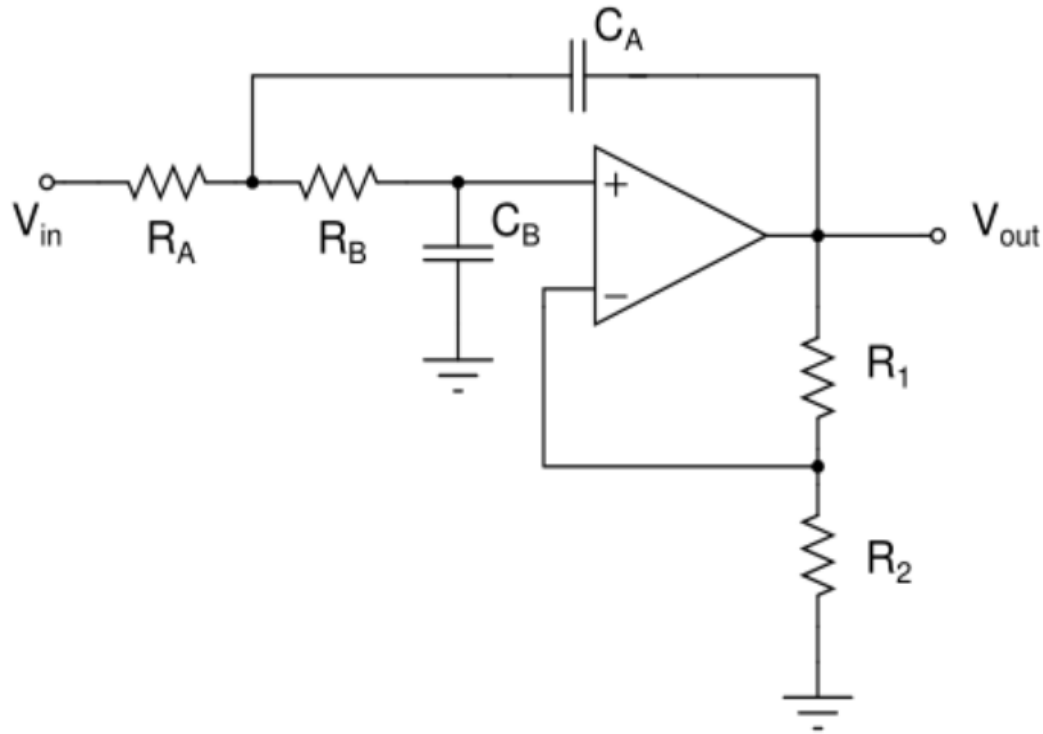Sallen-Key (2-pole) Active Low-pass Filter




- 2-pole filter
- -40 dB/decade roll-off
- Need to choose R_1 and R_2 carefully (to take care of damping factor)

20 x log10(G) ----->

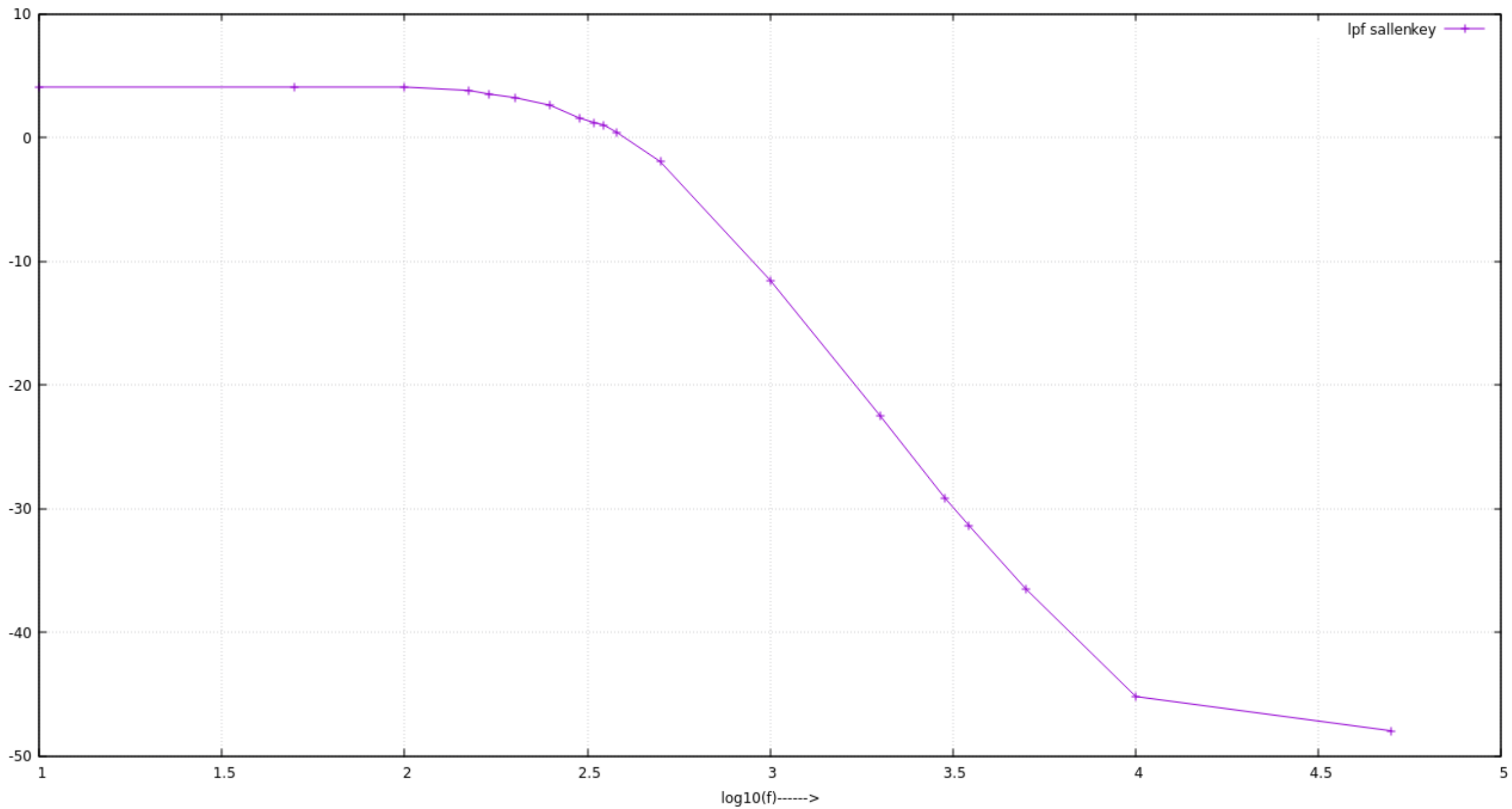


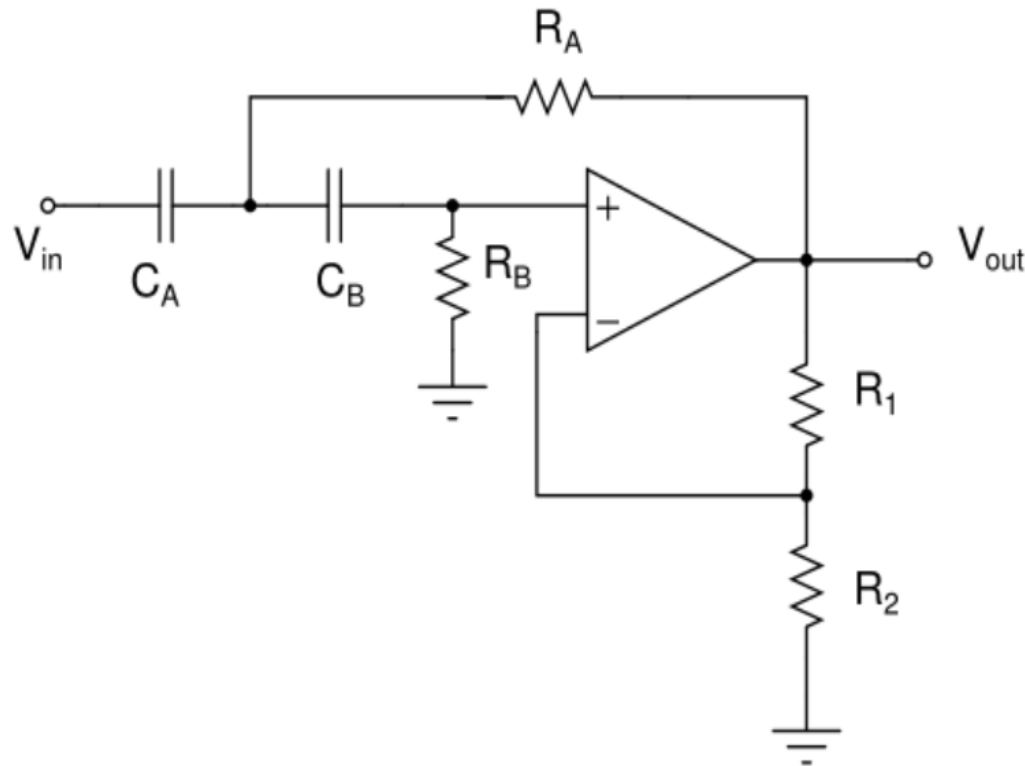Sallen-Key (2-pole) Active High-pass Filter



- 2-pole filter
- -40 dB/decade roll-off
- Need to choose R_1 and R_2 carefully (to take care of damping factor)

20 x log10(G) ----->

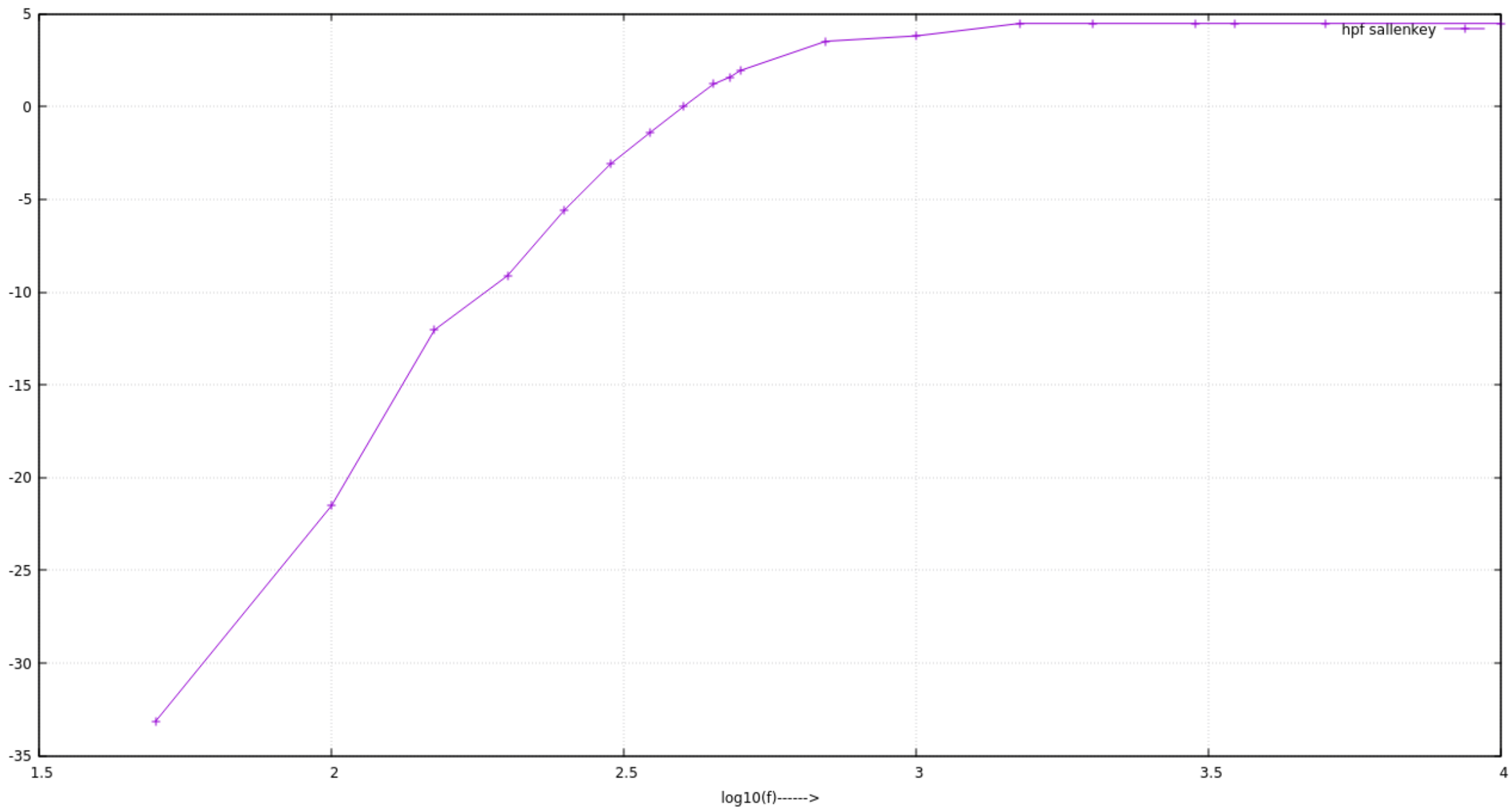

Announcements

- Expt Handout of Expt 8 (please use only Ver 3, Oct 1)
 - Mistakes corrected (Ver 2.1, Sep 29): Lab Report: both Precision Rectifiers and Active Filters
 - Mistakes corrected (Ver 3, Oct 1): Sec 2.2 and Sec 2.3 - $R_1 = 9.1 \text{ k}\Omega$, $R_2 = 1 \text{ k}\Omega$
- Doubts – both Expt 7 and Expt 8